

A Workflow for the Design of Mixed-signal Systems with Asynchronous Control

Vladimir Dubikhin, Danil Sokolov, Alex Yakovlev, Chris J. Myers

AMS Trends & Challenges

Key Drivers

- Internet of Things
- Mobile computing
- Automotive electronics

Trends

- Technology scaling
- Multiple power and time domains
- Analog and digital integration

Challenges

- Tighter reliability margins
- Concurrent analog and digital analysis
- Short development cycle

What this means for AMS?

- **Achieving better verification of *analog and digital blocks***
- **Verifying the increasing amount of digital logic in analog designs**
- **Creating a *higher level of abstraction* for analog and mixed signal blocks**
- **Automating the manual custom design steps**
- **Adopting *circuit analytics* that tell *why* and *where* the circuit is failing to perform**

Why Asynchronous Logic?

- **Insensitive to delays**
- **Robust to process-voltage-temperature**
- **Average case performance**
- **Low power consumption and EMI**

Why Asynchronous Logic?

- **Insensitive to delays**
- **Robust to process-voltage-temperature**
- **Average case performance**
- **Low power consumption and EMI**
- **Incompatible with commercial EDA tools**

Workcraft

- Modeling with signal transition graphs (STG)
- Formal verification of STG models
- Logic synthesis of asynchronous circuits

celement2null [STG]

Property editor

A name	A
A type	input
B name	B
B type	input
C name	C
C type	output

Tool controls

Editor tools

Output

```
# EQN file for model /tmp/STG5873461039858768952
# Generated by petrify 4.2 (compiled 15-Oct-03 at 3:06 PM)
# Outputs between brackets "out" indicate a feedback to input "out"
# Estimated area = 1.00

INORDER = A B C;
OUTORDER = [C];
[C] = B;

# No set/reset pins required.
```

Workspace

- External
 - celement2.work

Why Formal Verification?



- **Increased robustness of the system**
- **Abstract modeling**
- **Reduced need for conventional simulation**

Why Formal Verification?


- **Increased robustness of the system**
- **Abstract modeling**
- **Reduced need for conventional simulation**
- **Limited tool support**

LEMA

 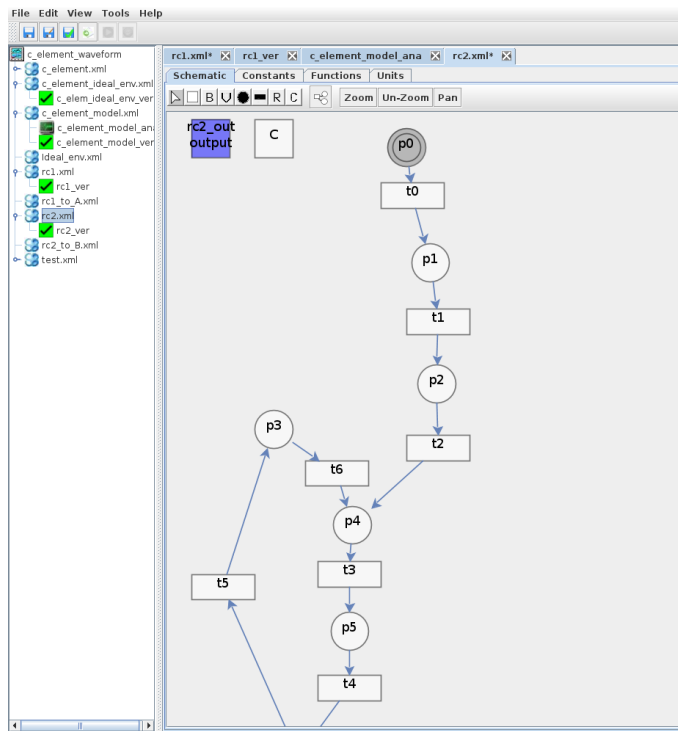- Modeling with labeled Petri nets(LPN)
- Automatic model generation
- Property expression and checking
- Model extraction as SystemVerilog netlist




LEMA Tool Flow

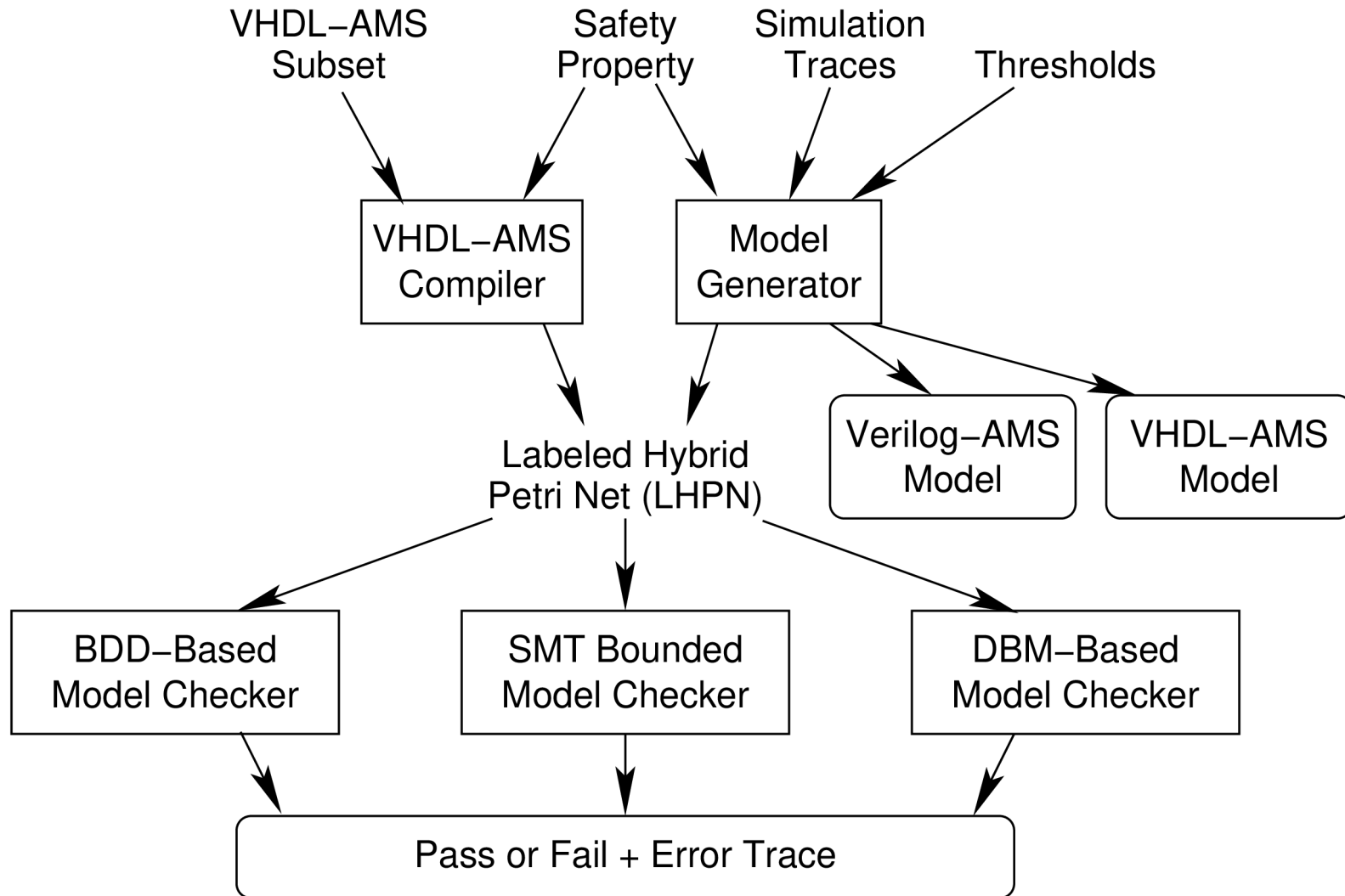


Labeled Petri Nets (LPNs)

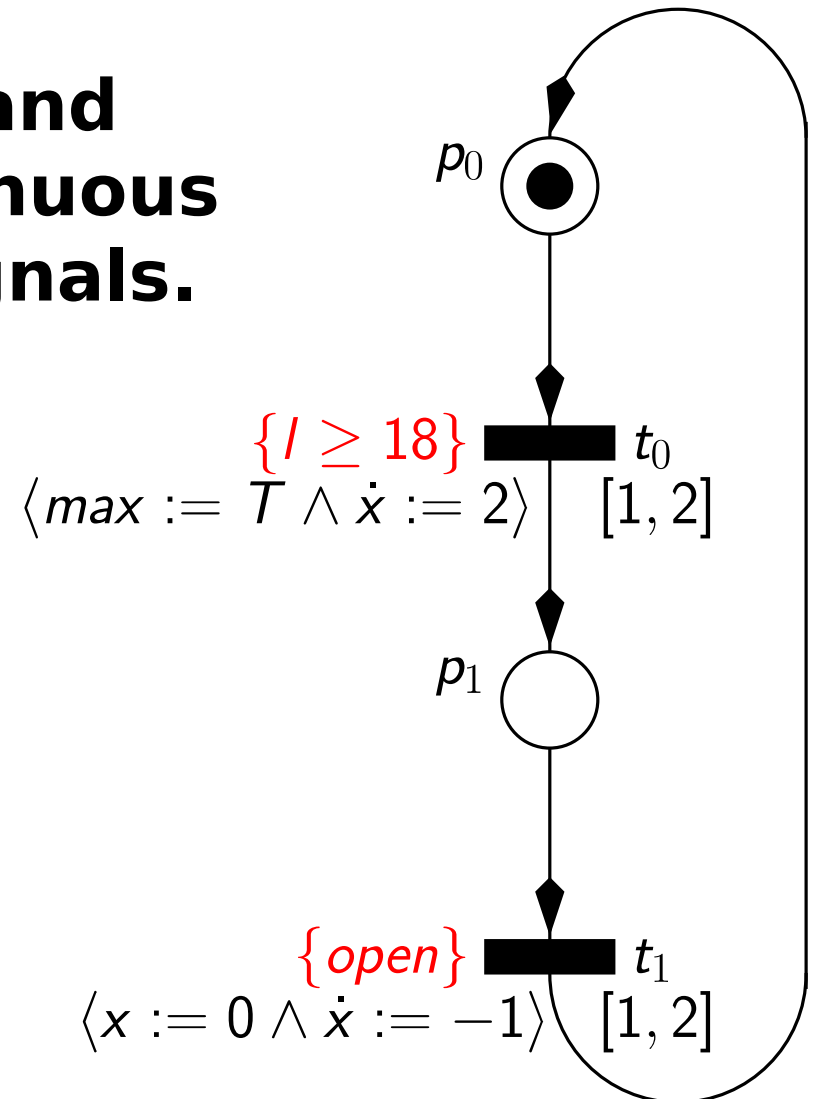- Composed of a Petri net and labels operating on continuous variables and Boolean signals.
- Label types are:
 - **Enablings**
 - **Delay bounds**
 - **Boolean assignments**
 - **Value assignments**
 - **Rate assignments**




LPN Model Generation

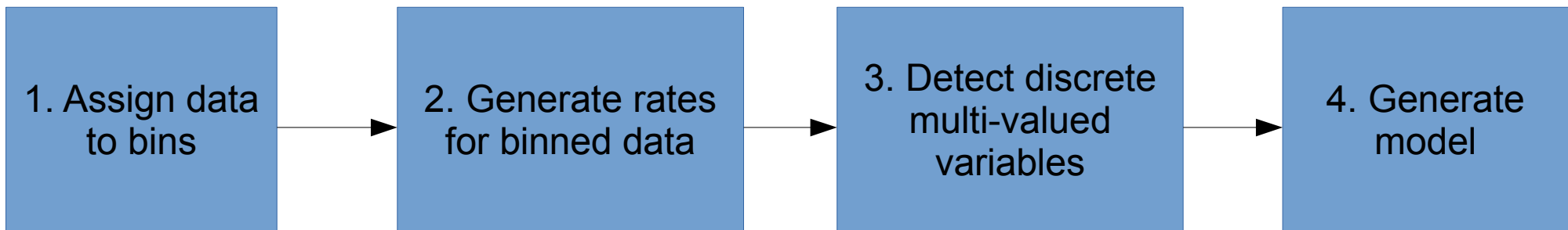- **Build abstract models of the circuit using:**
 - **Simulation traces.**
 - **Thresholds on the design variables.**
 - **A property to verify.**




Switched Capacitor

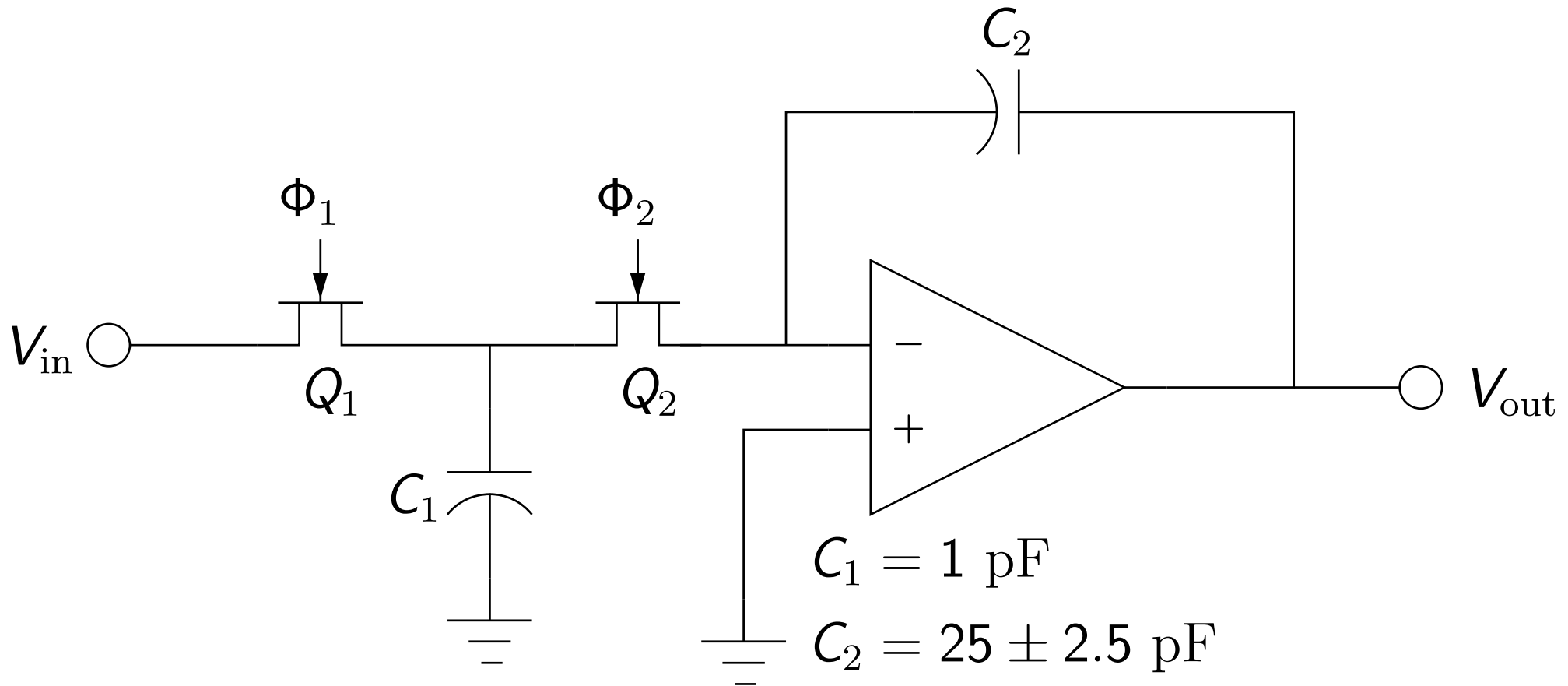

$$V_{\text{in}} = \pm 1000 \text{ mV}$$
$$\text{freq}(V_{\text{in}}) = 5 \text{ kHz}$$


$$\text{freq}(\Phi_1) = \text{freq}(\Phi_2) = 500 \text{ kHz}$$
$$dV_{\text{out}}/dt = \pm(18 \text{ to } 22) \text{ mV}/\mu\text{s}$$

Simulation Trace

 


Data Binning

 
- **Each data point is assigned a bin based upon thresholds.**
- **Each bin represents an operating region of the system.**




Data Binning

 


Data Binning

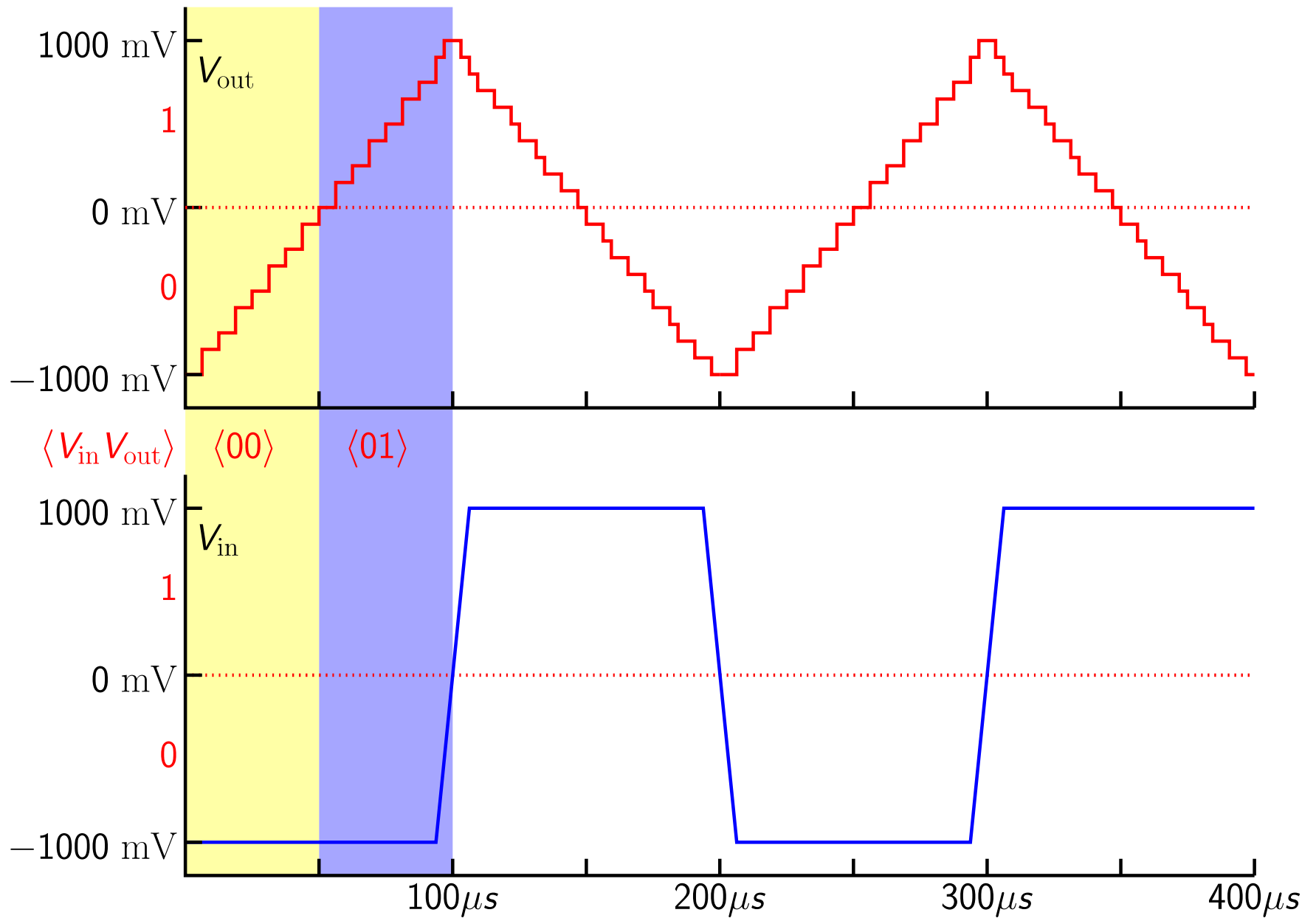

Data Binning

 


Data Binning

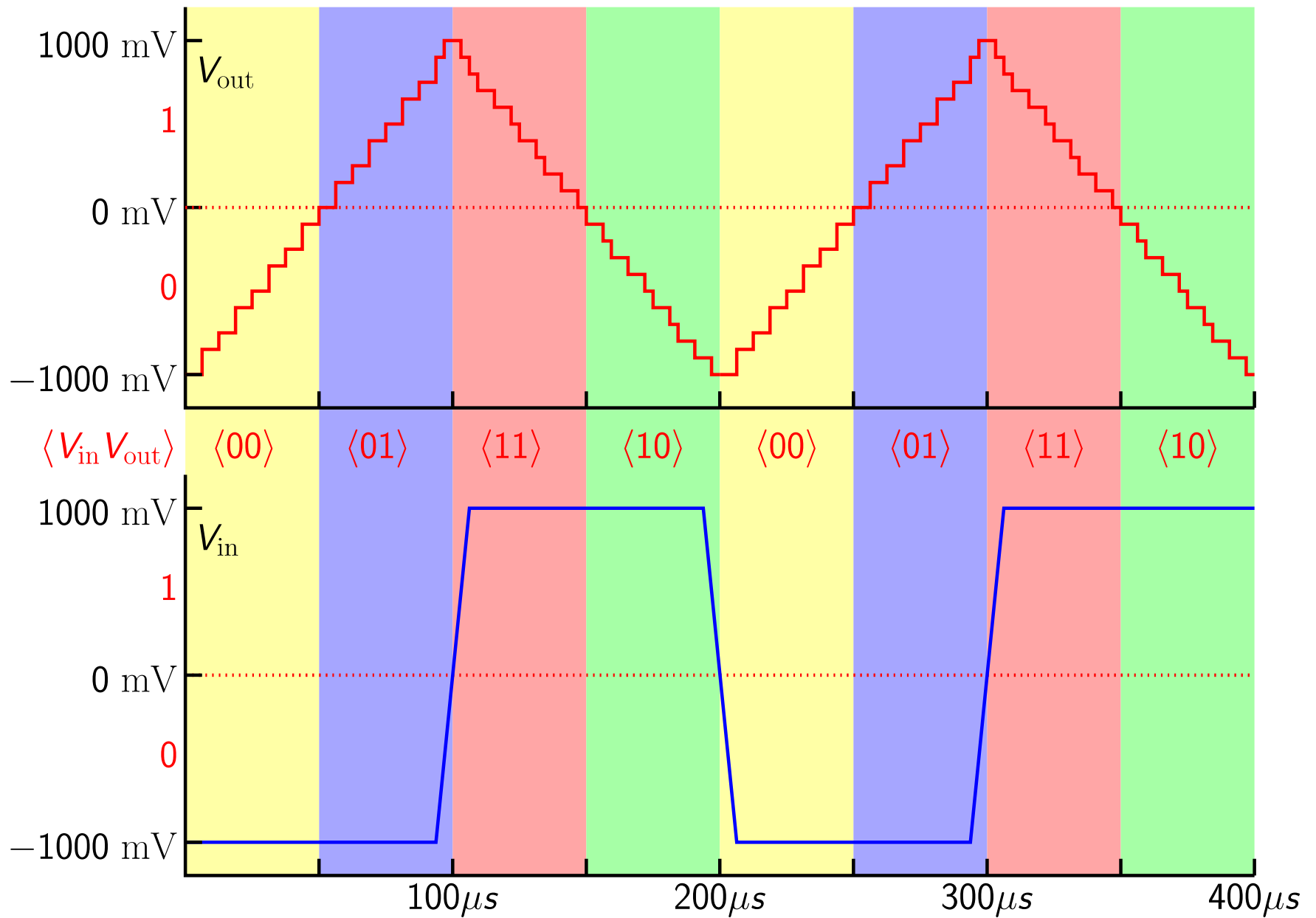


Rate Calculation

 - Rates are calculated for each eligible data point in each bin.
- Low pass filtering smooths edge effects and transitory pulses.
- Minimum and maximum rates are tabulated for each bin.




Rate Calculation

 

$$(-652 - -1000) / (15.0 - 0.51) = 23.93 \text{ mV}/\mu s$$

$$V'_{out00} = [23, 24]$$


Rate Calculation

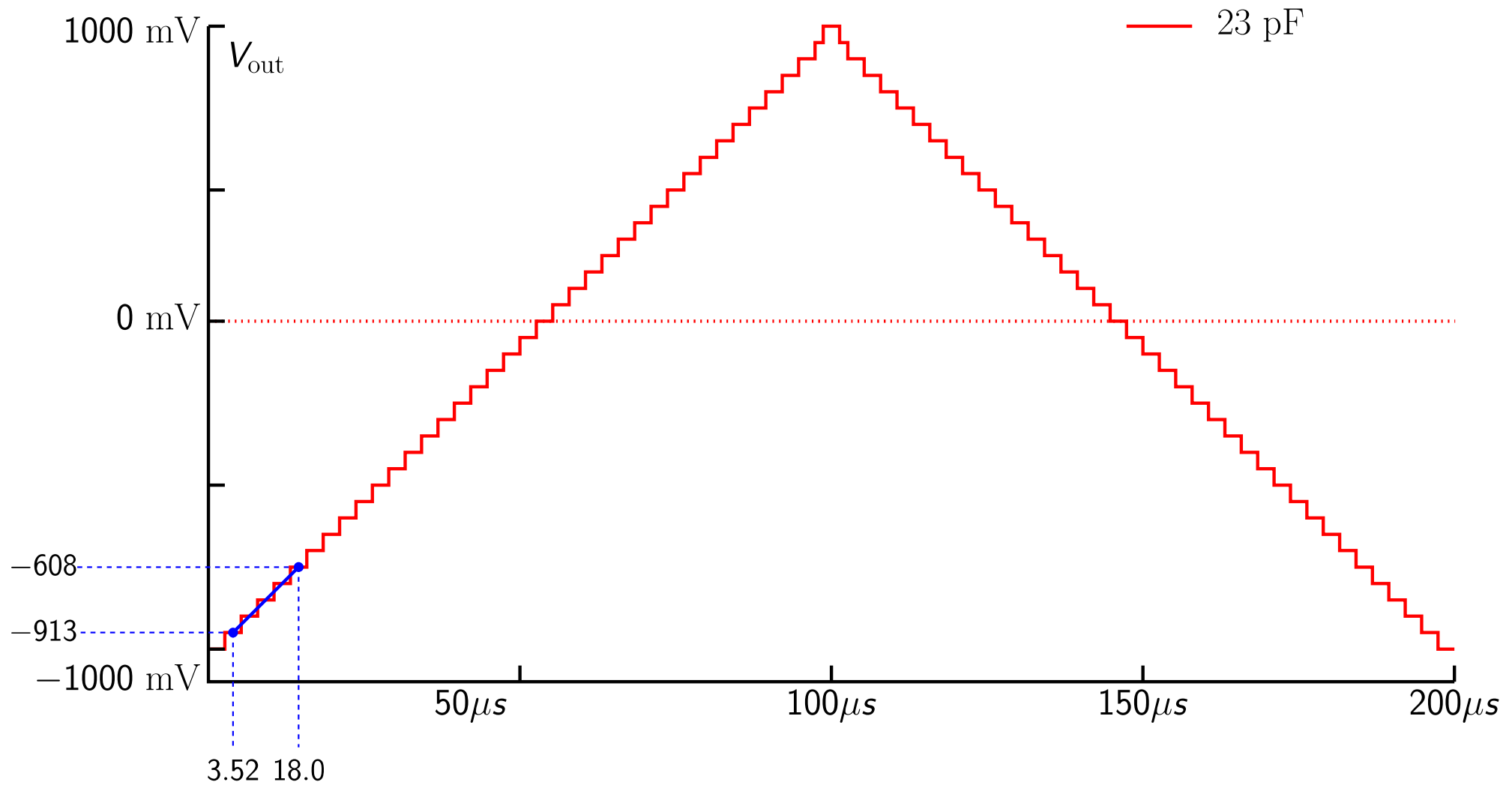

$$(-608 - -913) / (18.0 - 3.52) = 21.06 \text{ mV} / \mu s$$

$$V'_{out00} = [21, 24]$$


Rate Calculation

 

No rate calculated.

$V'_{out00} = [19, 24]$

Rate Calculation

 

Final rate calculations after $C_2=27$ pF.


$V'_{out00}=[17,24]$

DMV Variables

- **Stable signals are handled differently to aid efficiency.**
- **Stability is determined by:**
 - **Remaining constant within an epsilon value for a specified time.**
 - **Total percent of the entire signal marked stable.**
- **Delay is calculated for each constant value.**
- **Min/max delay and constant values are extracted.**

Generating an LPN

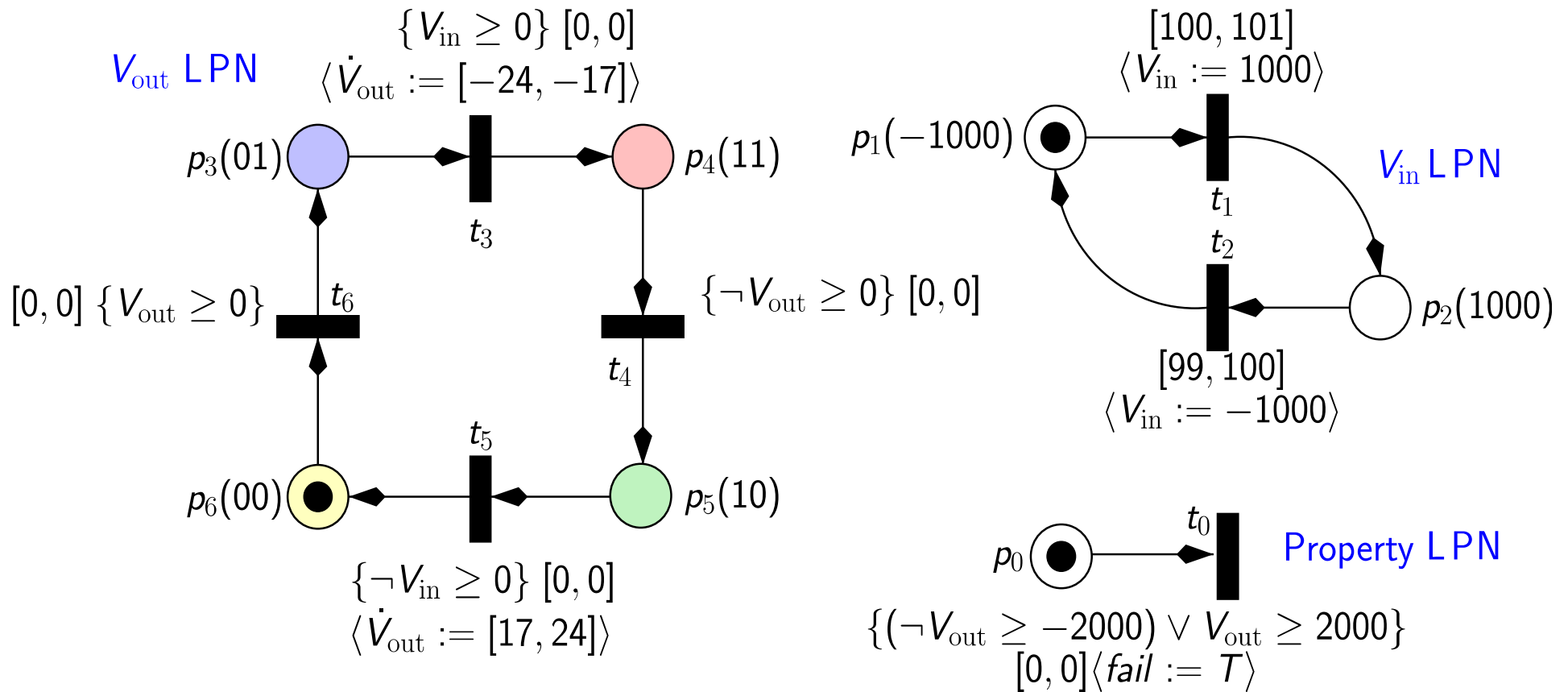Initial values = $\{V_{out} = -1000\text{ mV}, V_{in} = -1000\text{ mV}, fail = F\}$; Initial rates = $\{V'_{in} = 0, V'_{out0} = [17, 24]\}$





Property Language

- **delay(d)** - wait for d time units.
- **wait(b)** - wait until boolean expression, b, becomes true.
- **waitPosedge(b)** - wait for a positive edge on b.
- **wait(b, d)** - wait at most d time units for b to become true.
- **assert(b, d)** - ensure that b remains true for d time units.
- **assertUntil(b1, b2)** - ensure that b1 remains true until b2 is true.
- **if-else** - statement for selections.
- **always(conditionsList){statements}** - continue to execute statements until one of the signals in the list of variables conditionsList changes, then break out.

LEMA DEMO

C-element Example



Analog | Digital

  

$$R_1 C_1 ? R_2 C_2$$



C-element Example

Analog | Digital

 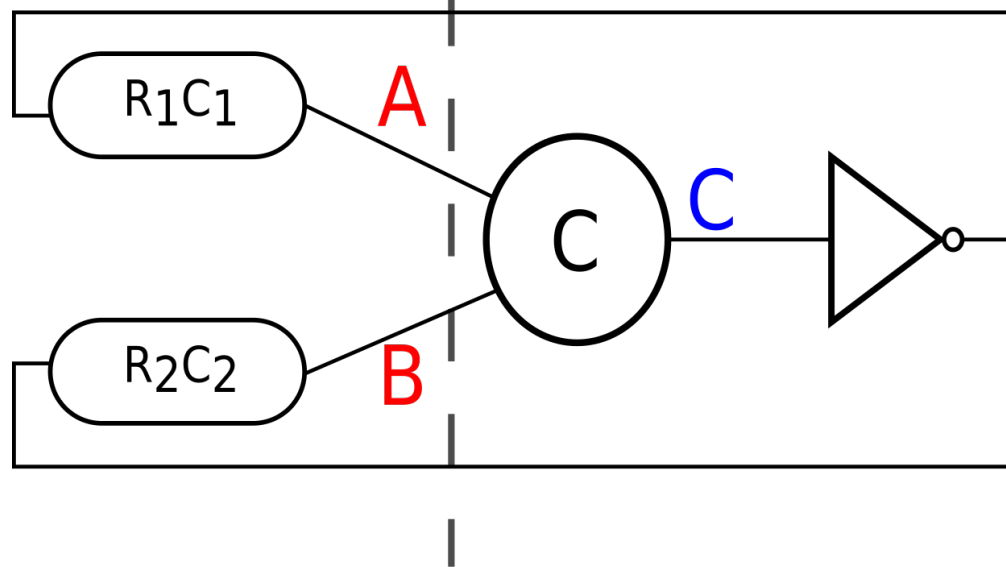

$$R_1 C_1 < R_2 C_2$$



C-element Example

 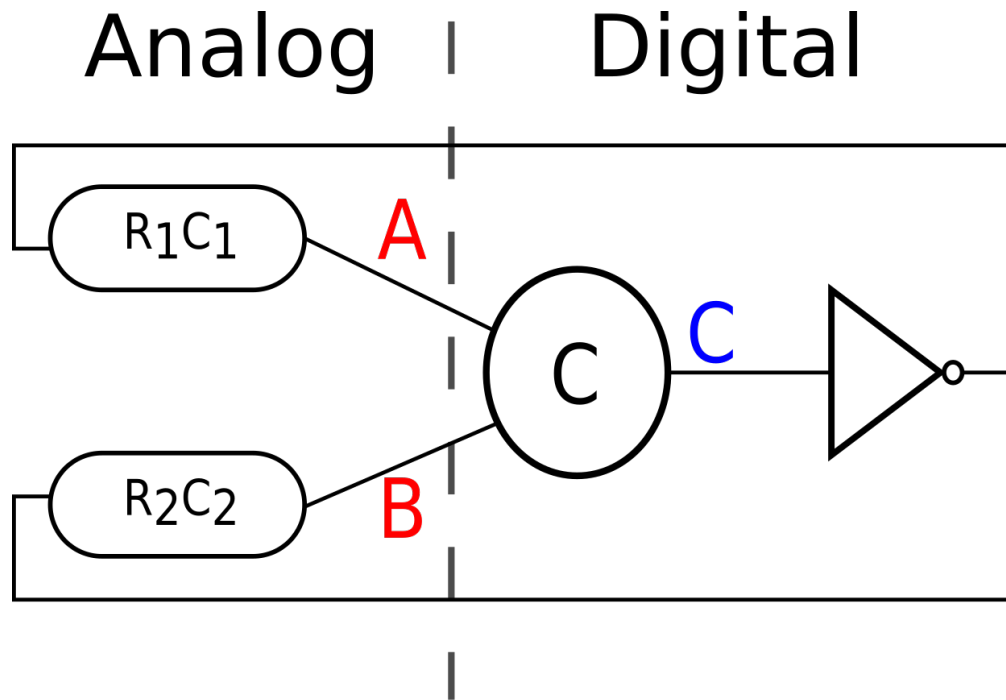

$$R_1 C_1 < R_2 C_2$$


C-element Example

Analog | Digital

 
 


$$R_1 C_1 < R_2 C_2$$



AMS verification workflow

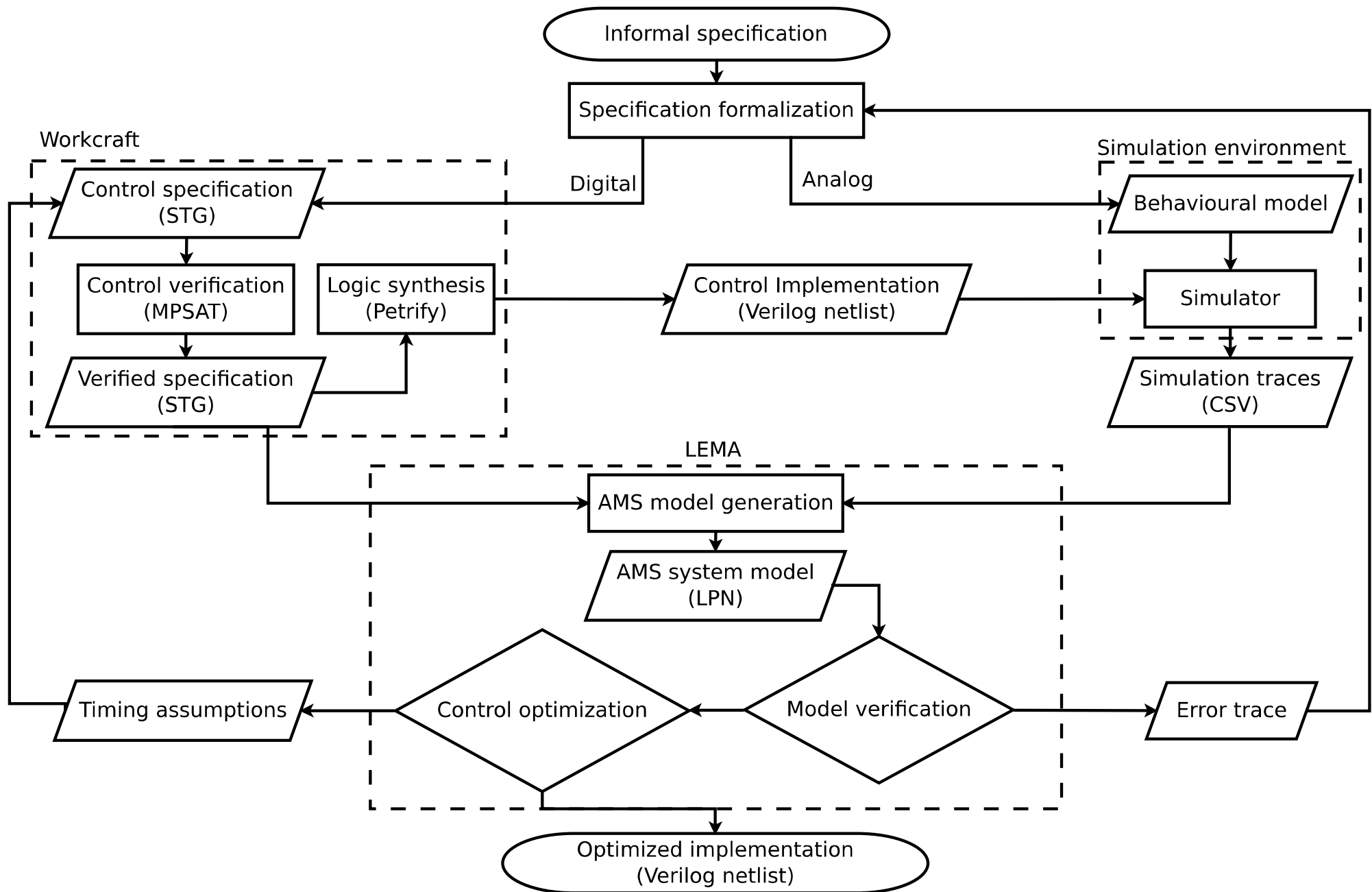

Buck converter

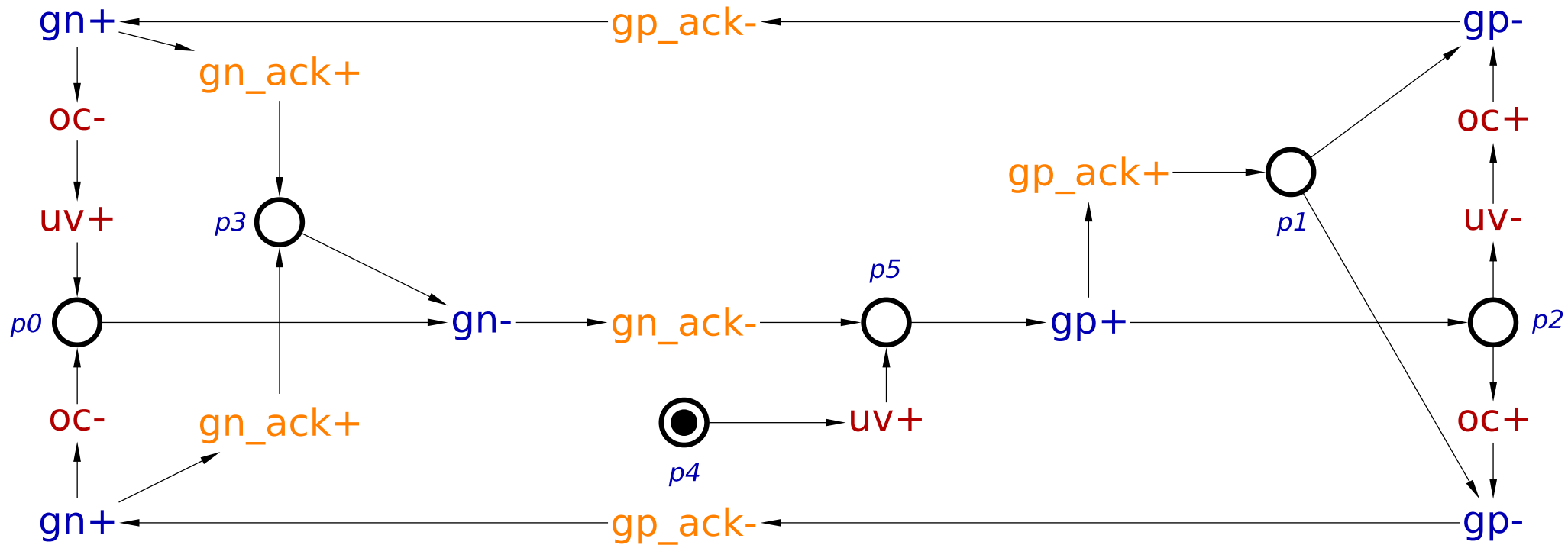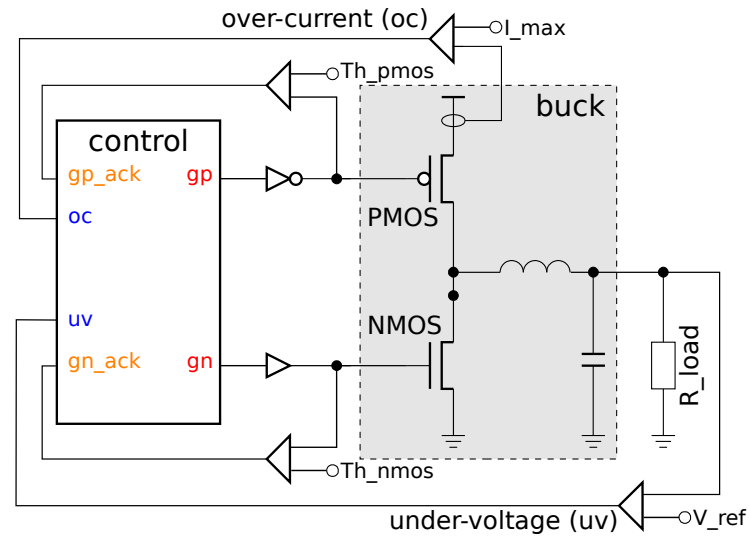


Model generation example

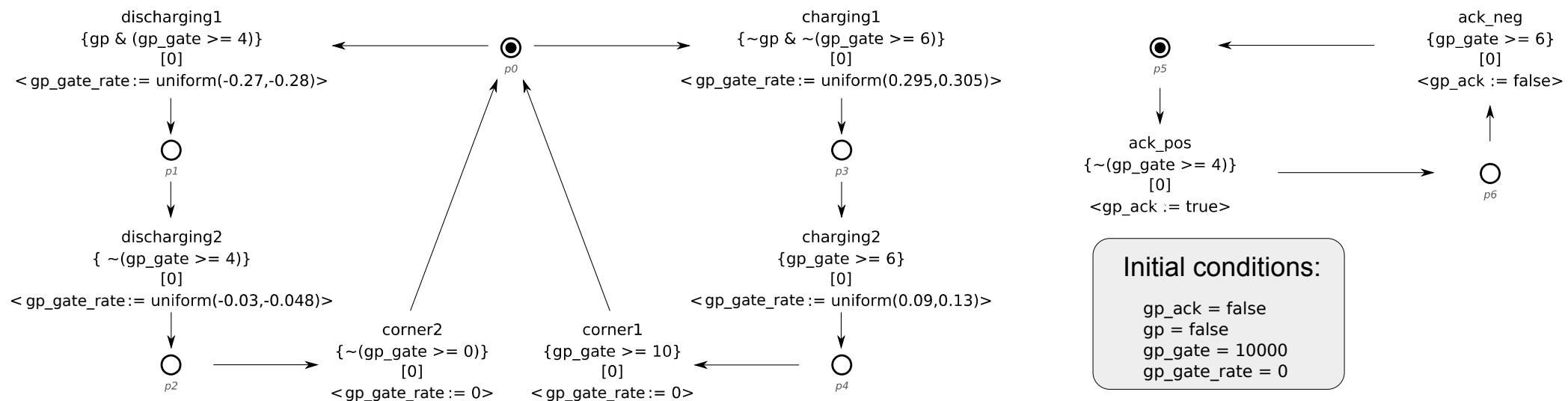 


Optimized specification

• Concurrency reduction

 

• Scenario elimination

 

Verification challenges

- **Modules partitioning** – trade-off between model's accuracy and verification speed
- **False positives** – dealing with verification false fail states due to overapproximation
- **Properties expression** – models properties expressed via non-standard language