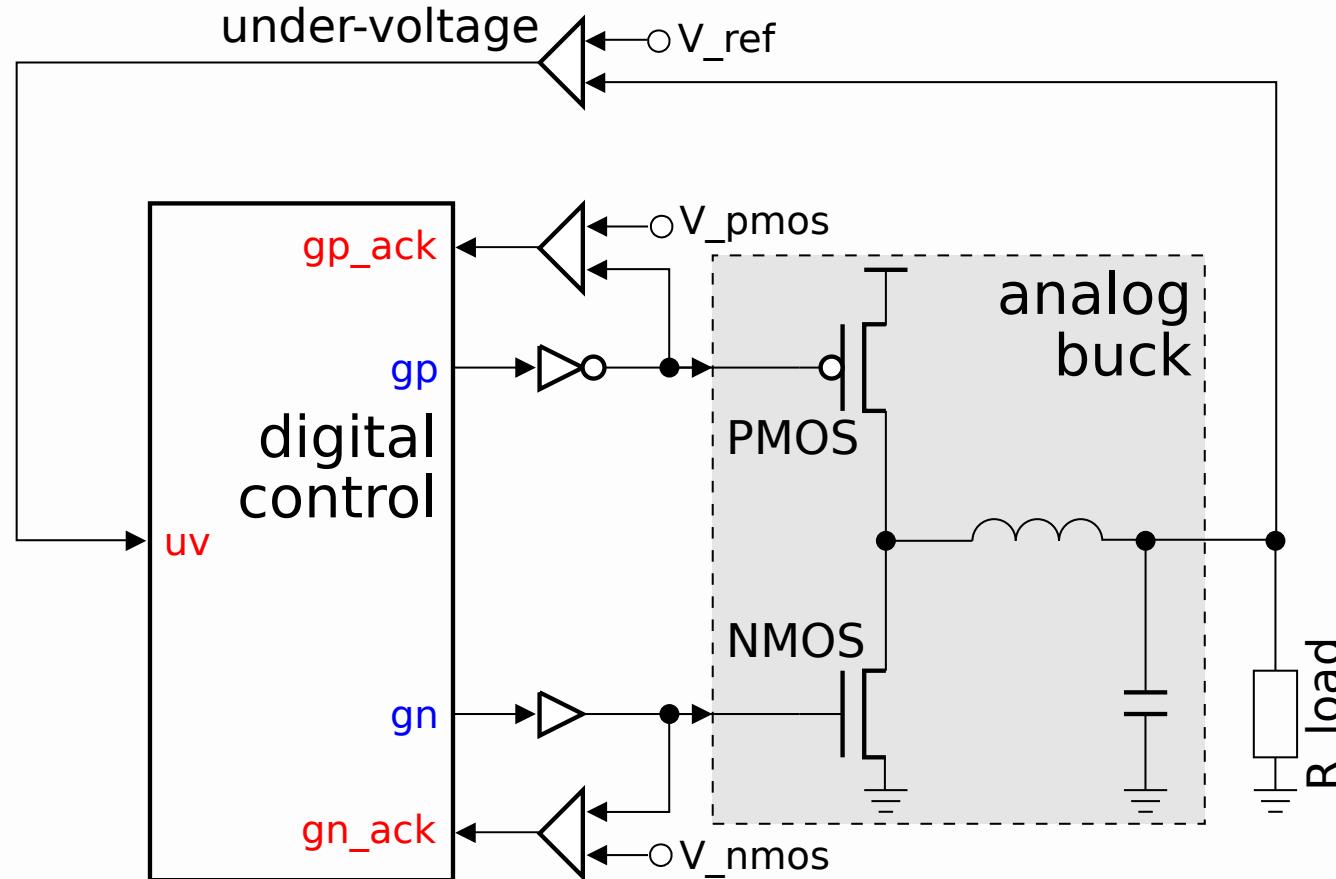


# Analog-to-asynchronous (A2A) interfaces


Danil Sokolov, Victor Khomenko, Alex Yakovlev

*Newcastle University, UK*

# Motivating example: toy buck converter




# Motivating example: toy buck converter

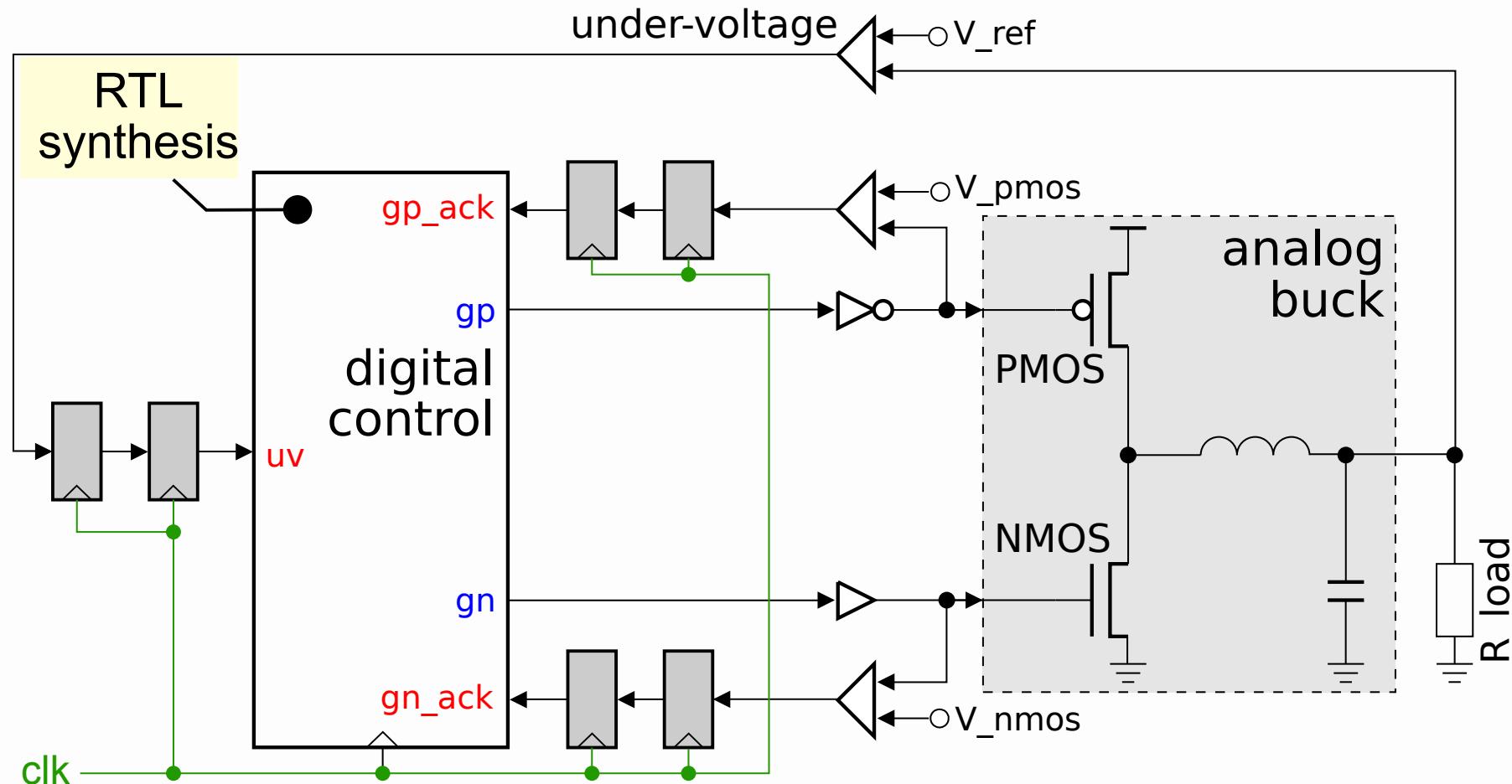

- Synchronous implementation – requires synchronisers for asynchronous inputs
  - Synchronisers also sanitize hazardous / dirty inputs from analog environment
  - Reaction time – 3 clock cycles

# Motivating example: toy buck converter


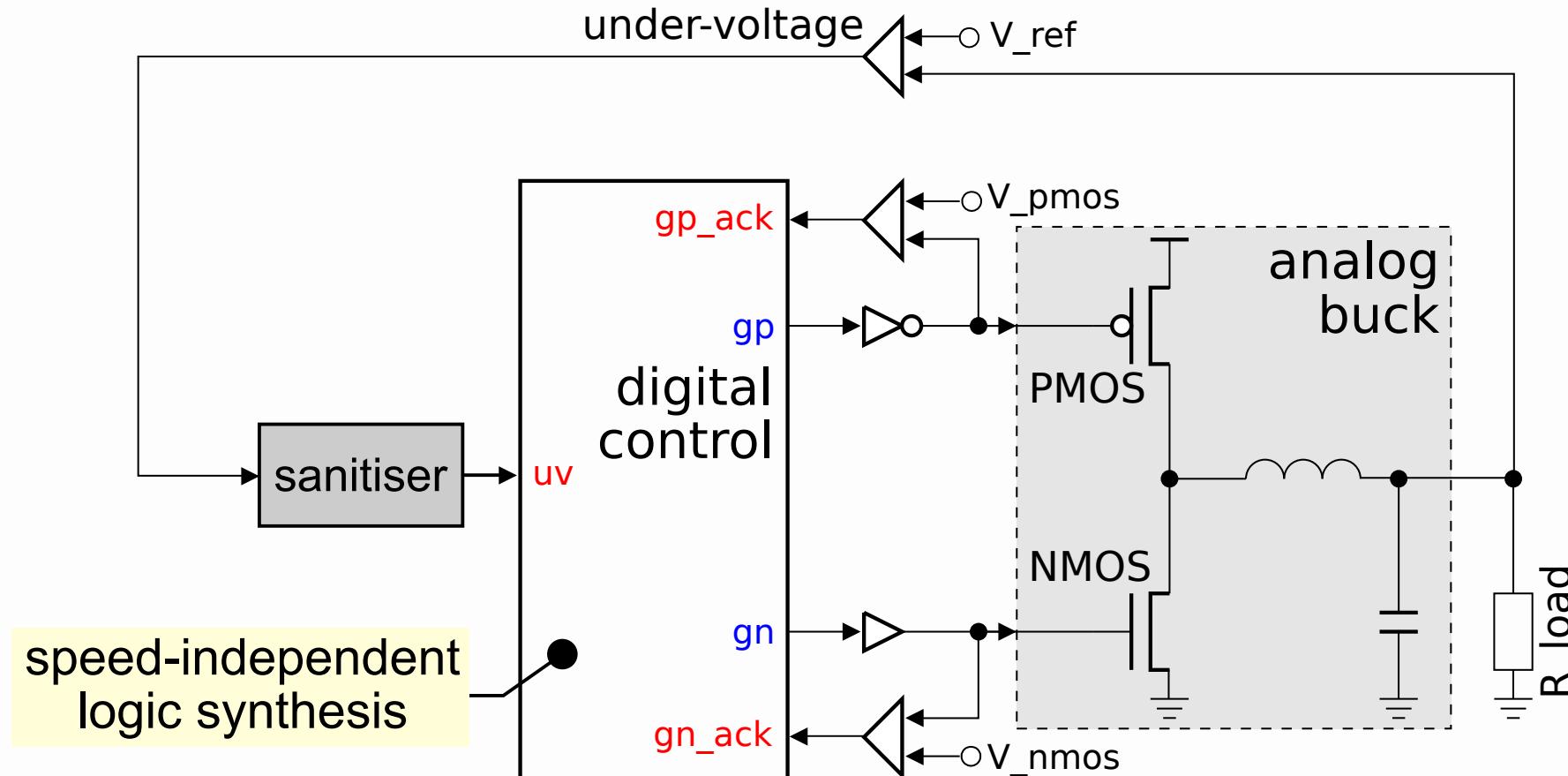


- Asynchronous implementation – natural for asynchronous inputs
  - Reaction time – several gate delays
  - Need to sanitise hazardous under-voltage input


# Asynchronous arbitration primitives

- Synchronisation
  - WAIT: synchronise with high level of hazardous input
  - RWAIT: WAIT that can be released/cancellation
  - WAIT01: synchronise with hazardous rising edge
  - WAIT2: synchronise with both phases of a hazardous input
- Decision-making
  - WAITX: arbitrate between two hazardous inputs
  - SAMPLE: sample a hazardous input

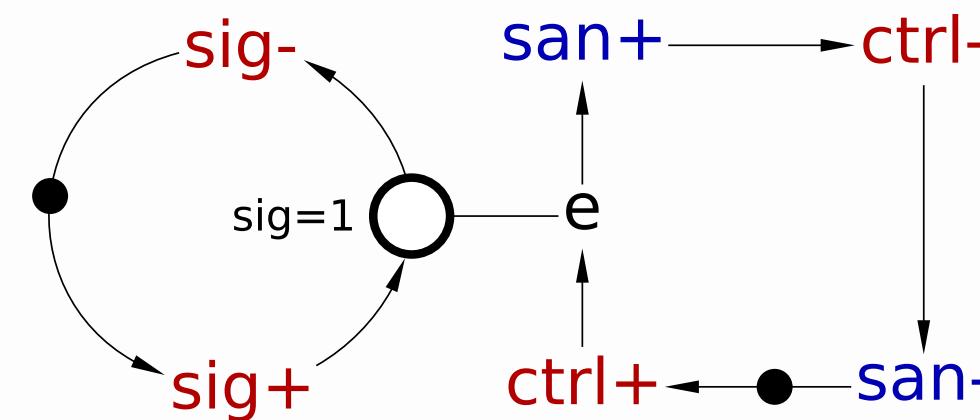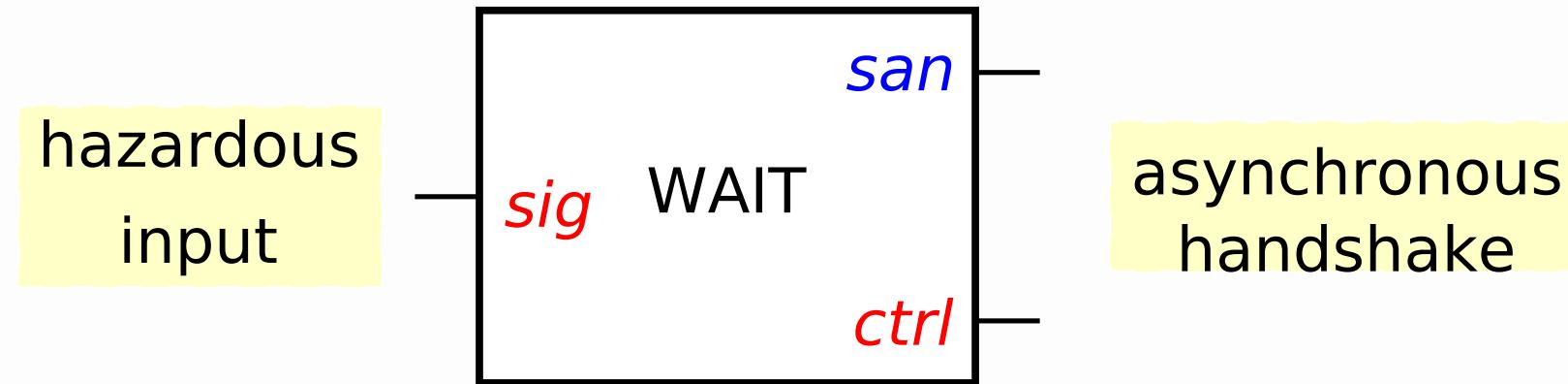
# WAIT: synchronise handshake with high level of hazardous input



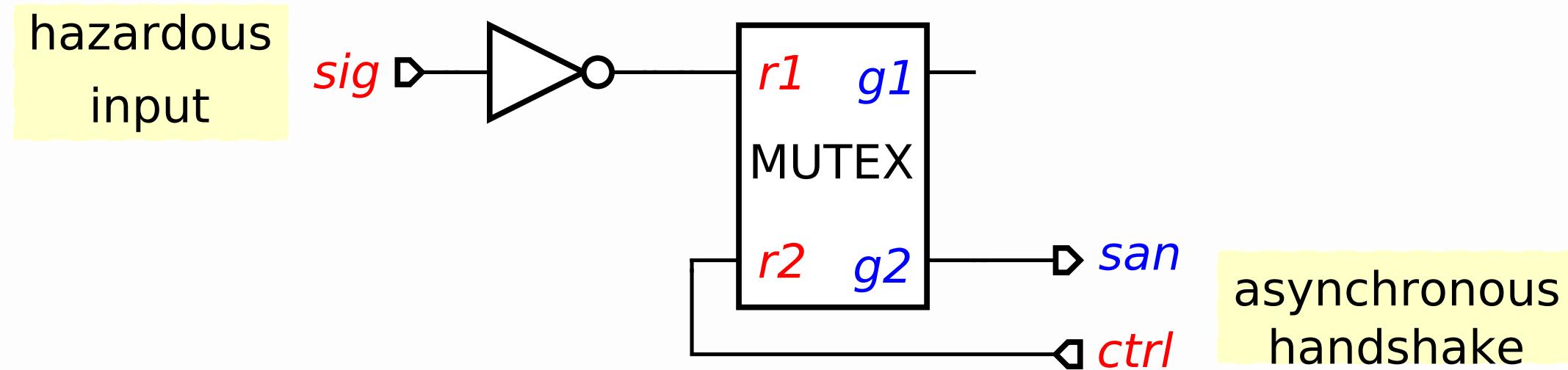
# WAIT: synchronise handshake with high level of hazardous input


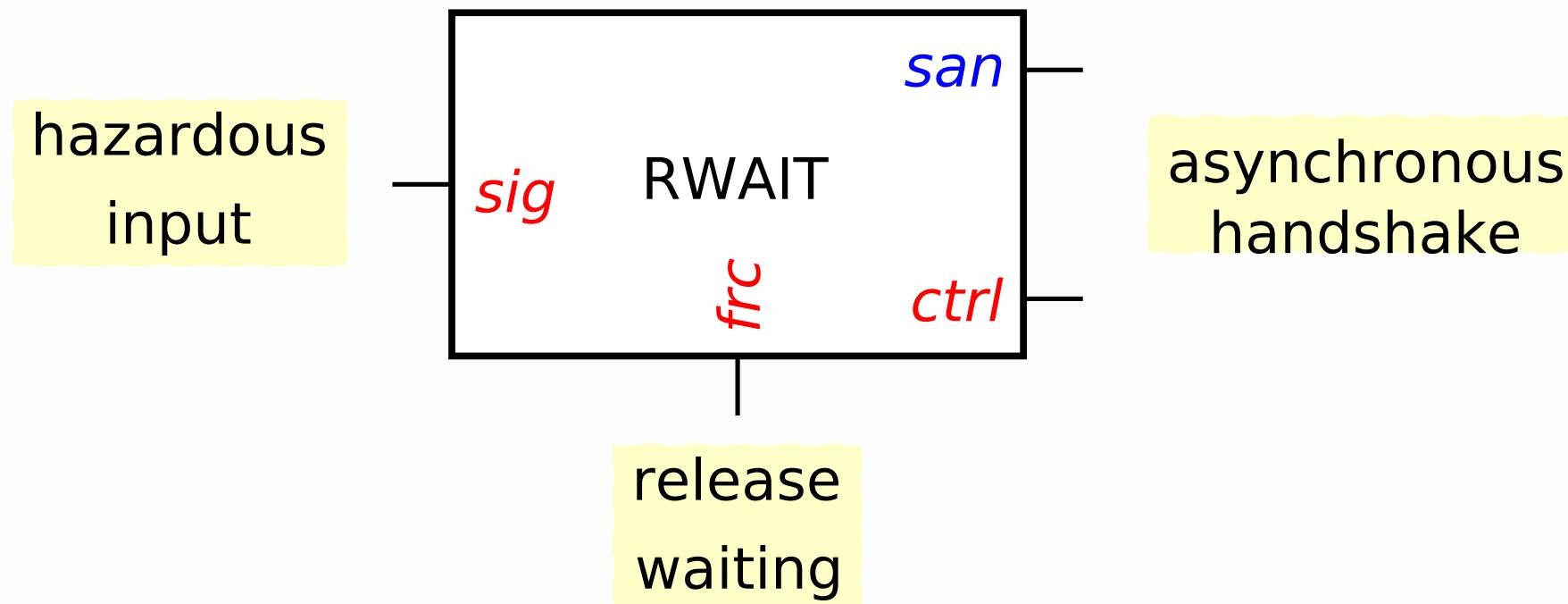
# RWAIT: WAIT that can be released/cancelled



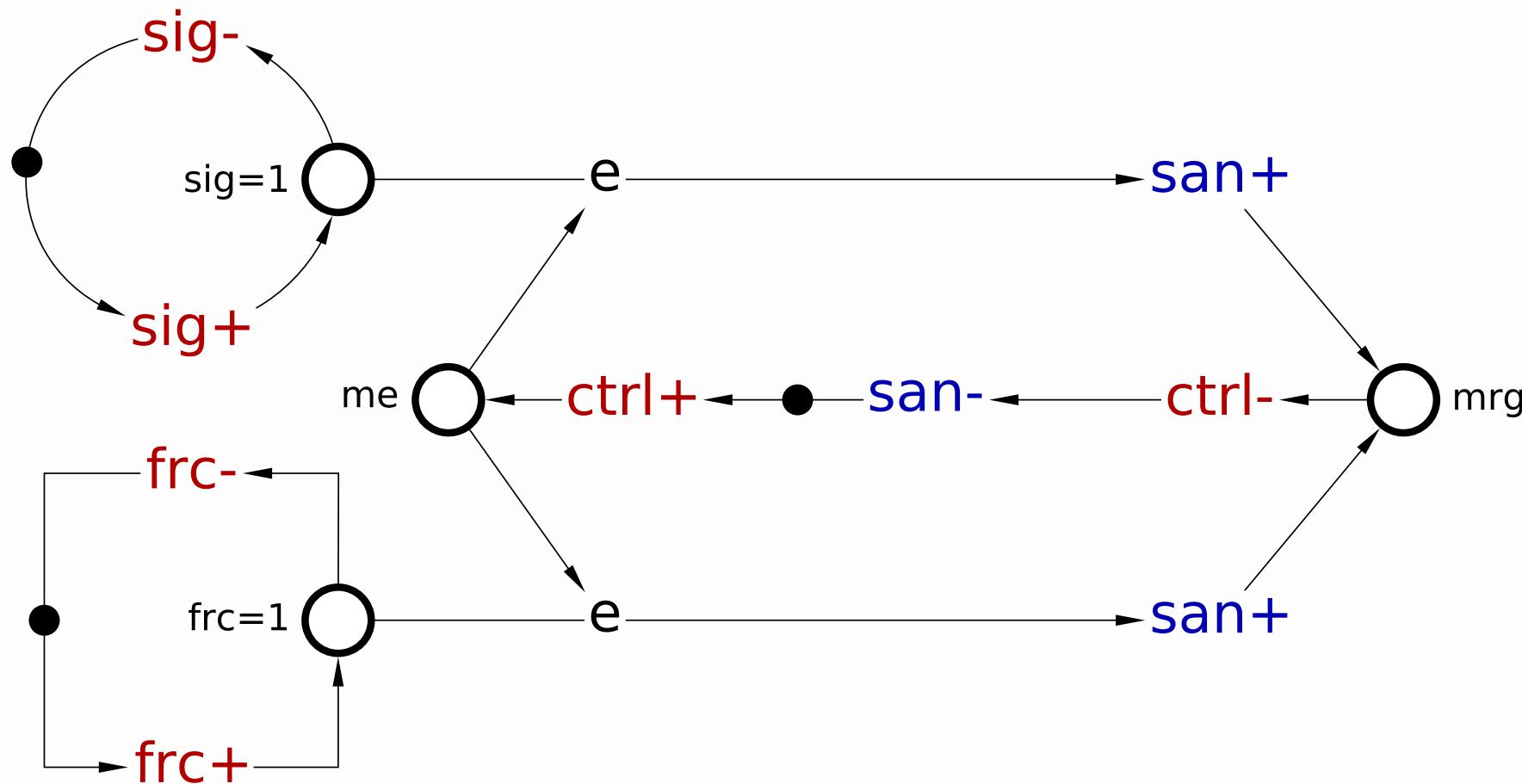
# RWAIT: WAIT that can be released/cancelled




frc and san form a handshake


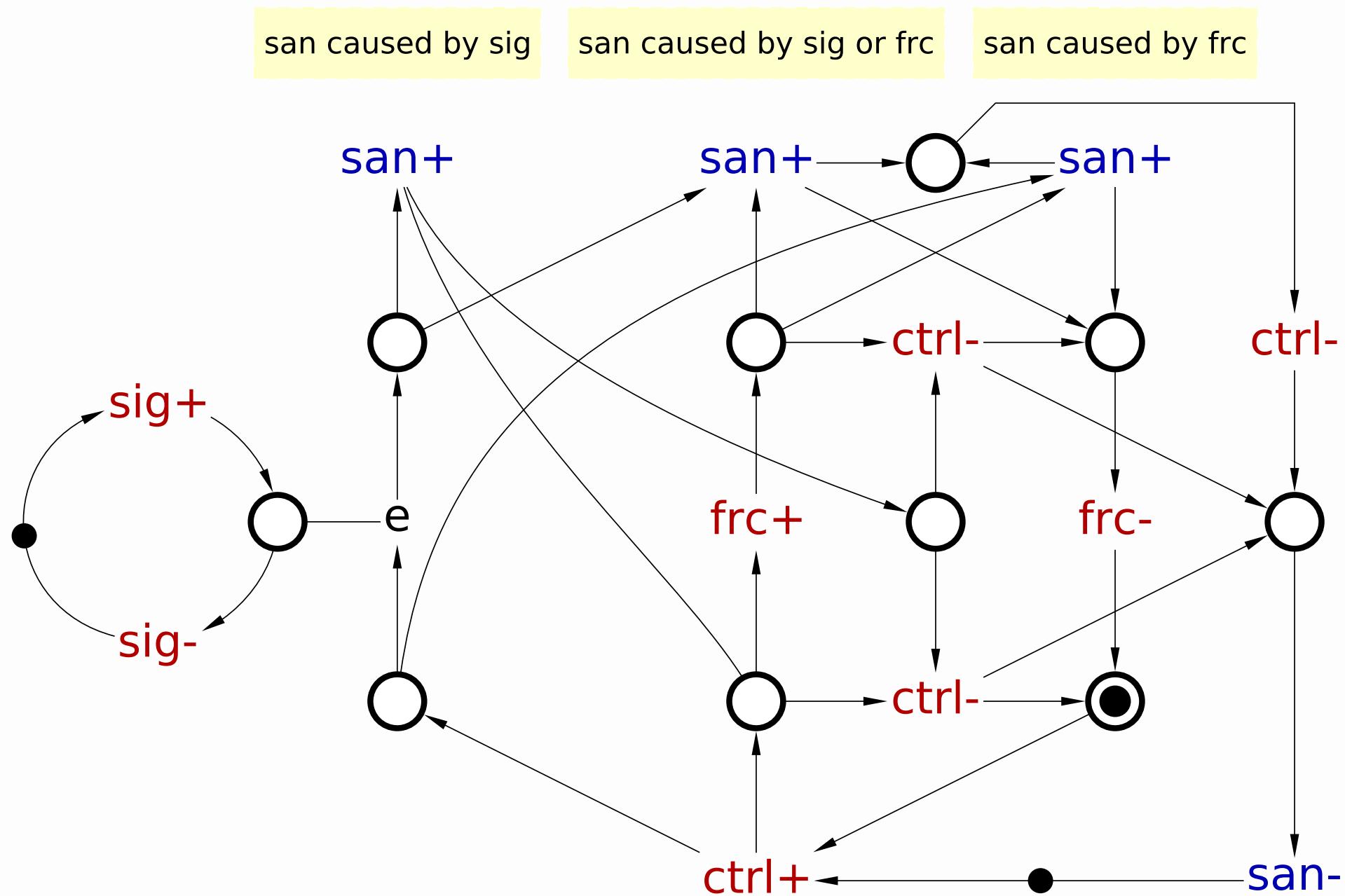
## RWAIT: WAIT that can be released/cancelled



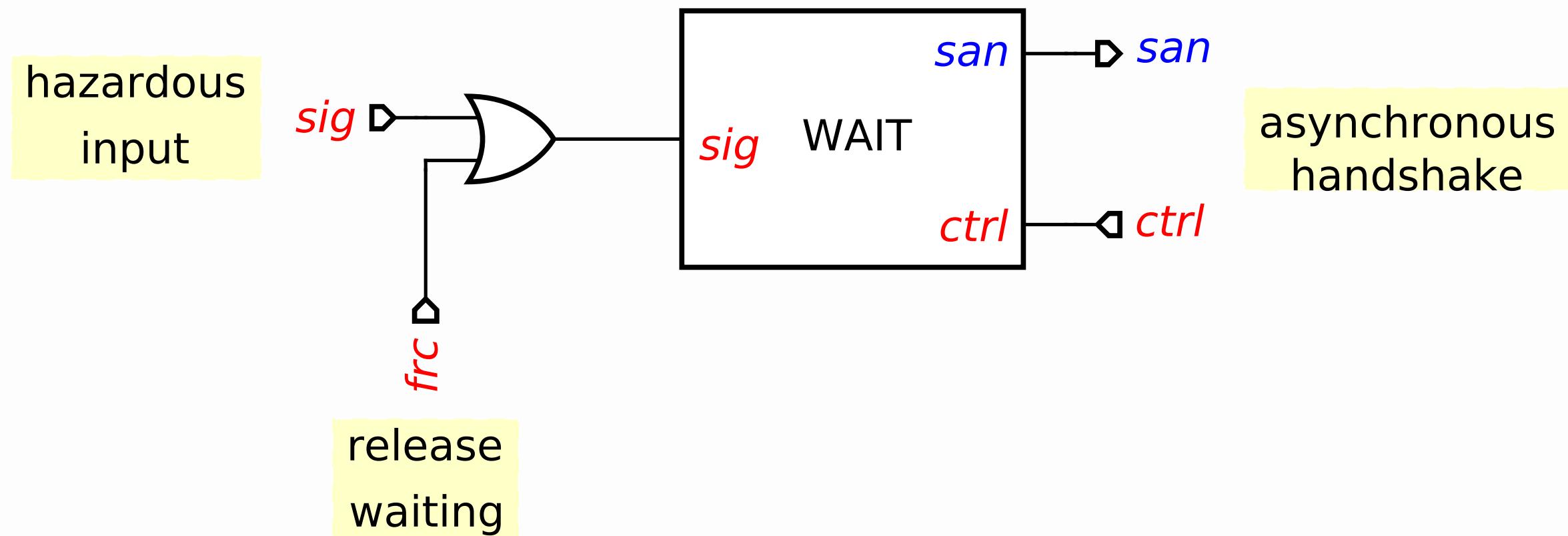
# RWAIT: WAIT that can be released/cancelled



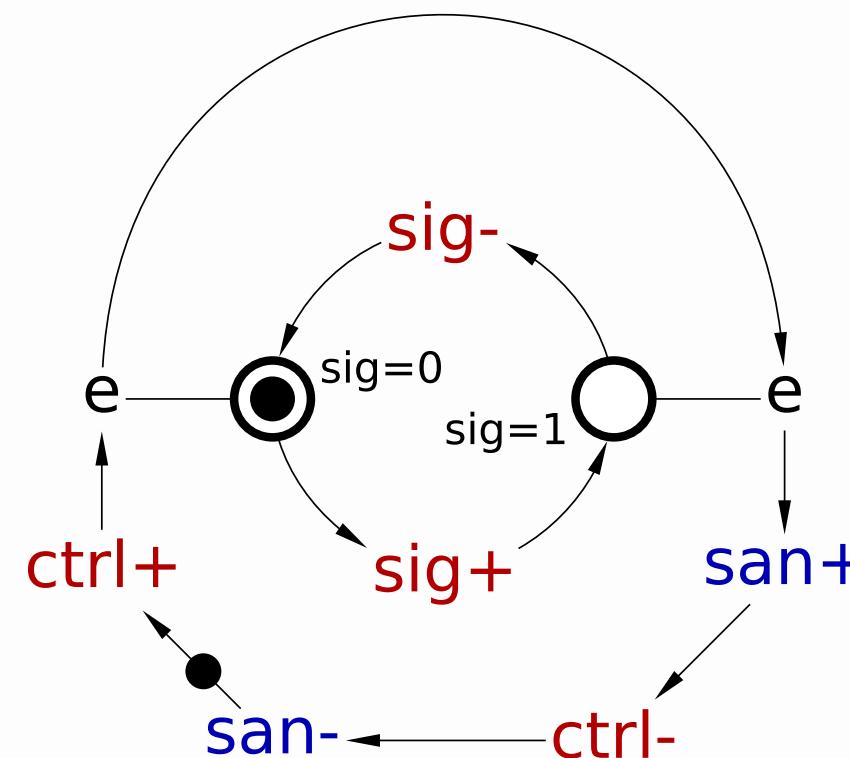
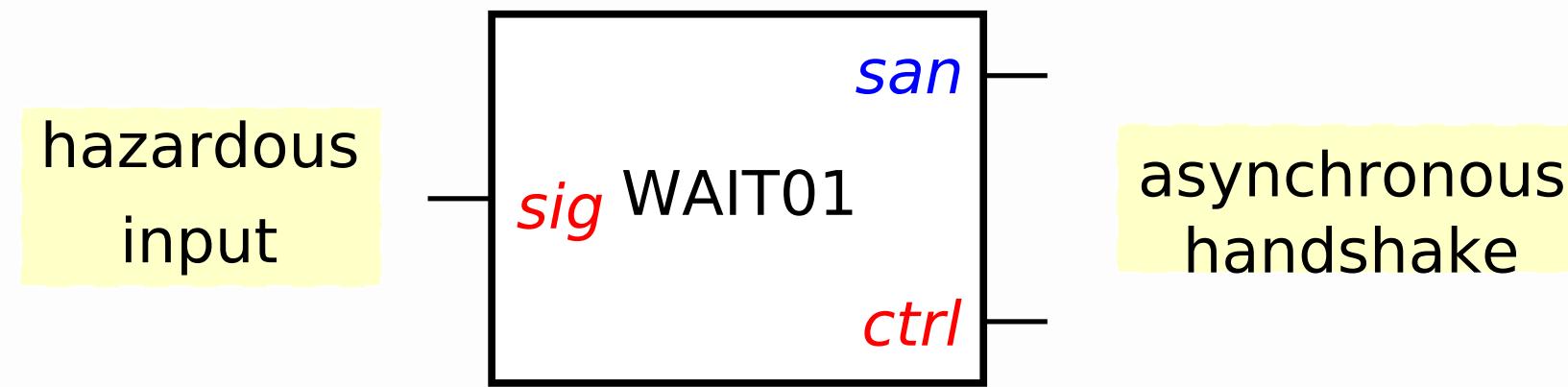
# WAIT01: synchronise handshake with rising edge of hazardous input



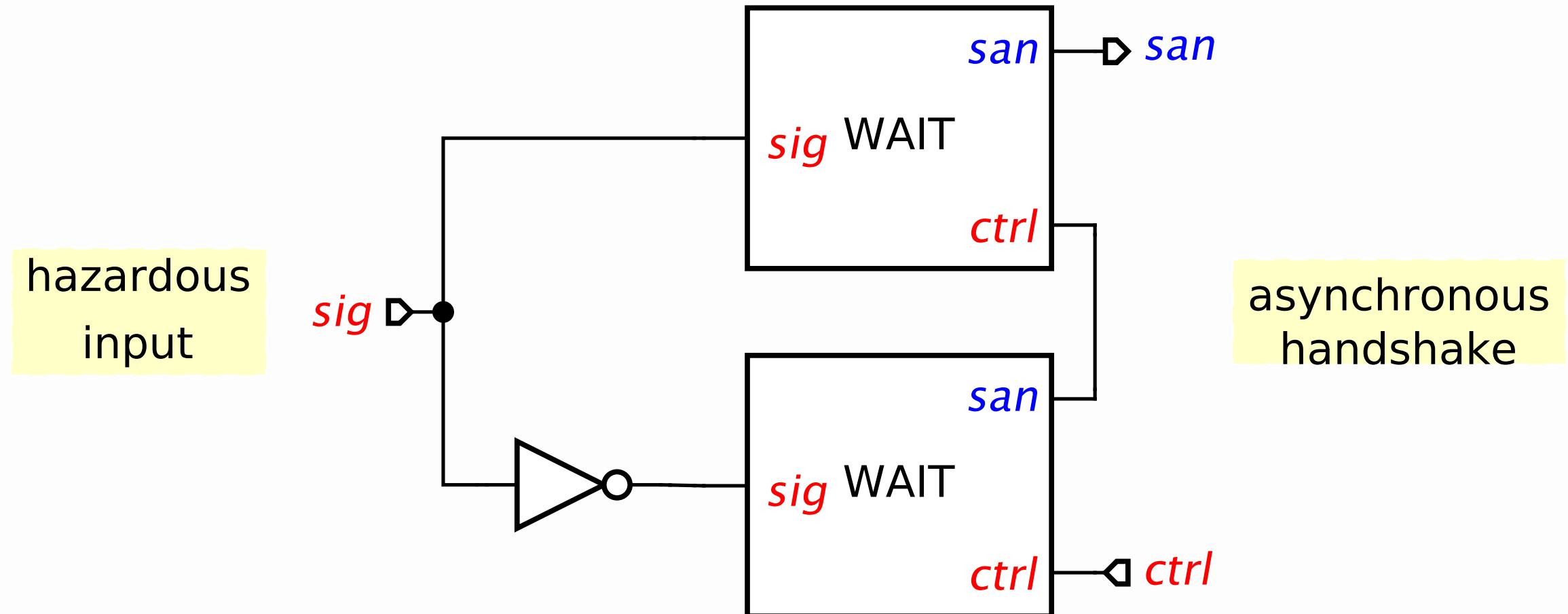
# WAIT01: synchronise handshake with rising edge of hazardous input



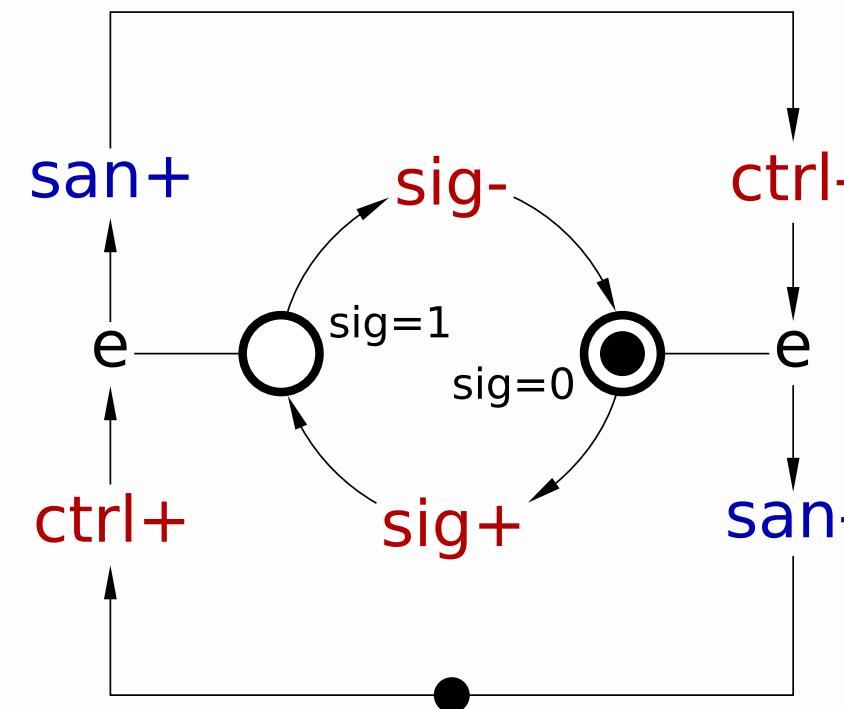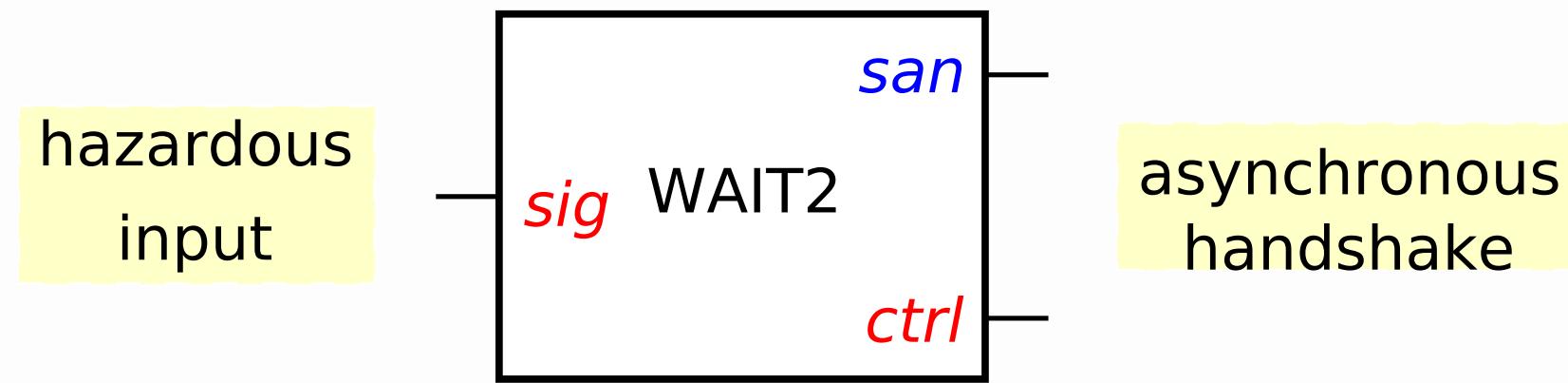
## WAIT2: synchronise handshake with both phases of hazardous input



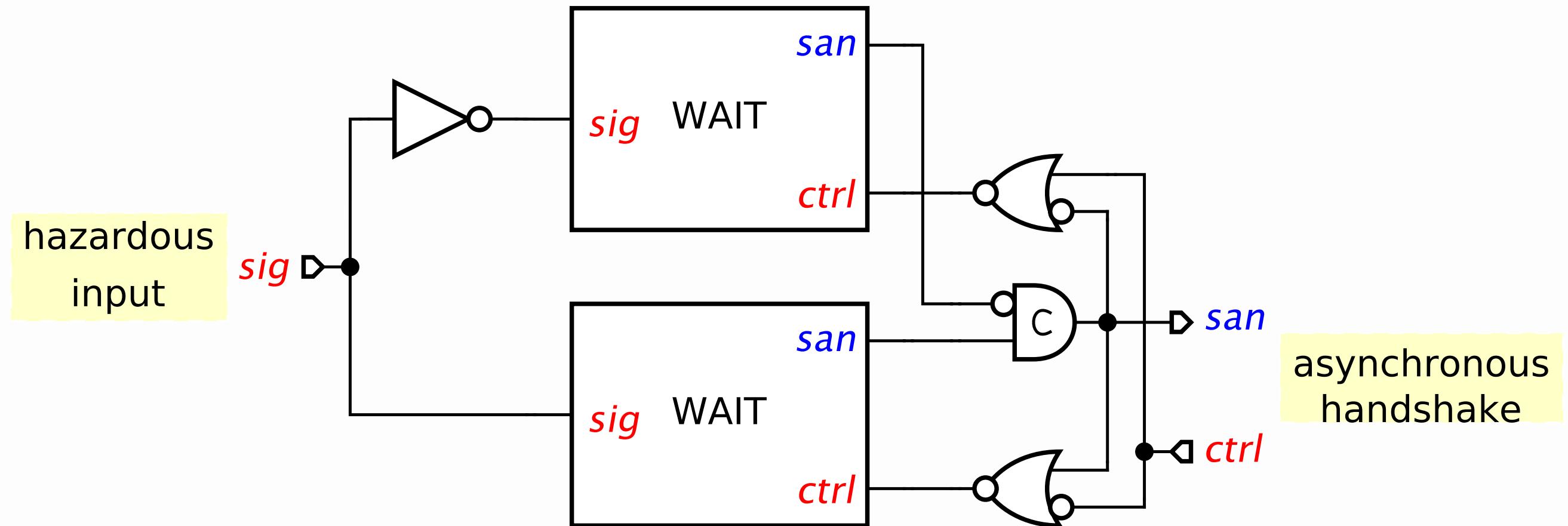
# WAIT2: synchronise handshake with both phases of hazardous input



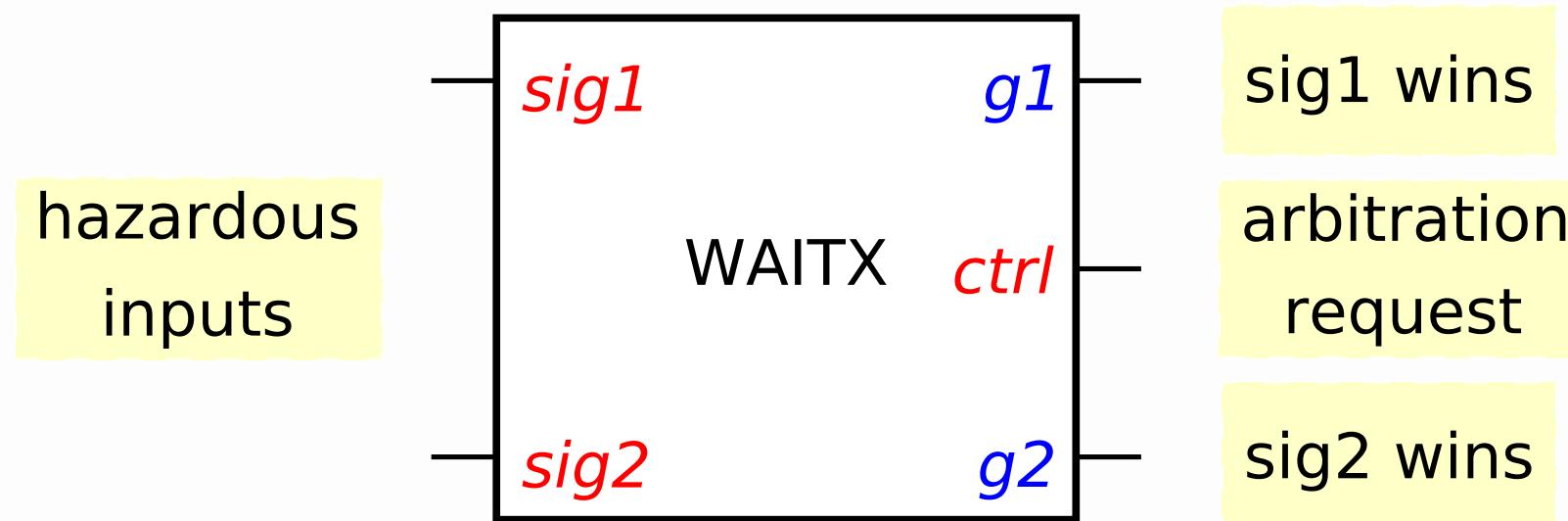
# WAITX: arbitrate between two hazardous inputs



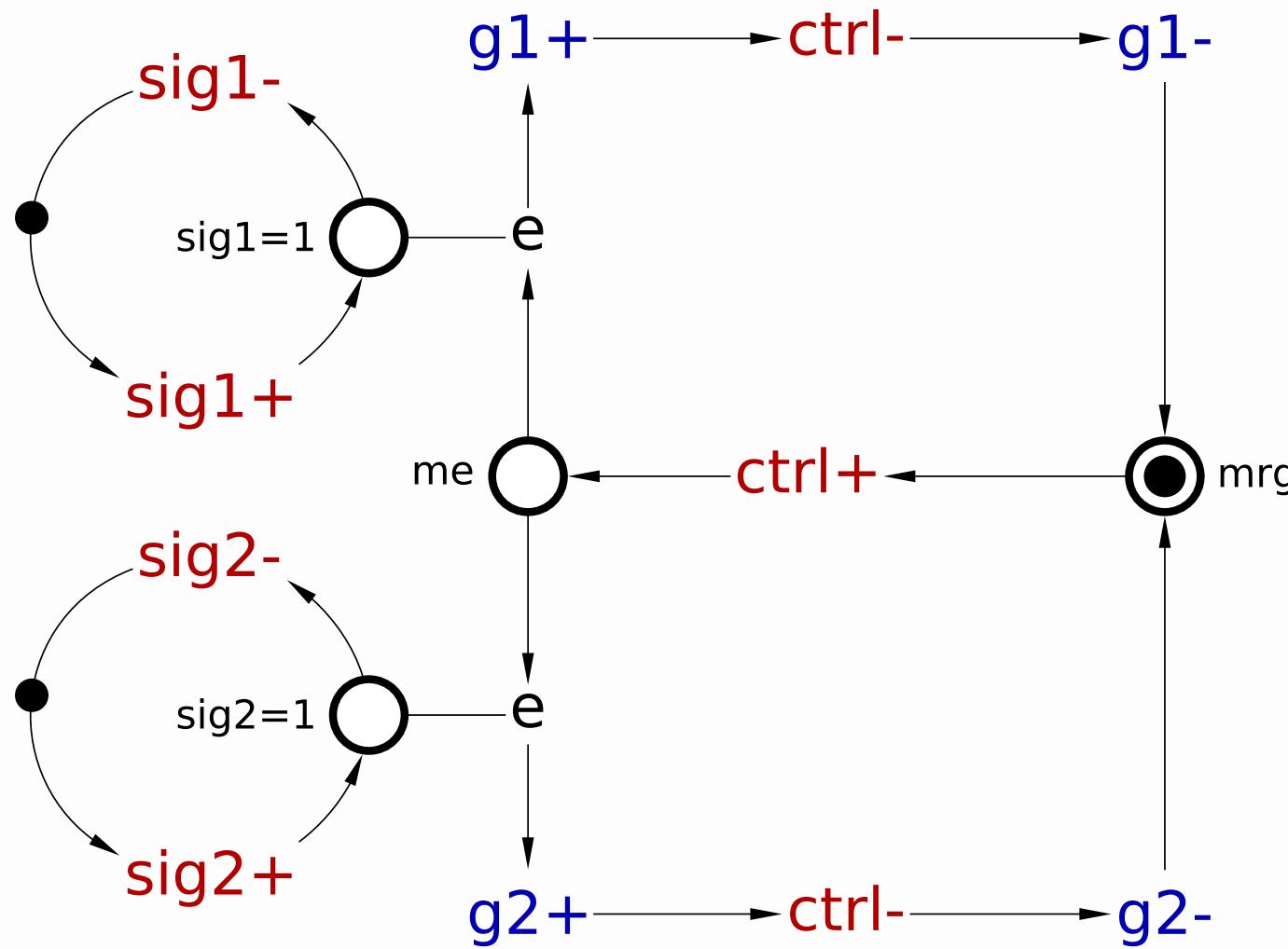
# WAITX: arbitrate between two hazardous inputs



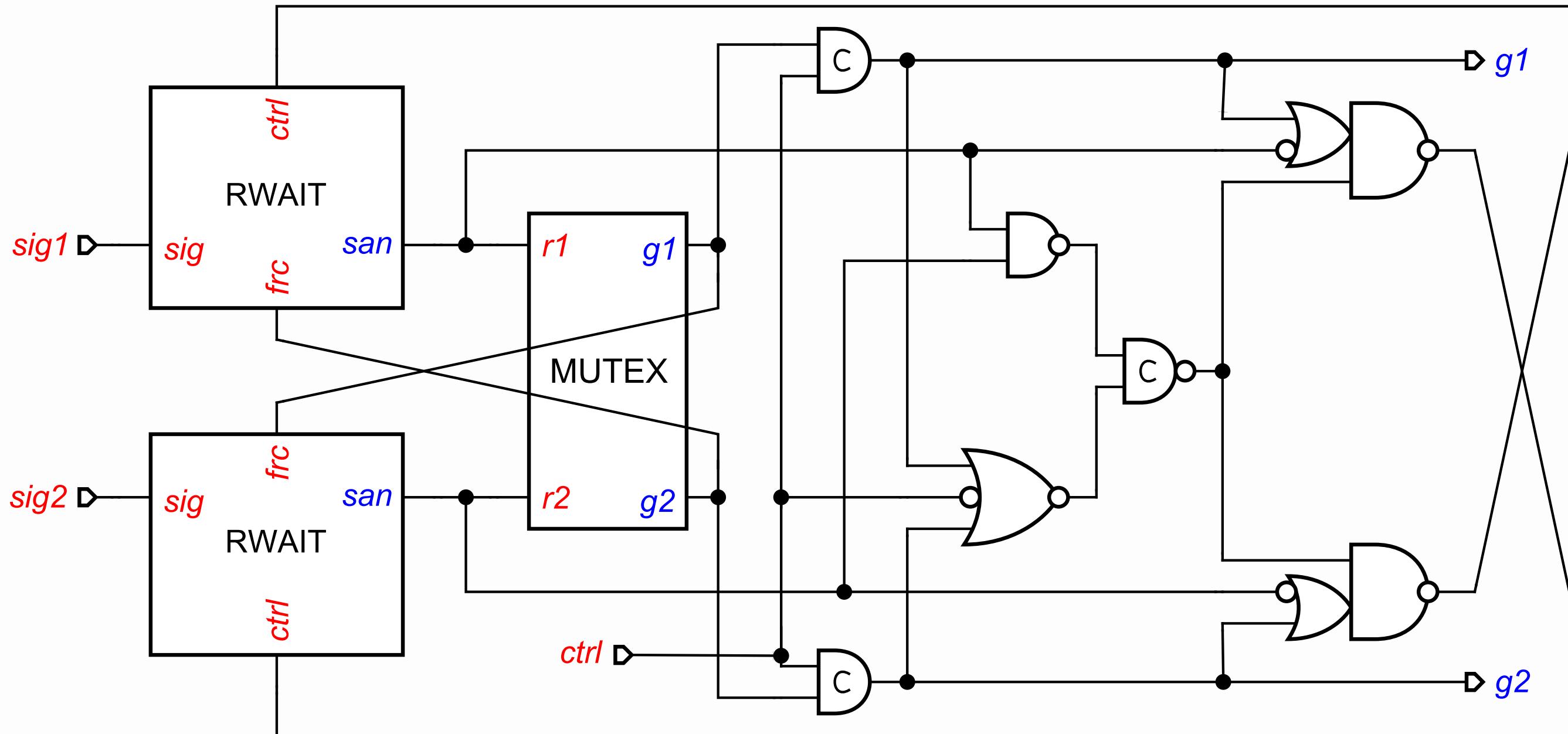
# WAITX: arbitrate between two hazardous inputs




# SAMPLE: sample a hazardous input

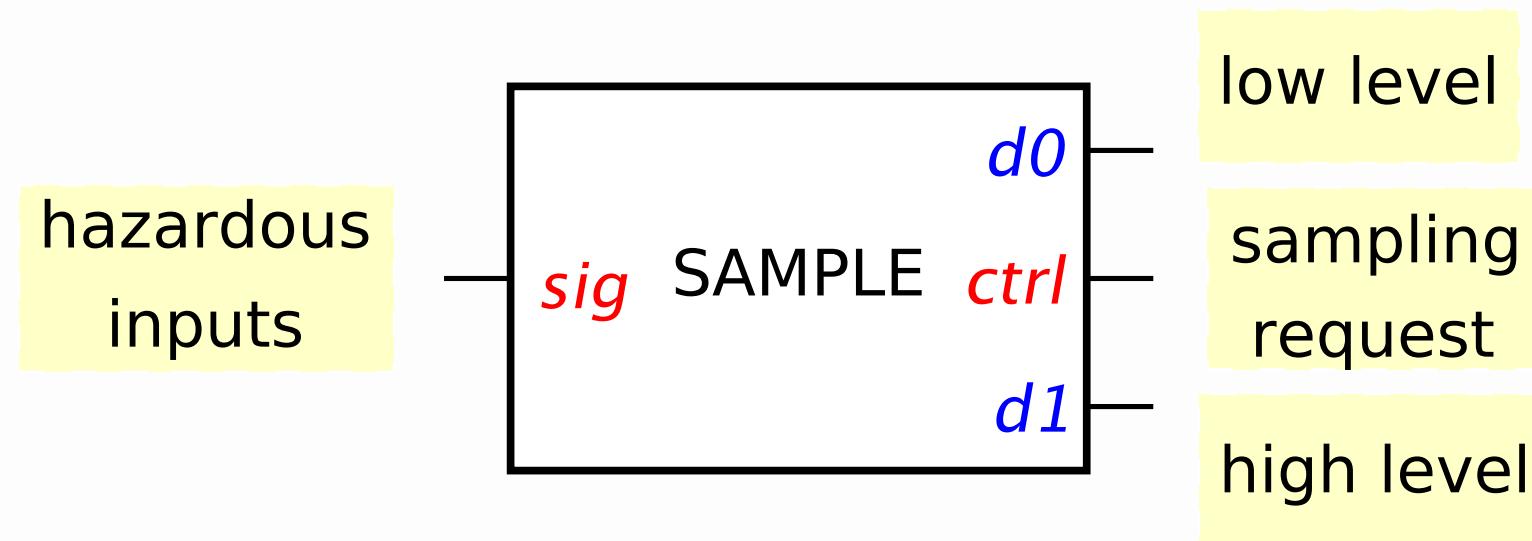


## SAMPLE: sample a hazardous input

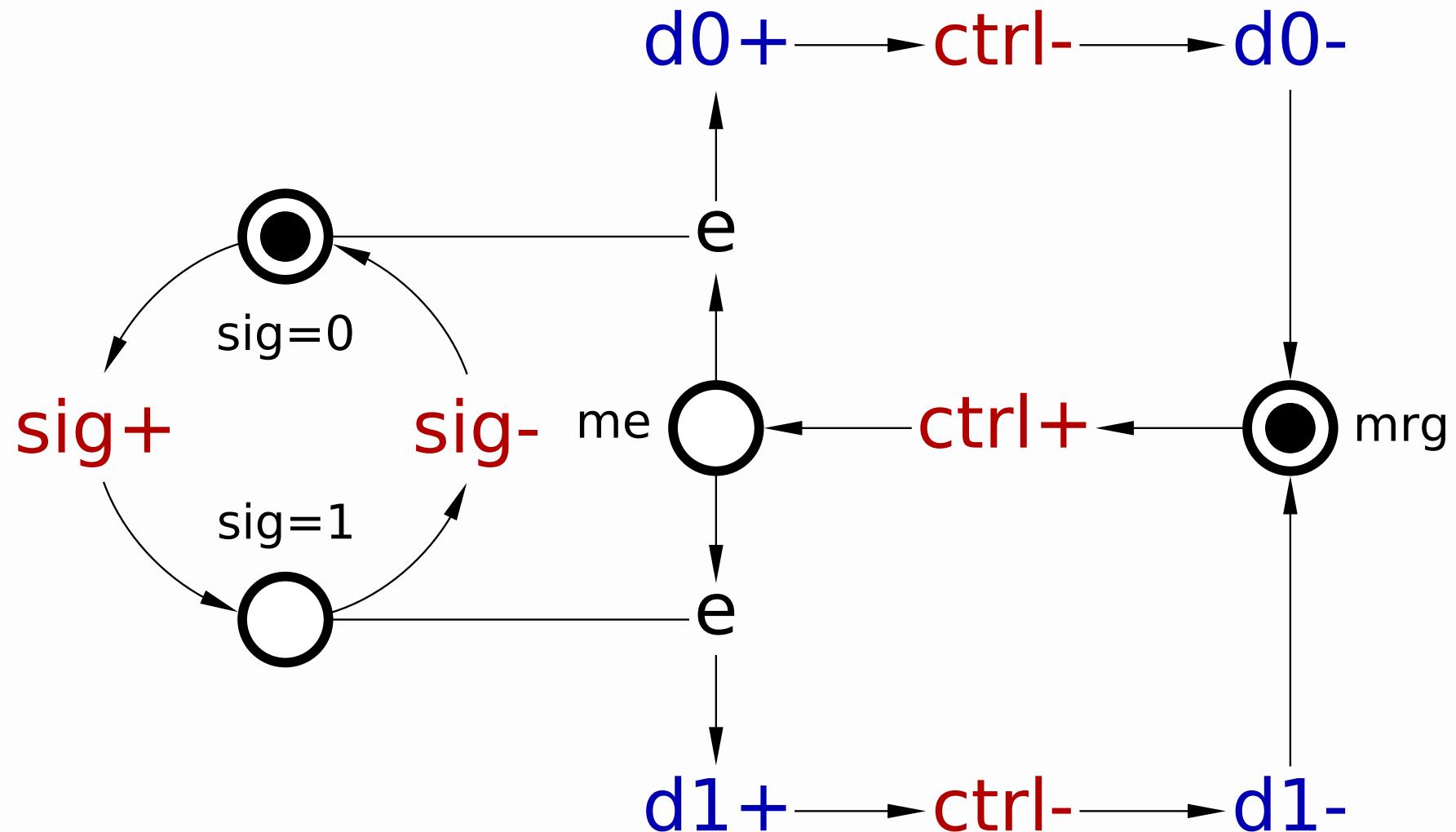

# SAMPLE: sample a hazardous input

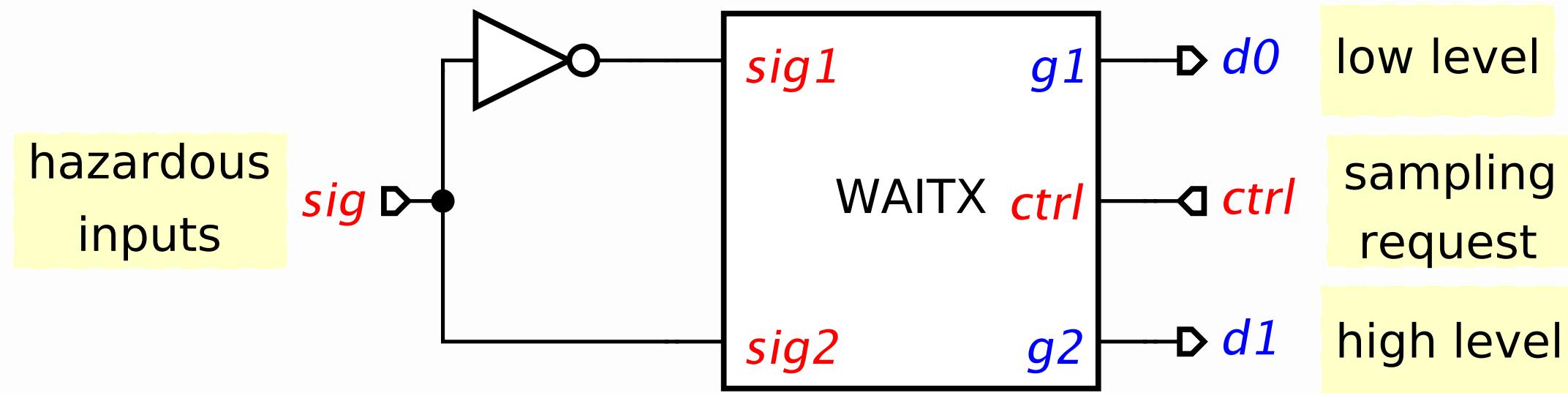

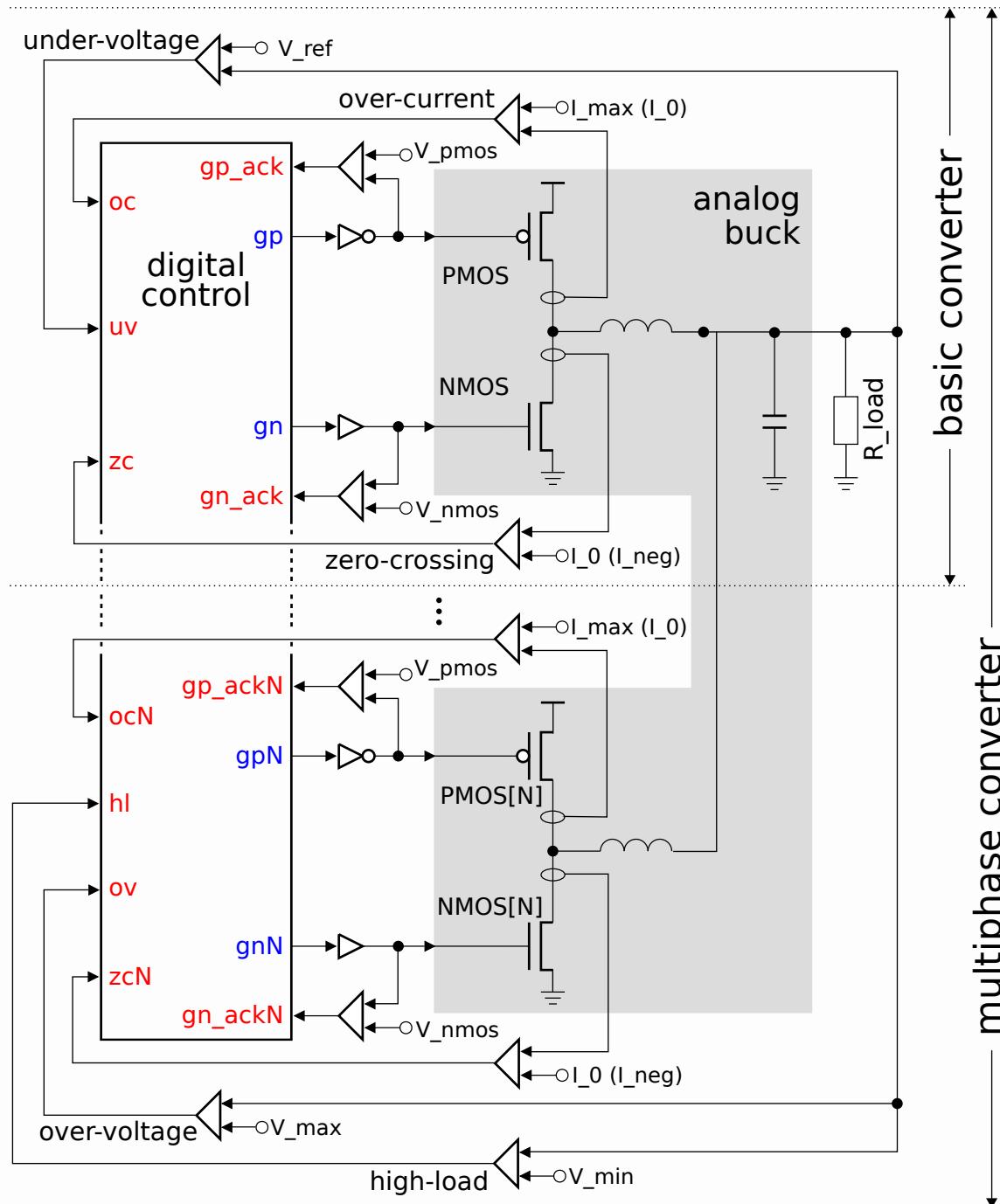
# Application example: multiphase buck converter



- Phases – pairs of power regulating transistors
  - Each phase operates as a basic buck
  - Phases are activated sequentially
  - Active phases may overlap
- Many operating modes
  - under-voltage (UV)
  - over-current (OC)
  - zero-crossing (ZC)
  - over-voltage (OV)
  - high-load (HL)
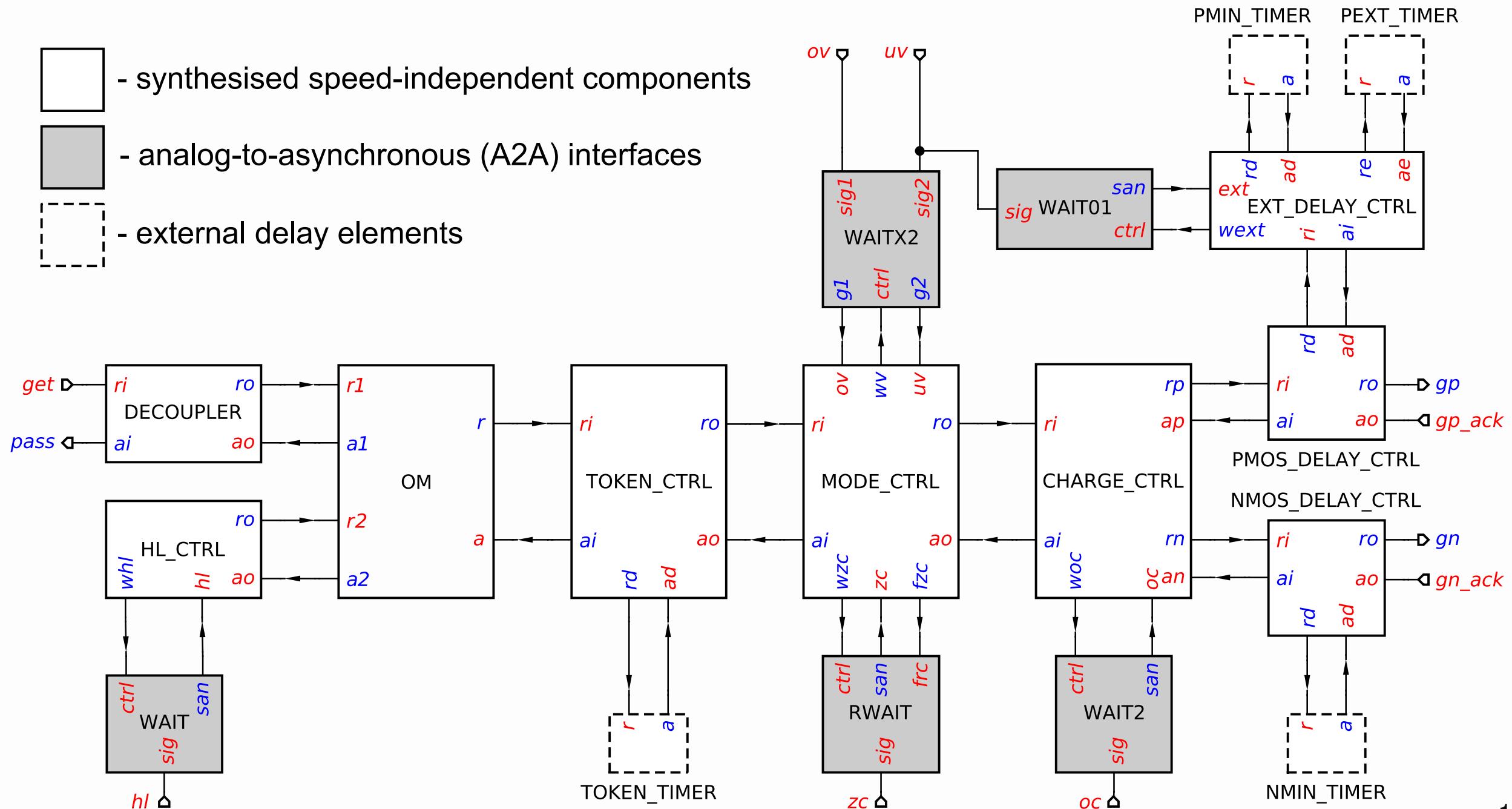
# Application example: multiphase buck converter



## Application example: multiphase buck converter

- Benefits over conventional synchronous design with synchronisers
  - No synchronisation failures
  - Quick response time (few gate delays)
  - Reaction time can be traded off for smaller coils
  - Lower voltage ripple and peak current

## Conclusions

- Library of asynchronous arbitration primitives ([workcraft.org/a2a](http://workcraft.org/a2a))
  - Low-latency synchronisation and decision-making
  - Developed and formally verified in WORKCRAFT
- Building blocks for applications that require:
  - Efficient synchronisation between clock and voltage domains
  - Sanitising ‘dirty’ signals from analog environment
- Demonstrated benefits in the domain of power converters