



Asynchronous Circuits:

Formal Verification and Synthesis

**Victor Khomenko, Andrey Mokhov,
Danil Sokolov, Alex Yakovlev**

Formal Verification of Asynchronous Circuits

2 kinds of verification

1. Verification of the STG specification

- there is no circuit yet, just an STG specification
- check if the STG makes sense
- check if the STG can be implemented as an SI circuit

2. Verification of the circuit

- given a gate-level implementation of a circuit and an STG modelling the behaviour of the environment, check if the circuit is correct

Verification of STG specification




Standard PN properties:

- **boundedness / safeness** – a digital circuit has finitely many reachable states
- **deadlock-freeness**
- **various custom reachability properties, e.g. mutual exclusion**

Verification of STG specification

Consistency: in each execution, the rising and falling edges of each signal must alternate, always starting from the same edge – reduces to a reachability property

   Intuition: at any reachable state the value of each signal is binary



Verification of STG specification


Output-persistency: an enabled output must not be disabled by another signal firing first

Intuition: disabling and enabled output can lead to a non-digital pulse on the corresponding gate output

✓ **input / input** choices: no OP violation, usually appear due to abstraction of the environment

✗ **input / output** choices: OP violation, very problematic – usually a mistake

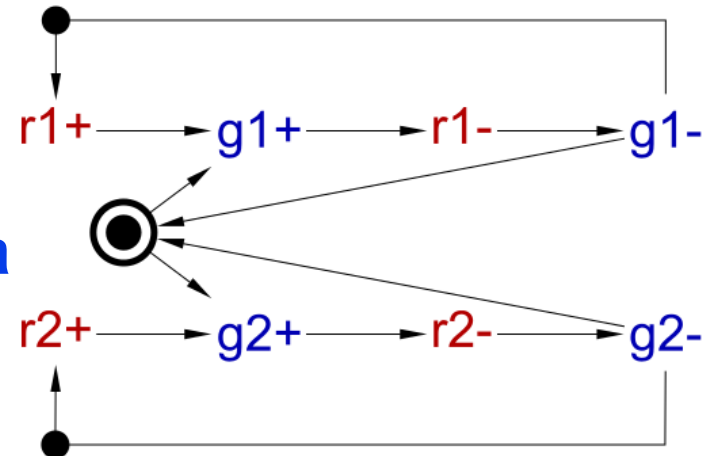😞 **output / output** choices: OP violation, usually due to arbitration; implementable using a **mutex** – can be ‘factored out’ into the environment to ensure OP




Verification of STG specification


Complete State Coding (CSC): If two reachable states have the same values of all signals then they should enable the same outputs; two states violating this property are said to be in **CSC conflict**

Intuition: the circuit can only 'see' the signal values (not the tokens in the STG!), and these should be sufficient to determine which outputs to produce

 Implementability property – CSC conflicts do not indicate that the STG is wrong; they can be resolved automatically



Example: CSC conflict

 


Verification of the circuit

Converting a gate-level circuit to an STG:


- Represent each signal s by two places, $p_{s=0}$ and $p_{s=1}$; exactly one of them is marked at any time, representing the current value of s
- Since there is no information about the environment's behaviour, it is taken to be the most general (i.e., it can always change the value of any input); this is modelled for each input signal i by adding transitions $p_{i=0} \rightarrow i+ \rightarrow p_{i=1}$ and $p_{i=1} \rightarrow i- \rightarrow p_{i=0}$
- For each output o with the next-state function $[o]=E$, compute the set and reset functions $[o\uparrow]=E|_{o=0}$ and $[o\downarrow]=\neg E|_{o=1}$ as minimised DNF
- For each term m of the set function, add a transition $p_{o=0} \rightarrow o+ \rightarrow p_{o=1}$, and for each literal s (resp. $\neg s$) in m , connect $o+$ to $p_{s=1}$ (resp. $p_{s=0}$) by a read arc; a similar process is used to define the transitions $o-$ using the reset function

Example: modelling a C-element

 

$$\begin{aligned}
 [\text{out}] &= \text{out} \cdot (\text{in1} + \text{in2}) + \text{in1} \cdot \text{in2} \\
 [\text{out}\uparrow] &= 0 \cdot (\text{in1} + \text{in2}) + \text{in1} \cdot \text{in2} = \text{in1} \cdot \text{in2} \\
 [\text{out}\downarrow] &= \neg(1 \cdot (\text{in1} + \text{in2}) + \text{in1} \cdot \text{in2}) = \\
 &= \neg(\text{in1} + \text{in2} + \text{in1} \cdot \text{in2}) = \neg(\text{in1} + \text{in2}) = \\
 &= \neg\text{in1} \cdot \neg\text{in2}
 \end{aligned}$$

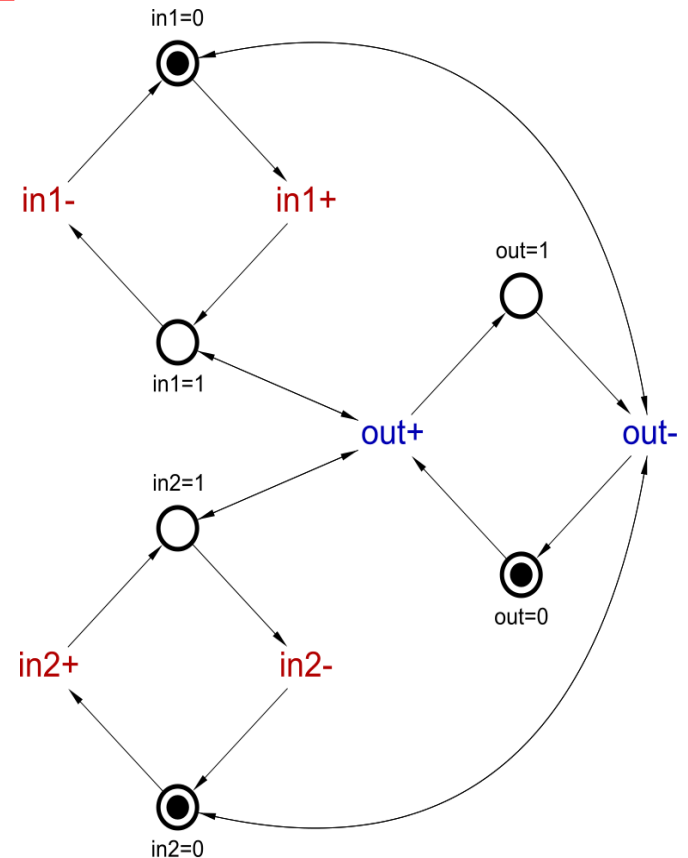- This PN has more behaviour than the specification of C-element
- Not output-persistent: after in1+ in2+ the output out+ can be disabled by in1- or in2- , i.e. there is a **hazard**
- This is because the circuit (and thus this STG) **lacks information about the environment's behaviour!**
- The circuit works correctly in an environment that fulfils the original contract



Gate-level modelling: Verification


Gate-level circuit has no information about its environment, so naïve verification will **always** reveal hazards in any non-trivial circuit with inputs. Hence need to supply the environment's behaviour during verification: **Assuming the environment fulfils the contract**, the circuit must:

- be free from **hazards**: no output can be disabled by another signal (except in mutex)
- **conform** to its environment, i.e. never produce an unexpected output – the circuit must fulfil its contract too
- be deadlock-free
- etc.

Gate-level modelling: Verification

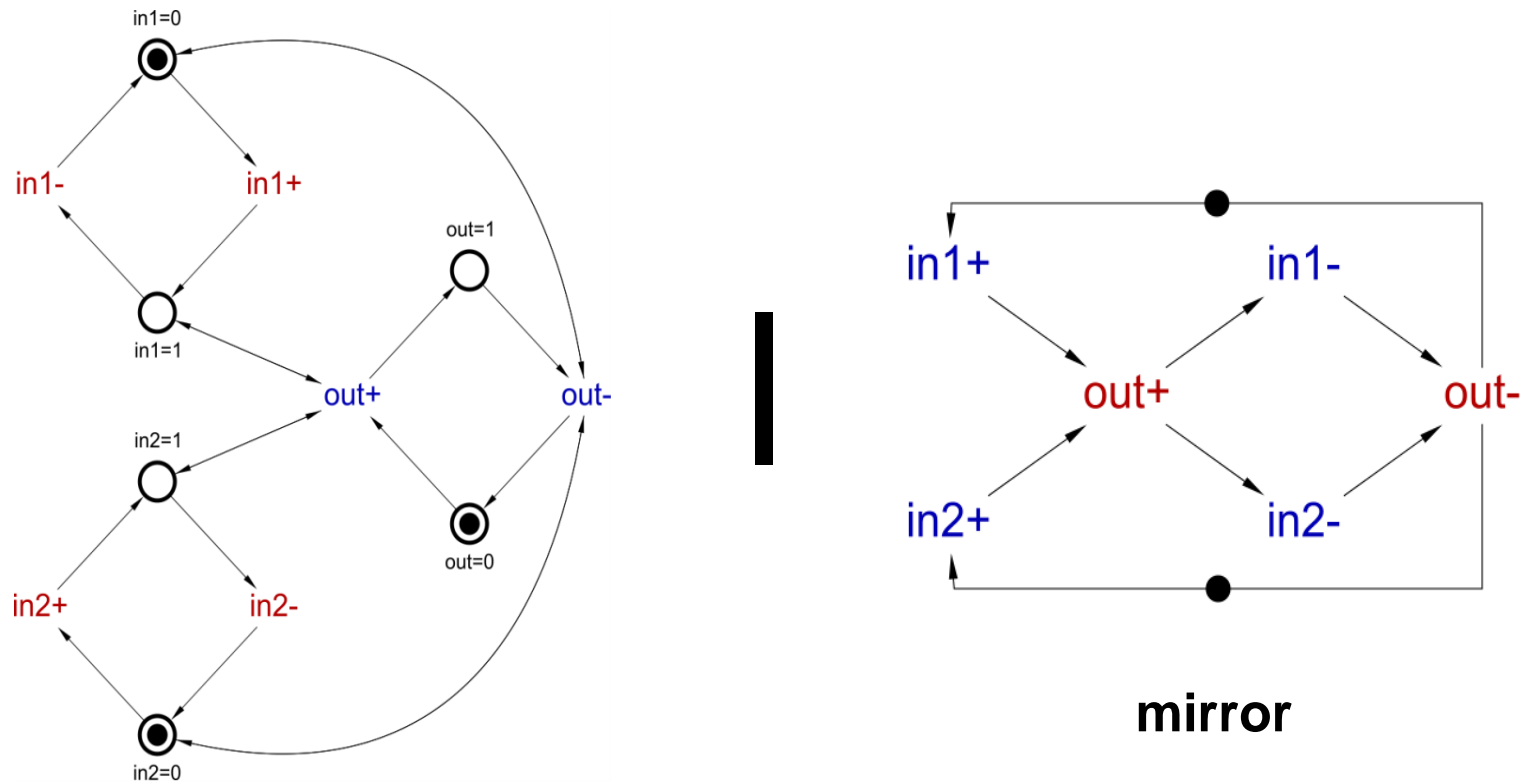
Problem: how to restrict the behaviour of the circuit by the behaviour of the environment to verify the properties?

Idea: use parallel composition! First, convert the circuit into an STG and then compose the latter with the **mirror** (i.e. inputs and outputs are swapped) of the original STG spec:





Parallel composition

 - **Idea:** Fuse transitions from different STGs that have the same label (if STGs have several transitions with the same label, fuse each such transition in STG_1 with each such transition in STG_2)
- **Example:**



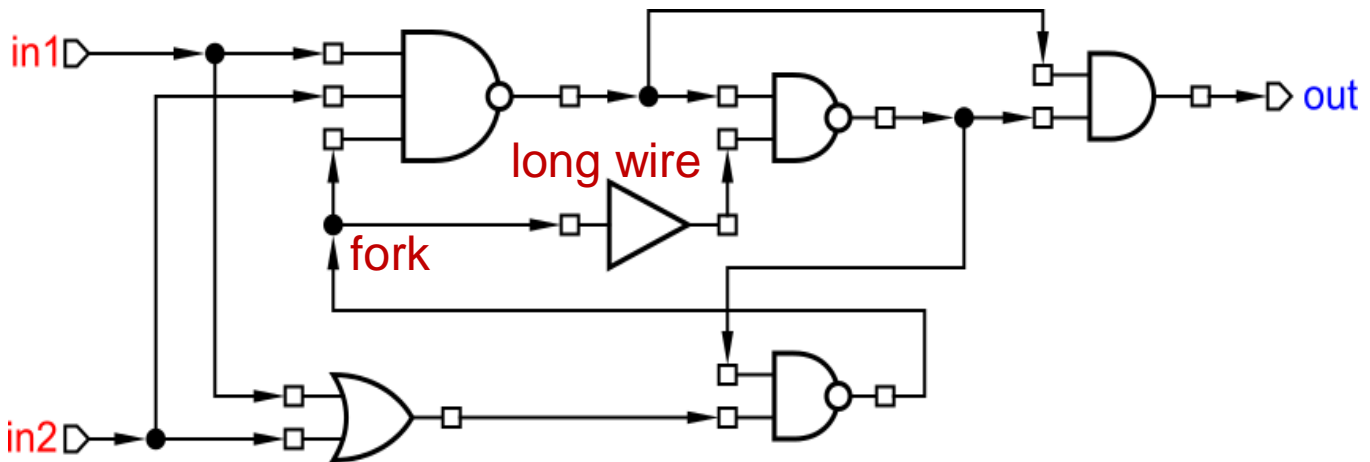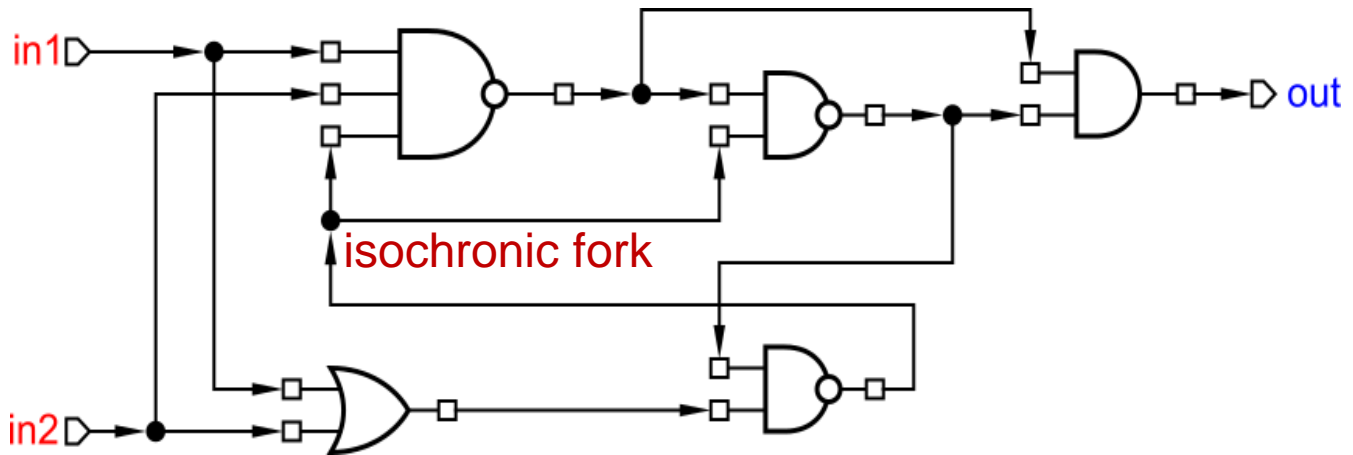Example: C-element

Can a C-element be implemented by the following circuits?



Under the Bonnet of Workcraft

PUNF – parallel unfolder

- Tool for building Petri net **unfoldings**
- Utilises multiple processor cores
- Unfoldings alleviate the **state space explosion** problem – the number of reachable states is generally exponential in the size of the specification
- Works very well for asynchronous circuits due to high concurrency and small number of choices – an ideal case for unfoldings

MPSAT – verification and synthesis


- Uses PUNF-generated prefixes as an input – completely avoids state graph
- Employs a SAT solver for efficiency
- Verifies many relevant properties, like deadlocks, CSC, etc.
- Supports **REACH** – a language to specify custom properties
- Synthesis: CSC resolution, deriving complex-gate, gC, stdC implementations, logic decomposition

PCOMP – parallel composition


- **Composes several STGs, optionally hiding the internal communication, e.g.:**
 - **to compose several modules into one**
 - **to compose a circuit with its environment for verification**

CSC Conflict Resolution


Example: VME Bus Controller

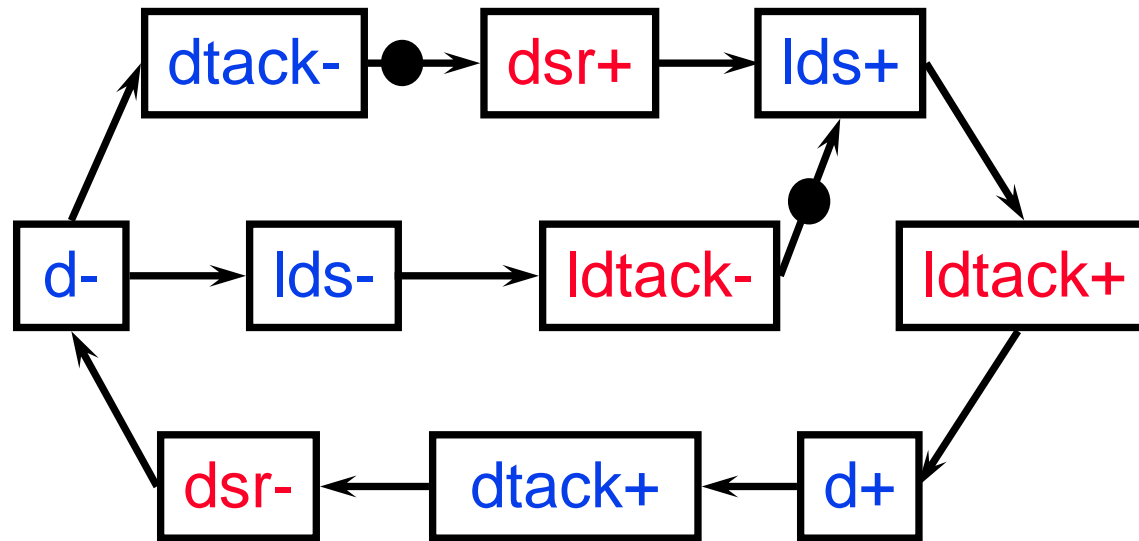

Example: CSC conflict

 


Example: Resolving the conflict

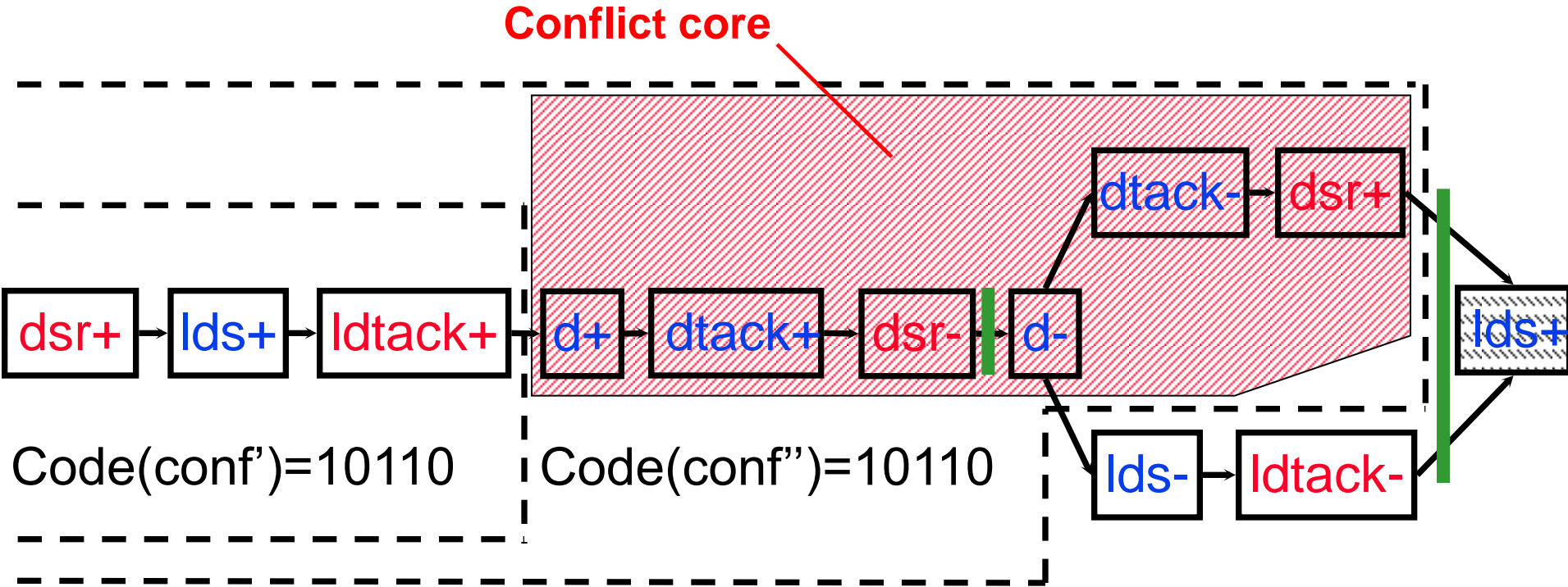


Idea: Insert **csc+** into the core and **csc-** outside the core to break the balance

Note: Cannot delay inputs!

Example: Resolving the conflict

 


Example: Resolving the conflict

 


Core map

 - Cores often overlap
- High-density areas are good candidates for signal insertion
- Analogy with topographic maps



Example: core map

 

Concurrency reduction

Introduces a new arc in the STG: $a \rightarrow b$


Note: Must not delay inputs, i.e. b cannot be an input!

Note: Changes the behaviour, impacts the environment!


Heuristic: Try not to introduce new triggers of b , e.g. if there is an arc $a^+ \rightarrow b^+$ then $a^- \rightarrow b^-$ is preferred

Used for resolving CSC conflicts and circuit simplification

 ‘Drag’ some events into the core to break the balance:




Example: Resolving the conflict

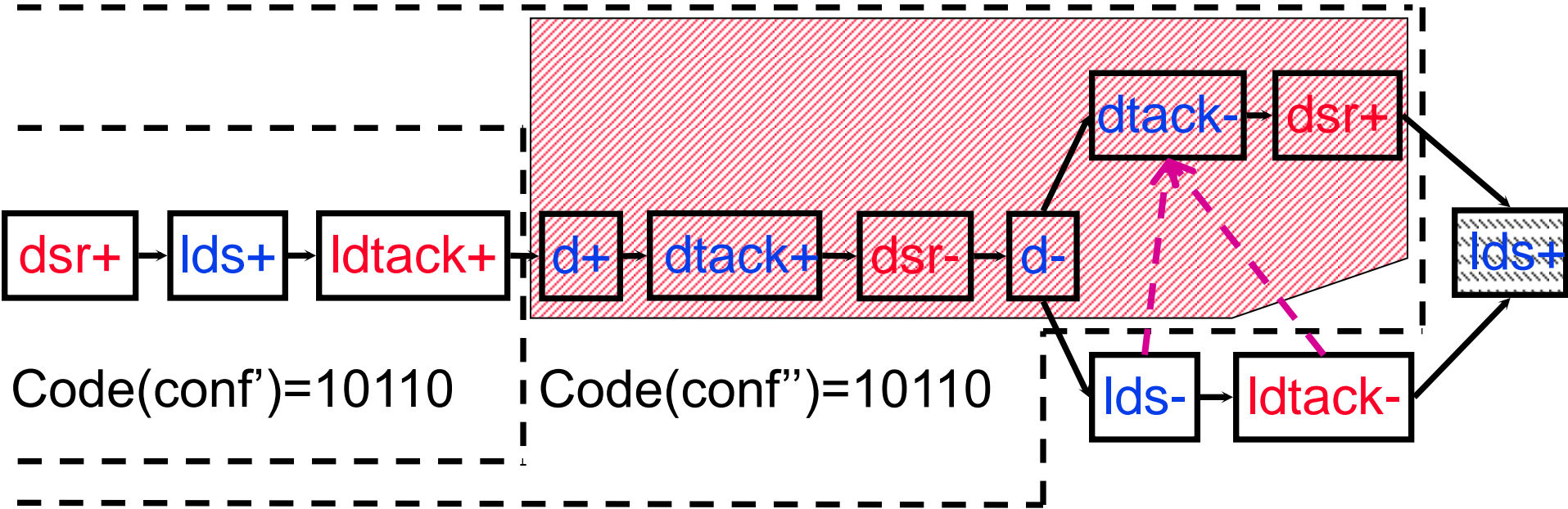


May be problematic!

Example: Resolving the conflict

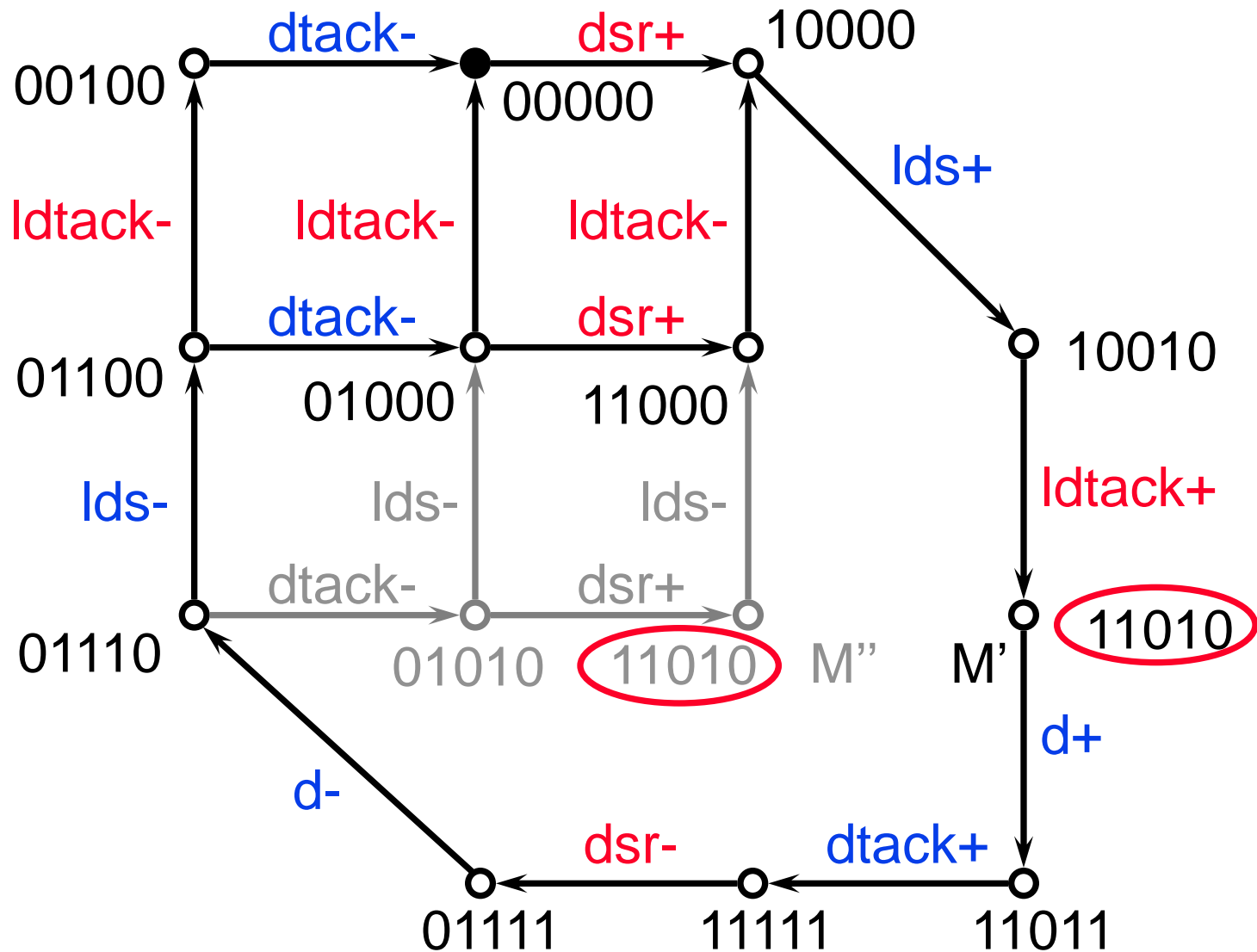


Relative timing assumptions

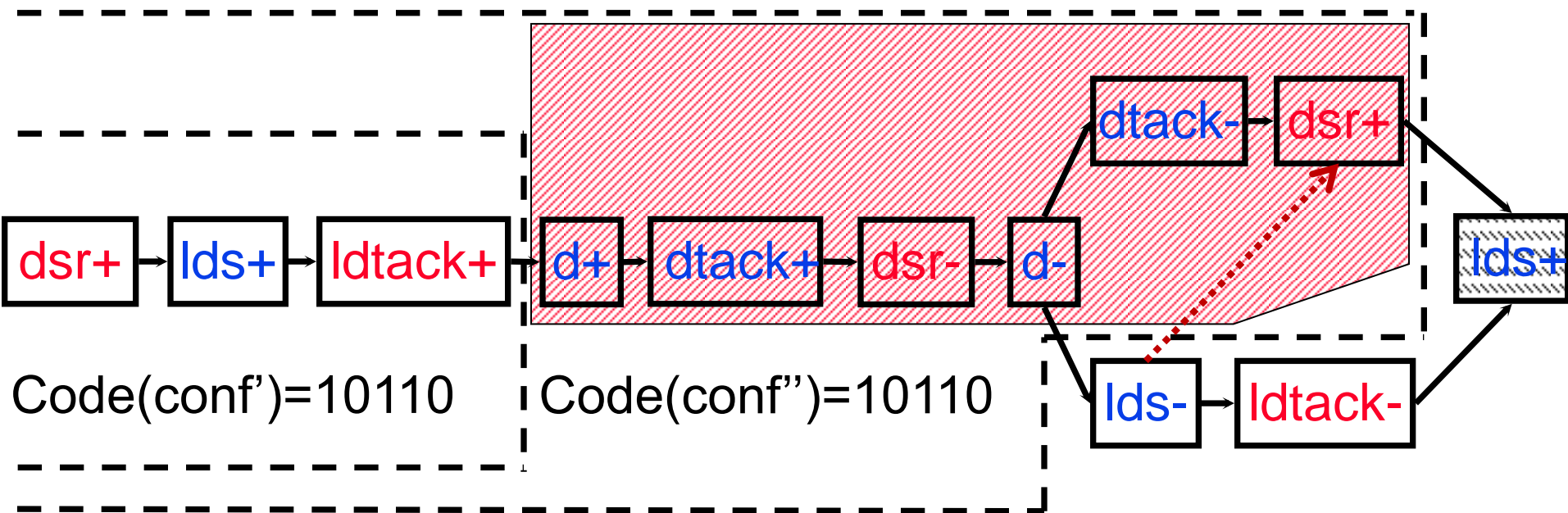- “This event will happen faster than that one”
- Break speed-independence, and generally problematic
- Similar to concurrency reductions, but the introduced arcs are special, in particular they don't trigger signals
- Can “delay” inputs



Example: Resolving the conflict

 


Comparison of the methods

- **Signal insertions – paracetamol**
 - 😊 behaviour is preserved
 - 😞 inserted signals have to be implemented
- **Concurrency reductions – antibiotic**
 - 😊 no new signals
 - 😊 reduced state graph and so more don't-cares in minimisation tables
 - 😞 change the behaviour: need to be careful if input → output (even indirectly) – this puts a new assumption on the environment!
 - 😞 can introduce deadlocks: **Circuit: a → b & Environment: b → a**
- **Timing assumptions – surgery**
 - 😊 no new signals
 - 😊 reduced state graph and so more don't-cares in minimisation tables
 - 😞 break speed-independence
 - 😞 require deep understanding of theory and the circuit's behaviour
 - 😞 introduce layout constraints, and need extensive validation
 - 😞 fragile due to variability (manufacturing, temperature, voltage, etc.)

Logic Synthesis and Implementation Styles in Asynchronous Circuits Design


Speed-independence assumptions

 - Gates/latches are **atomic** (so no internal hazards)




- Gate delays are positive and finite, but variable and unbounded
- Wire delays are negligible (SI)
- Alternatively, [some] wire forks are isochronic (QDI), i.e. wire delays can be added to gate delays

SI decomposition

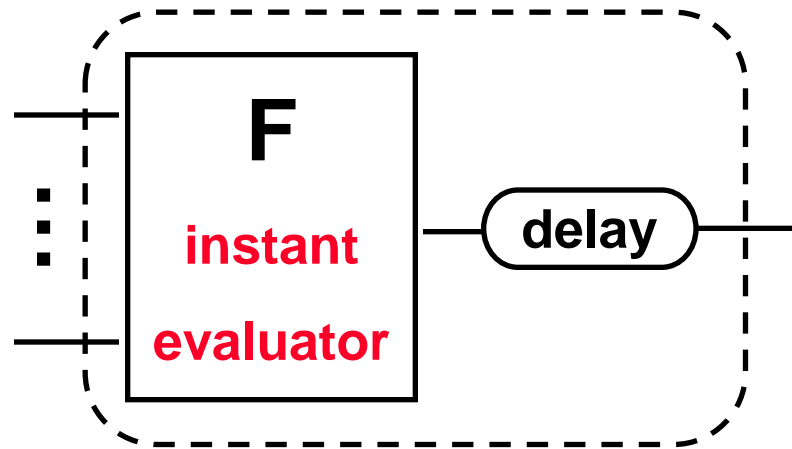

 Hazards can be introduced due to these delays!




Gates & latches

- Good citizens: **unate** gates/latches, e.g. BUFFER, AND, OR, NAND, NOR, AND-OR, OR-AND, C-element, SR-latch, RS-latch
 - Output inverters ('bubbles') can be used liberally, e.g. NAND, NOR, as the inverter's delay can be added to the gate's delay
 - Input inverters are suspect as they introduce delays, but in practice are ok if the wire between the inverter and the gate is short
- Suspects: **binate** gates, e.g. XOR, NXOR, MUX, D-latch – may have internal hazards, but may still be useful

Logic synthesis

- **Encoding (CSC) conflicts must be resolved first**
- **Several kinds of implementation can then be derived automatically:**
 - **complex-gate (CG)**
 - **generalised C-element (gC)**
 - **standard-C implementation (stdC)**
- **Can mix implementation styles on per-signal basis**
- **Logic decomposition may still be required if the gates are too complex**

Example: complex-gate synthesis

 


Code	Nxt_c
0100	1
0000	0
1000	0
0110	1
0010	0
1100	0
1110	1
1111	1
1101	1
else	-


Eqn	$(\bar{a}+c)b+d$
-----	------------------

$$Nxt_z(s) = Code_z(s) \oplus Out_z(s)$$

 
The size of this Boolean expression is not limited!



Support, triggers and context

 

 Signals whose occurrence can immediately enable a signal are called its **triggers**, e.g. the triggers of c are $\{b, d\}$. Triggers are unique, and are always in the support.




Signals that are the inputs of the gate producing a signal form its **support**, e.g. the support of c is $\{a, b, c, d\}$. Supports are not unique in general.

Signals in the support which are not triggers are called the **context**, e.g. the context of c is $\{a, c\}$. Context is not unique in general.

support = triggers + context


Example: gC implementation

 


Code	Set _c	Reset _c
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-
Eqn	$\bar{a}b+d$	\bar{b}

$$Set_z(s) = \begin{cases} 1 & \text{if } Out_{z+}(s) = 1 \\ 0 & \text{if } Next_z(s) = 0 \\ - & \text{otherwise} \end{cases} \quad Reset_z(s) = \begin{cases} 1 & \text{if } Out_{z-}(s) = 1 \\ 0 & \text{if } Next_z(s) = 1 \\ - & \text{otherwise} \end{cases}$$

 Implemented as pull-up and pull-down networks of transistors and a 'keeper'; assumed to be **atomic**





Example: stdC implementation

 

Code	Set _c	Reset _c
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-

'Monotonic cover' constraints

Eqn	Set _c	Reset _c
	$\bar{a}b\bar{c}+d$	\bar{b}

  

Logic Decomposition

- Often complex-gates are too complex to be mapped to a gate library, and so **logic decomposition** is required
- Cannot naïvely break up complex-gates – this is likely to introduce hazards (at least, timing assumptions are required)
- Decomposition is one of the most difficult tasks – no guarantee that automatic decomposition will succeed
- Manual changes in the STG may be required:
 - identify the most complex gates
 - try some concurrency reductions
 - try to decompose your circuit into smaller blocks
 - ‘be creative’