



# **Logic Synthesis and Implementation Styles in Asynchronous Circuits Design**


**[Victor.Khomenko@ncl.ac.uk](mailto:Victor.Khomenko@ncl.ac.uk)**

**School of Computing Science,**

**Newcastle University, UK**

 
# Speed-independence assumptions

- Gates/latches are **atomic** (so no internal hazards)




- Gate delays are positive and finite, but variable and unbounded
- Wire delays are negligible (SI)
- Alternatively, [some] wire forks are isochronic (QDI), i.e. wire delays can be added to gate delays

# SI decomposition

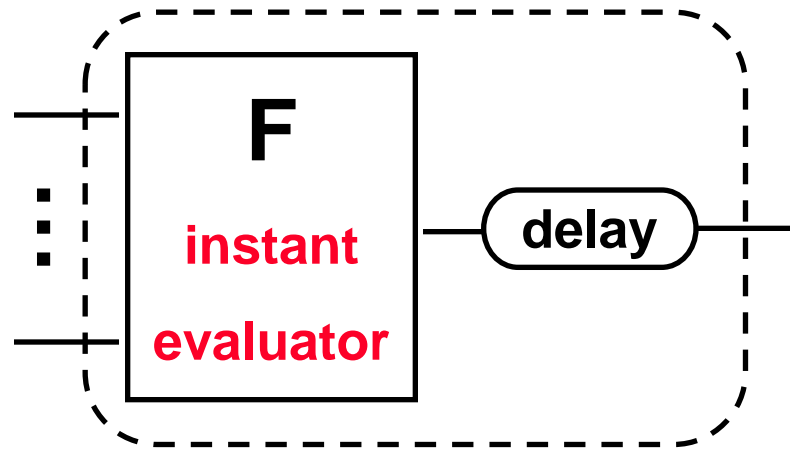

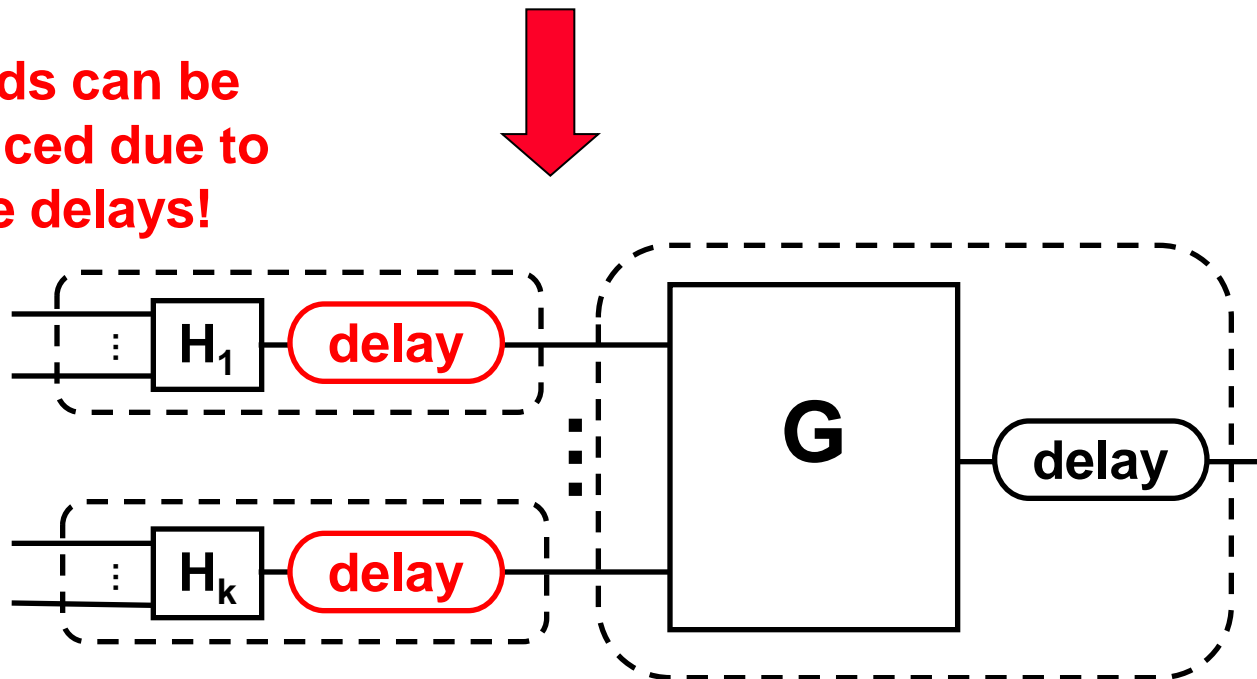Hazards can be introduced due to these delays!




# Gates & latches

- Good citizens: **unate** gates/latches, e.g. BUFFER, AND, OR, NAND, NOR, AND-OR, OR-AND, C-element, SR-latch, RS-latch
  - Output inverters ('bubbles') can be used liberally, e.g. NAND, NOR, as the inverter's delay can be added to the gate's delay
  - Input inverters are suspect as they introduce delays, but in practice are ok if the wire between the inverter and the gate is short
- Suspects: **binate** gates, e.g. XOR, NXOR, MUX, D-latch – may have internal hazards, but may still be useful

# Logic synthesis

- **Encoding (CSC) conflicts must be resolved first**
- **Several kinds of implementation can then be derived automatically:**
  - **complex-gate (CG)**
  - **generalised C-element (gC)**
  - **standard-C implementation (stdC)**
- **Can mix implementation styles on per-signal basis**
- **Logic decomposition may still be required if the gates are too complex**

# Example: complex-gate synthesis

 


Code	Nxt <sub>c</sub>
0100	1
0000	0
1000	0
0110	1
0010	0
1100	0
1110	1
1111	1
1101	1
else	-


Eqn	$(\bar{a}+c)b+d$
-----	------------------

$$Nxt_z(s) = Code_z(s) \oplus Out_z(s)$$

 
**The size of this Boolean expression is not limited!**



# Support, triggers and context

 

 Signals whose occurrence can immediately enable a signal are called its **triggers**, e.g. the triggers of  $c$  are  $\{b, d\}$ . Triggers are unique, and are always in the support.




Signals that are the inputs of the gate producing a signal form its **support**, e.g. the support of  $c$  is  $\{a, b, c, d\}$ . Supports are not unique in general.

Signals in the support which are not triggers are called the **context**, e.g. the context of  $c$  is  $\{a, c\}$ . Context is not unique in general.

**support = triggers + context**


# Example: gC implementation

 

Code	Set <sub>c</sub>	Reset <sub>c</sub>
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-
Eqn	$\bar{a}b+d$	$\bar{b}$


$$Set_z(s) = \begin{cases} 1 & \text{if } Out_{z+}(s) = 1 \\ 0 & \text{if } Next_z(s) = 0 \\ - & \text{otherwise} \end{cases} \quad Reset_z(s) = \begin{cases} 1 & \text{if } Out_{z-}(s) = 1 \\ 0 & \text{if } Next_z(s) = 1 \\ - & \text{otherwise} \end{cases}$$

 Implemented as pull-up and pull-down networks of transistors and a 'keeper'; assumed to be **atomic**







# Example: stdC implementation

 

Code	Set <sub>c</sub>	Reset <sub>c</sub>
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-

'Monotonic cover' constraints

Eqn	$\bar{a}b\bar{c}+d$	$\bar{b}$
-----	---------------------	-----------

  

# Logic Decomposition

- Often complex-gates are too complex to be mapped to a gate library, and so **logic decomposition** is required
- Cannot naïvely break up complex-gates – this is likely to introduce hazards (at least, timing assumptions are required)
- Decomposition is one of the most difficult tasks – no guarantee that automatic decomposition will succeed
- Manual changes in the STG may be required:
  - Identify the most complex gates
  - Try some concurrency reductions
  - Try to decompose your circuit into smaller blocks
  - ‘Be creative’




# CSC Conflict Resolution


[Victor.Khomenko@ncl.ac.uk](mailto:Victor.Khomenko@ncl.ac.uk)

Online tutorial available from [workcraft.org](http://workcraft.org)


# Example: VME Bus Controller

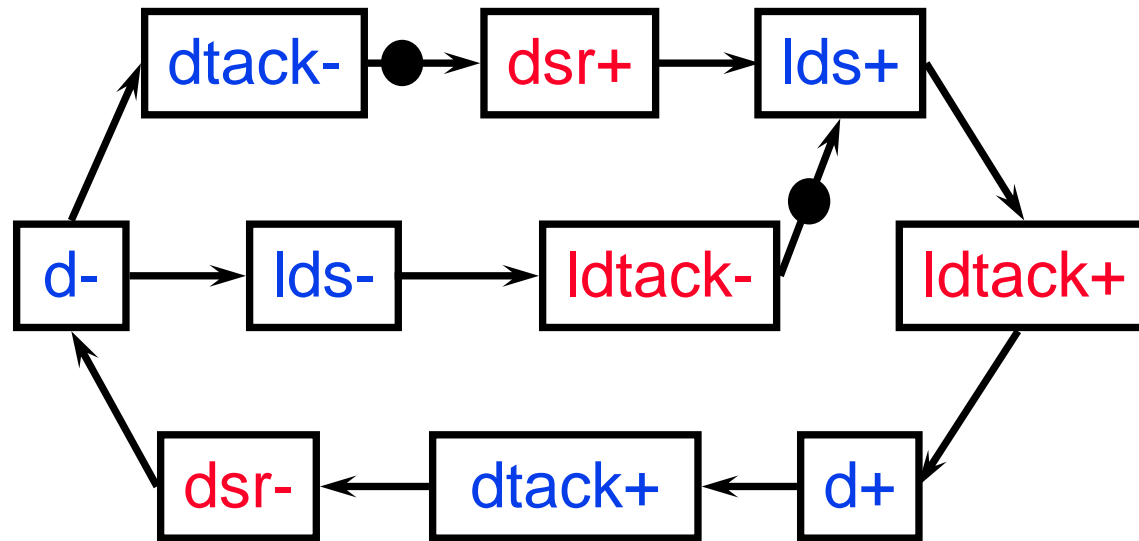

# Example: CSC conflict

 


# Example: Resolving the conflict

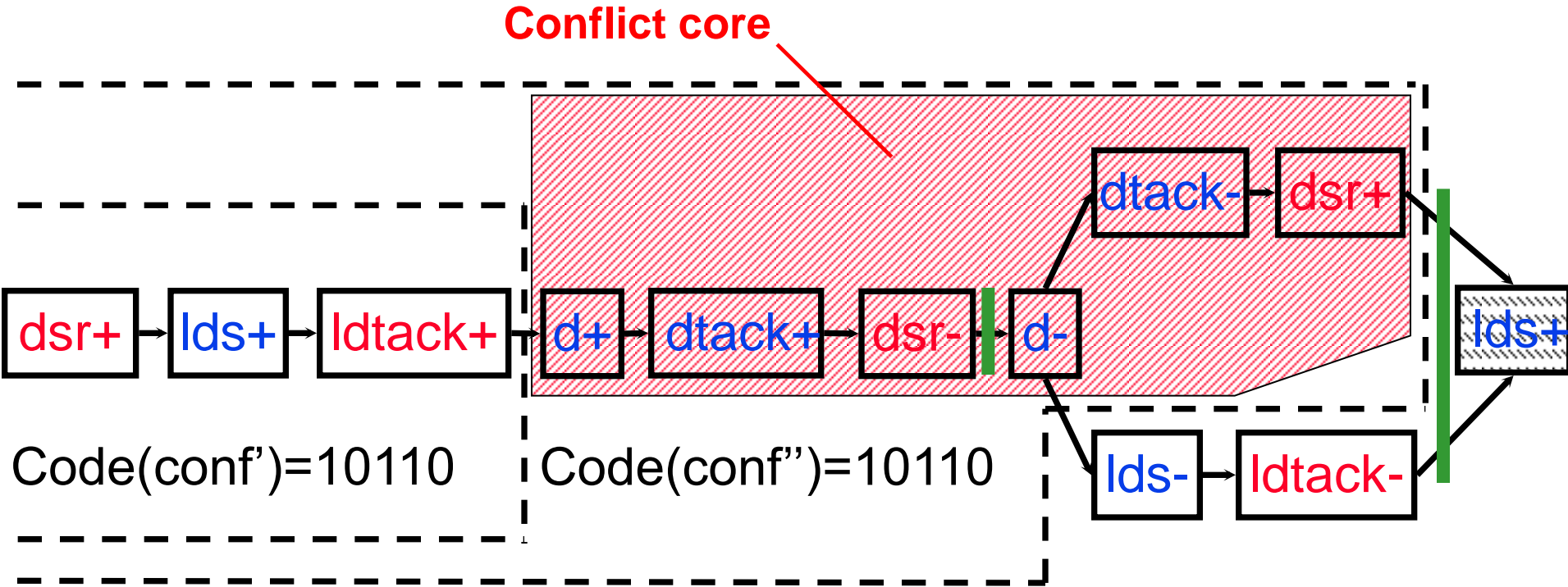


**Idea:** Insert **csc+** into the core and **csc-** outside the core to break the balance

**Note:** Cannot delay inputs!

# Example: Resolving the conflict

 


# Example: Resolving the conflict

 



 
# Core map

- Cores often overlap
- High-density areas are good candidates for signal insertion
- Analogy with topographic maps



# Example: core map

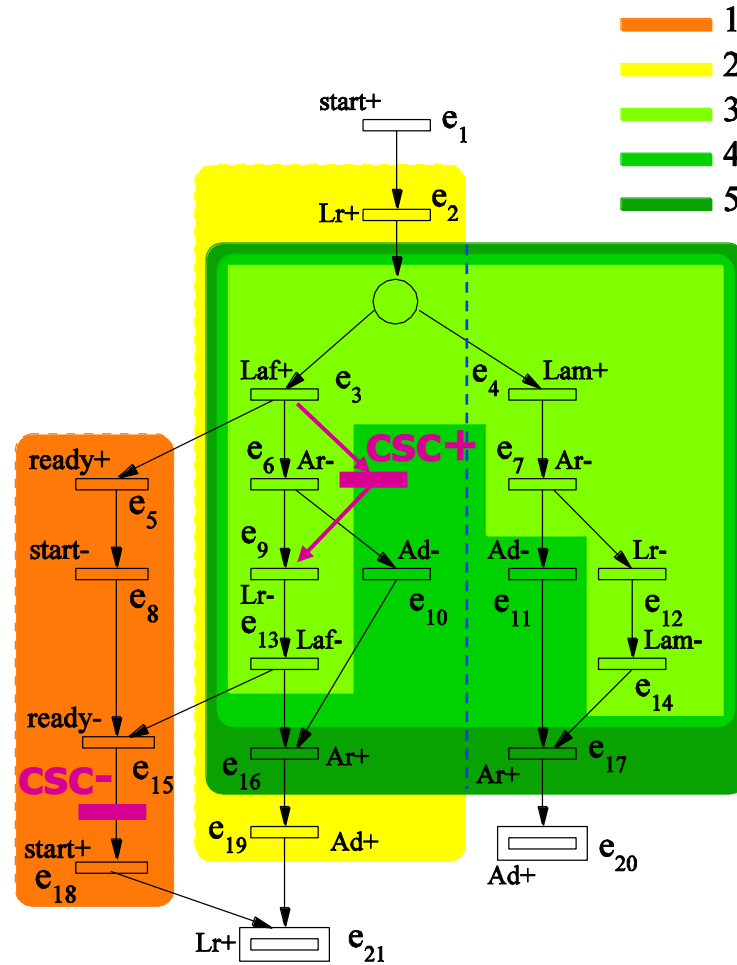

# Concurrency reduction

Introduces a new arc in the STG:  $a \rightarrow b$


**Note:** Must not delay inputs, i.e.  $b$  cannot be an input!

**Note:** Changes the behaviour, impacts the environment!


**Heuristic:** Try not to introduce new triggers of  $b$ , e.g. if there is an arc  $a^+ \rightarrow b^+$  then  $a^- \rightarrow b^-$  is preferred

Used for resolving CSC conflicts and circuit simplification

 ‘Drag’ some events into the core to break the balance:




# Example: Resolving the conflict

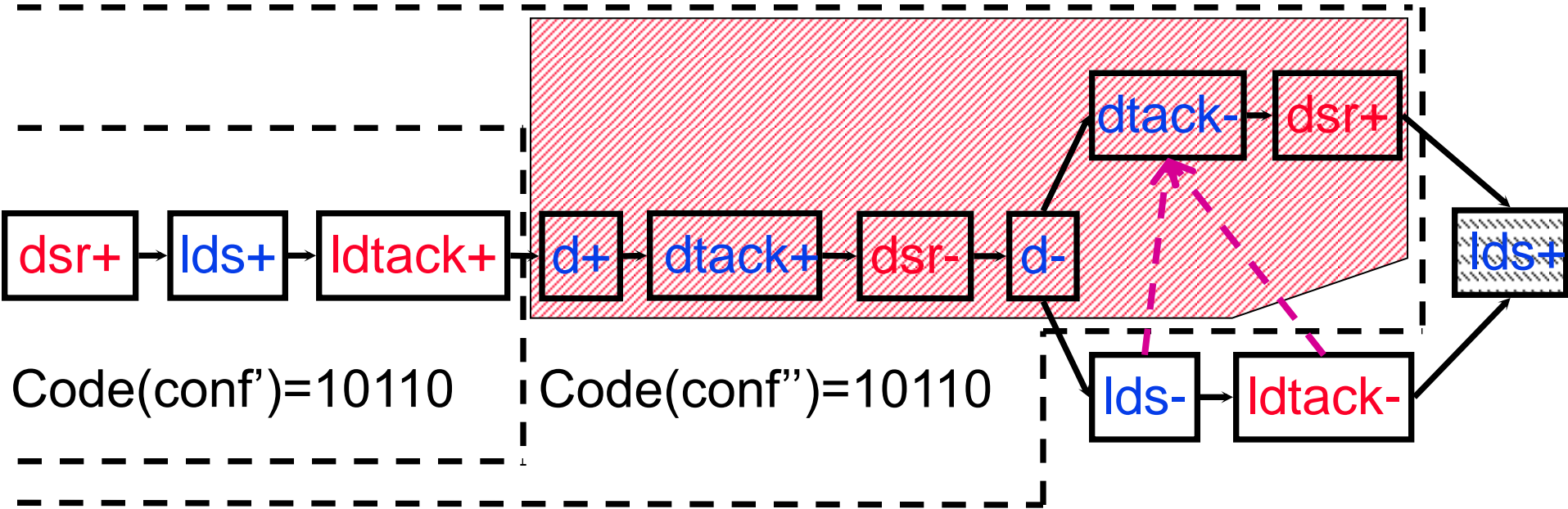


**May be problematic!**

# Example: Resolving the conflict

 

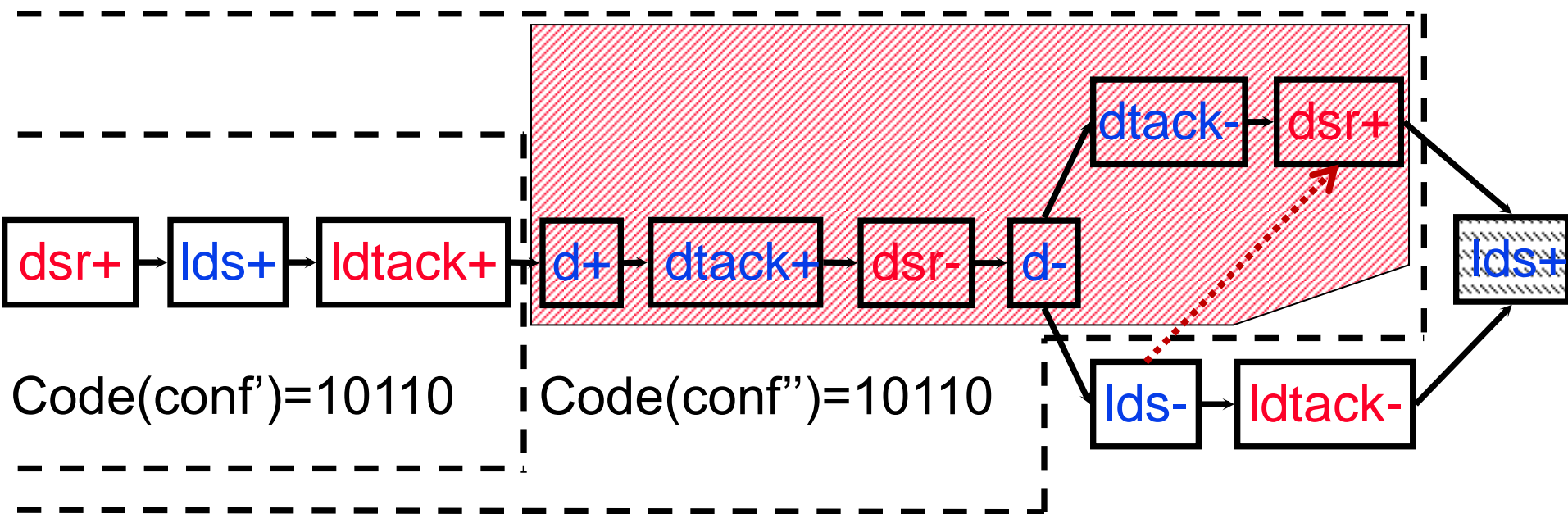
# Relative timing assumptions

- “This event will happen faster than that one”
- Break speed-independence, and generally problematic
- Similar to concurrency reductions, but the introduced arcs are special, in particular they don't trigger signals
- Can “delay” inputs



# Example: Resolving the conflict

 

# Comparison of the methods

- **Signal insertions – paracetamol**
  - 😊 behaviour is preserved
  - 😞 inserted signals have to be implemented
- **Concurrency reductions – antibiotic**
  - 😊 no new signals
  - 😊 reduced state graph and so more don't-cares in minimisation tables
  - 😞 change the behaviour: need to be careful if input  $\rightarrow$  output (even indirectly) – this puts a new assumption on the environment!
  - 😞 can introduce deadlocks: **Circuit:  $a \rightarrow b$  & Environment:  $b \rightarrow a$**
- **Timing assumptions – surgery**
  - 😊 no new signals
  - 😊 reduced state graph and so more don't-cares in minimisation tables
  - 😞 break speed-independence
  - 😞 require deep understanding of theory and the circuit's behaviour
  - 😞 introduce layout constraints, and need extensive validation
  - 😞 fragile due to variability (manufacturing, temperature, voltage, etc.)

Online tutorial:  
[workcraft.org](http://workcraft.org)