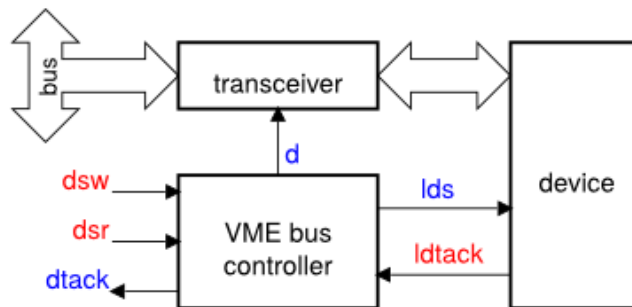


## Synthesis and verification of VME bus controller

A controller for VME bus [[http://en.wikipedia.org/wiki/VME bus](http://en.wikipedia.org/wiki/VME_bus)] provides an interface between a data bus and a slave device, as shown in the following diagram.





The controller has two modes of operation: reading from the device into the bus (activated by  $dsr+$ ) and writing from the bus into the device (activated by  $dsw+$ ).

In the reading mode, a request to read data from the device is made through  $lds+$ . When the device has the data ready and this is acknowledged by  $ldtack+$ , the controller opens the transceiver by  $d+$  and notifies the bus that data is ready for transfer by  $dtack+$ . After the read operation is complete, all the signals return to the initial state.

In the writing mode, once the data is stable on the bus, the transceiver is opened by  $d+$ , and the write request is made by  $lds+$ . When the device acknowledges the receipt of data by  $ldtack+$ , the transceiver is closed with  $d-$ , thus isolating the device from the bus, and the bus is notified that the write operation is complete by  $dtack+$ . After that all the signals return to the initial state.

 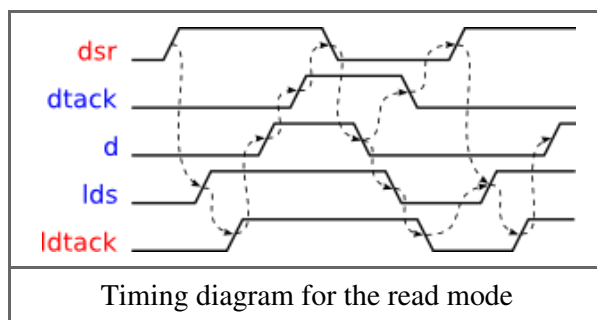These two modes of VME control are captured by the following timing diagrams.





## Modelling


Model the read mode of VME controller with an STG. Create a new STG work called *stg-vme-read* and capture the sequence of events of the corresponding timing diagram.

Do the same for the write mode of VME bus control, in a separate STG work called *stg-vme-write*.

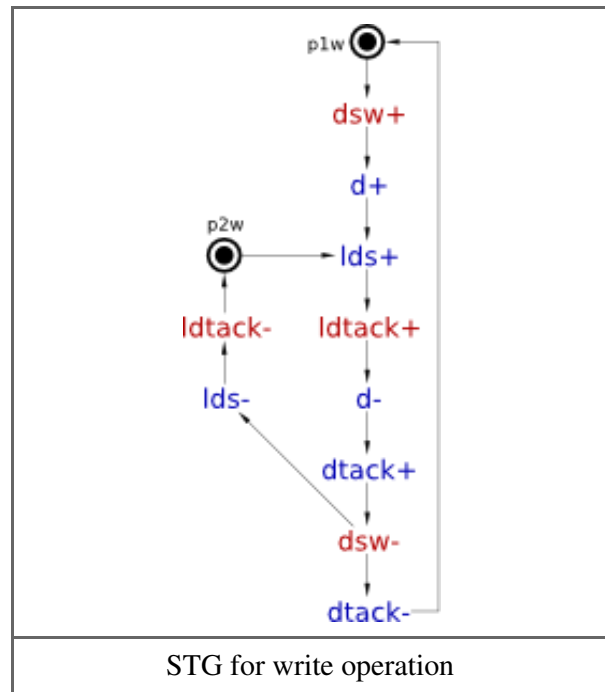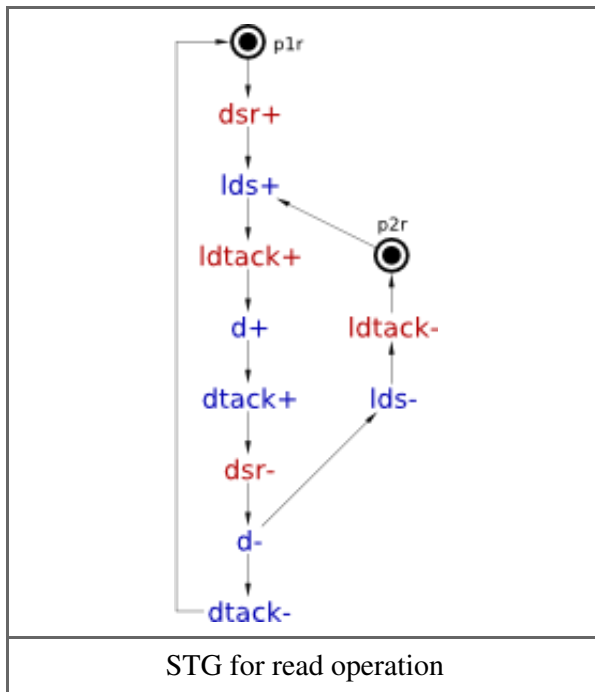The result should be similar to the following STGs.




The two STGs describe the behaviour of the same circuit and need to be combined into one specification by merging their initial states. Create a new STG work called *stg-vme-read\_write* and copy-paste the STGs from *stg-vme-read* and *stg-vme-write* works into it. Create a marked place  $p1$  that replaces the places  $p1r$  and  $p1w$ . Similarly, substitute the places  $p2r$  and  $p2w$  with a new marked place  $p2$ . The result should look as follows (note that the place  $p2$  is a *controlled choice* whose decision is determined by the *free choice* place  $p1$ ).

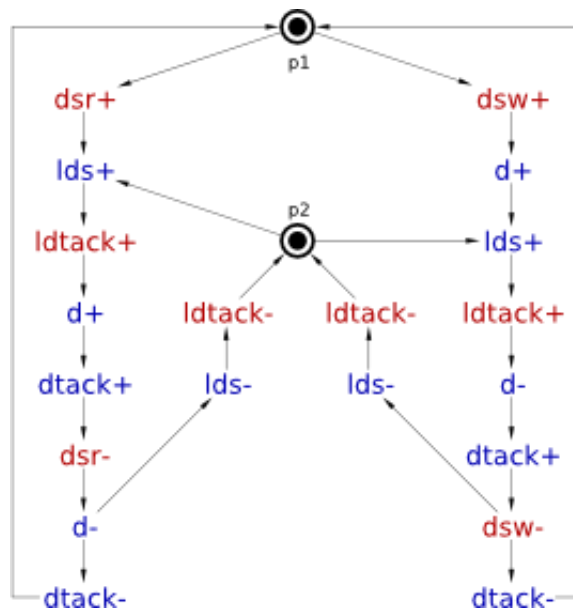

Note the concurrency between the transitions resetting the device ( $lds-$  and  $ldtack-$ ) and the new requests from the bus ( $dsr+$  and  $dsw+$ ): A new request can arrive while the device is still resetting, thereby allowing concurrent operation of the bus and the device. This concurrency is the “meaning of life” of VME bus controller.

# Validation and verification of the STG specification

Activate the **simulation tool**  and exercise the obtained STG model to better understand the behaviour of VME bus controller. Click one of the enabled signal transitions (they are highlighted in orange) to *fire* it. Note that the sequence of fired transitions is recorded in the simulation trace that is somewhat similar to the original timing diagram. Check that the simulation traces correspond to the intended behaviour of VME bus controller.

Verify the STG specification for the following properties using *Tools*→*Verification* menu:

- Deadlocks
- Consistency
- Output persistence
- Complete State Coding (CSC)


This STG does not have CSC, which means there are two reachable states that have the same value of all signals but enable different outputs. These states are said to be in *CSC conflict*. Specifications with CSC conflicts cannot be directly implemented as circuits. One way of resolving CSC conflicts is to insert new **internal** signals into the STG. These internal signals add memory into the circuit helping it to trace the current state.

## Synthesis

Resolve the encoding conflict using Petrifly via *Tools*→*Encoding conflicts*→*Resolve CSC conflicts [Petrify]* menu. Petrifly will insert a new signal **csc0** distinguishing between states that are in CSC conflict. The result could look like the following STG (note that the solution is not unique and you may get a slightly different STG):


The obtained STG specification has CSC and can now be synthesised into an asynchronous circuit implementation either with *Petrify* or *MPSat* backend tool. A complex gate solution obtained with *Petrify* is as follows (note that the solution is not unique and you may get slightly different equations):
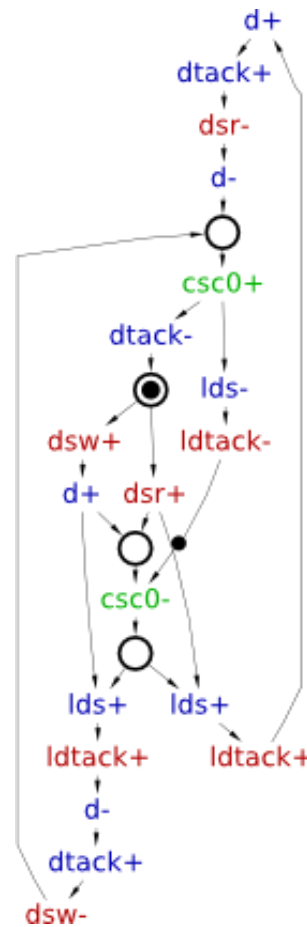
$$\begin{aligned}
 [d] &= dsr \ ldtack \ csc0' + dsw \ (csc0 + ldtack'); \\
 [dtack] &= d' \ dsr' \ csc0' + d \ dsw'; \\
 [lds] &= csc0'; \\
 [csc0] &= dsr' \ d' \ (dsw' + csc0) + ldtack \ csc0;
 \end{aligned}$$


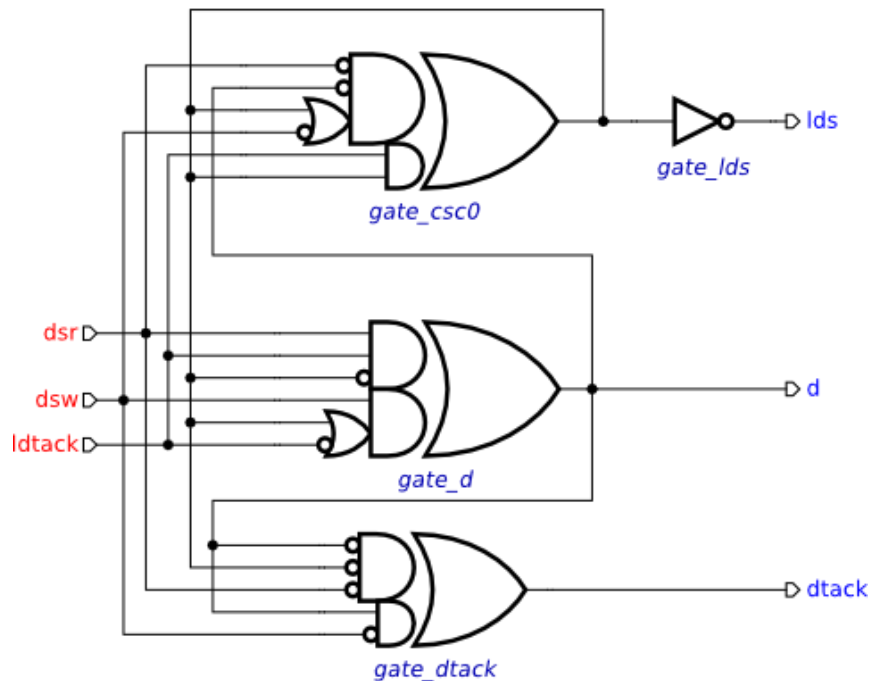
## Verification of the circuit implementation

Download the following complex-gate implementation of the VME bus controller [circuit-vme-cg.work](#) (4.99 KiB).



Assign the original STG describing the contract with the environment to the circuit model. This can be achieved as follows:

- In the circuit editor make sure that no components are selected (click on the editor canvas).
- In the property editor choose the *Environment URI* property and select the work file with the original STG specification.

Use the *Tools*→*Verification* menu to verify that the circuit implementation is:

- deadlock-free;
- hazard-free;
- conforms to the original STG specification.

## Solutions

Download all the Workcraft models discussed in this section here:

[VME bus controller models \(27.74 KiB\)](#)