 


Synthesis and verification of VME bus controller

A controller for VME bus [[http://en.wikipedia.org/wiki/VME bus](http://en.wikipedia.org/wiki/VME_bus)] provides an interface between a data bus and a slave device, as shown in the following diagram.





The controller has two modes of operation: reading from the device into the bus (activated by **dsr+**) and writing from the bus into the device (activated by **dsw+**).

In the reading mode, a request to read data from the device is made through **lds+**. When the device has the data ready and this is acknowledged by **ldtack+**, the controller opens the transceiver by **d+** and notifies the bus that data is ready for transfer by **dtack+**. After the read operation is complete, all the signals return to the initial state.

In the writing mode, once the data is stable on the bus, the transceiver is opened by **d+**, and the write request is made by **lds+**. When the device acknowledges the receipt of data by **ldtack+**, the transceiver is closed with **d-**, thus isolating the device from the bus, and the bus is notified that the write operation is complete by **dtack+**. After that all the signals return to the initial state.

  These two modes of VME control are captured by the following timing diagrams.





Modelling


Model the read mode of VME controller with an STG. Create a new STG work called *stg-vme-read* and capture the sequence of events of the corresponding timing diagram.

Do the same for the write mode of VME bus control, in a separate STG work called *stg-vme-write*.

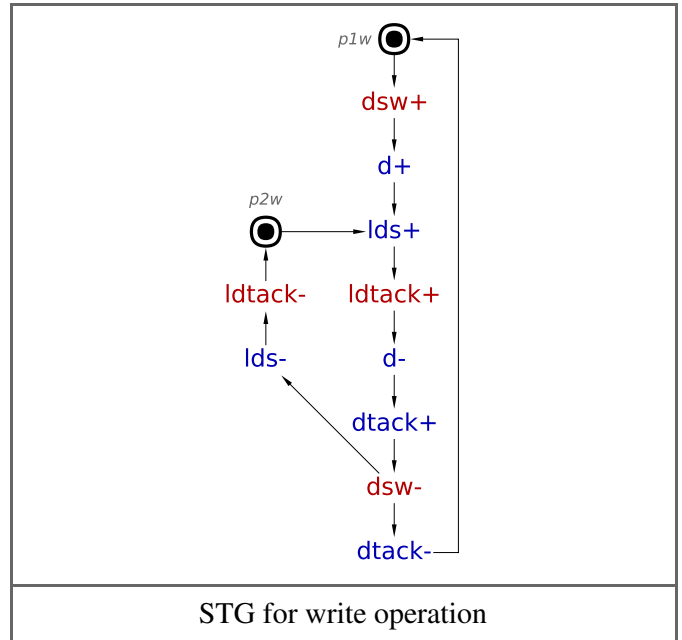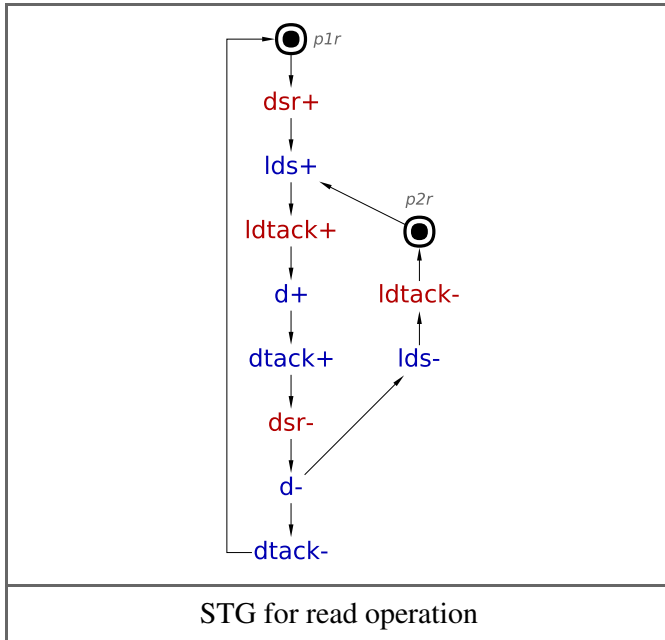The result should be similar to the following STGs.



The two STGs describe the behaviour of the same circuit and need to be combined into one specification by merging their initial states. Create a new STG work called *stg-vme-read_write* and copy-paste the STGs from *stg-vme-read* and *stg-vme-write* works into it. Merge places $p1r$ and $p1w$ into a single place by first selecting them (hold **Shift** and click them with the mouse) and then using the *Transformations* → *Merge selected places* menu item. Rename the resulting place to $p1$. Similarly, merge $p2r$ and $p2w$ and rename the resulting place to $p2$. The result should look as follows.

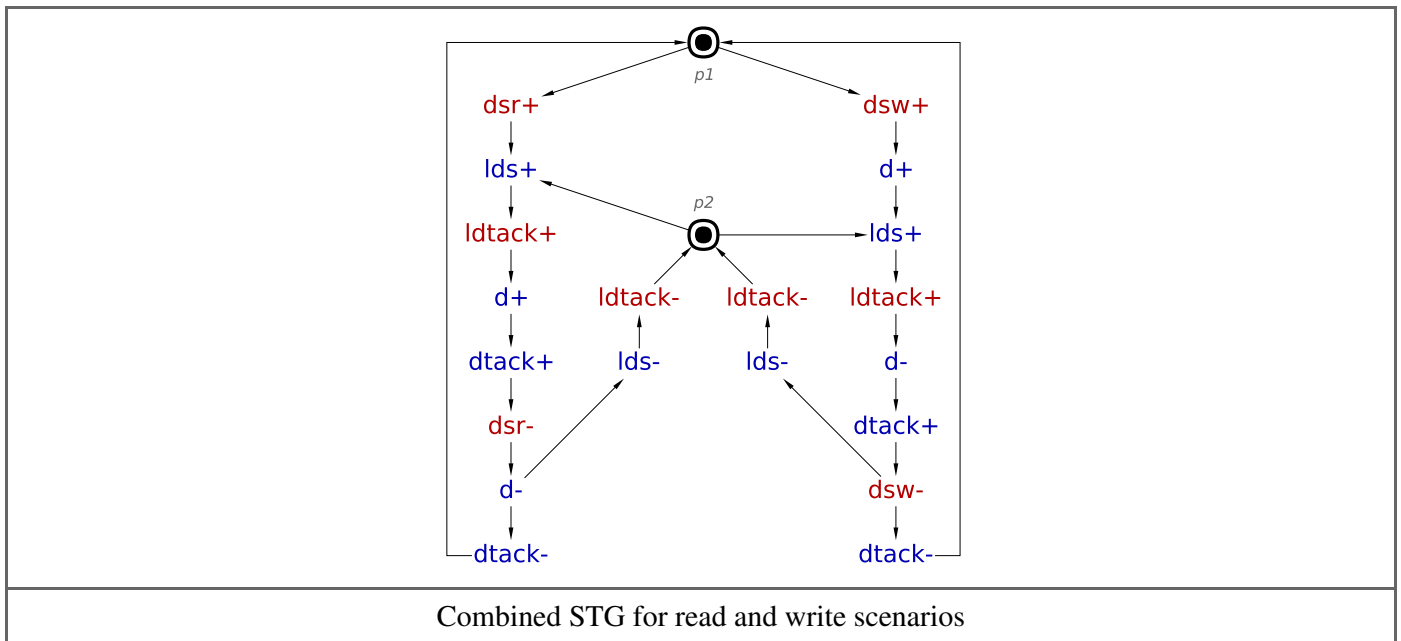


Note that place $p2$ is a *controlled choice* whose decision is determined by the *free choice* place $p1$.

Note the concurrency between the transitions resetting the device ($lds-$ and $ldtack-$) and the new requests from the bus ($dsr+$ and $dsw+$): A new request can arrive while the device is still resetting, thereby allowing concurrent operation of the bus and the device. This concurrency is the “meaning of life” of VME bus controller.


Optional simplification

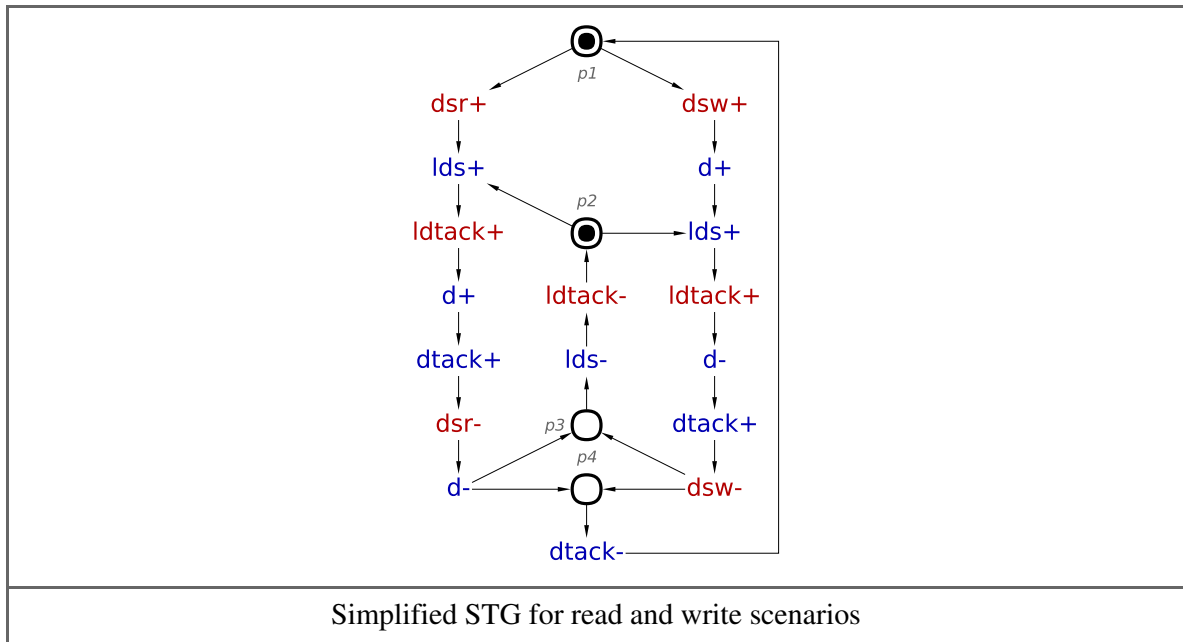Once the initially marked places are merged, one can notice that transitions **ldtack-**, **lds-** and **dtack-** occur in both branches of the choice and can be merged. Here is the simplified STG.



Validation and formal verification of the STG specification

Validation

Activate the **simulation tool**  and exercise the obtained STG model to better understand the behaviour of VME bus controller. Click one of the enabled signal transitions (they are highlighted in orange) to *fire* it. Note that the sequence of fired transitions is recorded in the simulation trace that is somewhat similar to the original timing diagram. Check that the simulation traces correspond to the intended behaviour of VME bus controller.

Formal verification

Verify that the STG specification satisfies the following properties using *Verification* menu:

- Deadlock freeness – every reachable marking enables at least one transition.
- Consistency – the '+' and '-' transitions of every signal alternate in every execution, always starting with the same sign.
- Input properness – an input cannot be disabled by an output or internal signal, and cannot be triggered by an internal signal.
- Output persistency – an enabled output or internal signal cannot be disabled by any other signal.

These are basic soundness properties which should be satisfied by most models – *Verification* menu has an entry that can check all these properties with a single click.


Now check whether the STG satisfies the *Complete State Coding (CSC)* property using *Verification* → *Complete State Coding (all cores) [MPSat]* menu item. This STG does not have CSC, which means there are two reachable states that have the same value of all signals but enable different outputs. These states are said to be in *CSC conflict*.

Specifications with CSC conflicts cannot be directly implemented as circuits. One way of resolving CSC conflicts is to insert new **internal** signals into the STG. These internal signals add memory into the circuit helping it to trace the current state. More about CSC conflicts and resolving them can be found in [another tutorial](#).


Synthesis

Note that the synthesis solutions shown in this section are not unique and you may get a slightly different results.

 Resolve the CSC conflicts automatically using Petrifly via *Tools*→*Encoding conflicts*→*Resolve CSC conflicts [Petrify]* menu. Petrifly will insert a new internal signal `csc0` distinguishing between conflicting states. The result could look like the following STG:



 The obtained STG specification has CSC and can now be synthesised into an asynchronous circuit. A complex-gate solution obtained via *Synthesis*→*Complex gate [MPSat]* is as follows [circuit-vme-cg.work \(5.33 KiB\)](#):




This solution uses complex gates that do not usually exist in real gate libraries. Such gates need to be decomposed, so they can be *mapped* into the existing library gates – this is done by technology mapping. Note that speed-independence of the circuit must be preserved during decomposition.

The library of available gates can be passed to Workcraft in *SIS GenLib* format via *Digital circuit*→*Gate library for technology mapping* option in global settings (*Edit*→*Preferences...*). By default `libraries/workcraft.lib` is used. It defines a representative set of gates found in several modern gate libraries and also C-elements and uses a

generalised naming convention for gates and pins.

 The results of technology mapping into `libraries/workcraft.lib` gate library via *Synthesis*→*Technology mapping* [MPSat] is as follows [circuit-vme-tm.work \(9.3 KiB\)](#):



A circuit can be exported to Verilog via *File*→*Export...*→*.v* (*Workcraft Verilog serialiser*) menu. By default the produced Verilog uses the names of gates and pins as they are defined in the GenLib file. These names can be substituted by providing a conversion file in *Digital Circuit*→*Substitution rules for export* global preferences. For example, `libraries/workcraft-tsmc_ghp.cnv` file has rules to convert `libraries/workcraft.lib` gates to match the naming convention of TSMC GHP library.

Verification of the circuit implementation

Make sure that the original STG describing the contract with the environment and the circuit model is set up:

- In the circuit editor make sure that no components are selected (click on the editor canvas).
- In the property editor the *Environment URI* property should point to the work file with the original STG

specification.

For circuits synthesised within Workcraft this property is automatically set up to the STG that was used for synthesis, i.e. in this case to the STG with internal signals inserted to resolve CSC conflicts. You should modify it to point to the original STG.

Use the *Verification* menu to verify that the circuit implementation is:

- deadlock-free;
- hazard-free;
- conforms to the original STG specification.


All these verification steps can be run via *Verification*→*Conformation, deadlock and hazard (reuse unfolding) [MPSat]* menu.

In theory, synthesised circuits are correct-by-construction. In practice, the synthesis tools are very complicated and may have bugs, so formally verifying the circuits is essential. This is especially true if the circuit was edited manually.

Initialisation


Initialisation (or reset) of a speed-independent circuit is a crucial part of the design process because a circuit can malfunction if its initial state is incorrect. There are several ways of circuit initialisation, that are usually used in combination:

- Rely on the initial state of the circuit inputs that propagate through the logic gates to initialise the internal and output signals.
- Substitute sequential gates with their set/reset counterparts that are initialised to 1/0 respectively.
- Insert additional gates to explicitly initialise the internal and output signals.

Use the *Initialisation analyser*  tool to decide how to properly reset the VME bus controller obtained by technology mapping.

The wires and pins whose initial state is guaranteed to be 0 or 1 are coloured **blue** or **red** respectively; initially *undefined* wires and pins are not coloured.

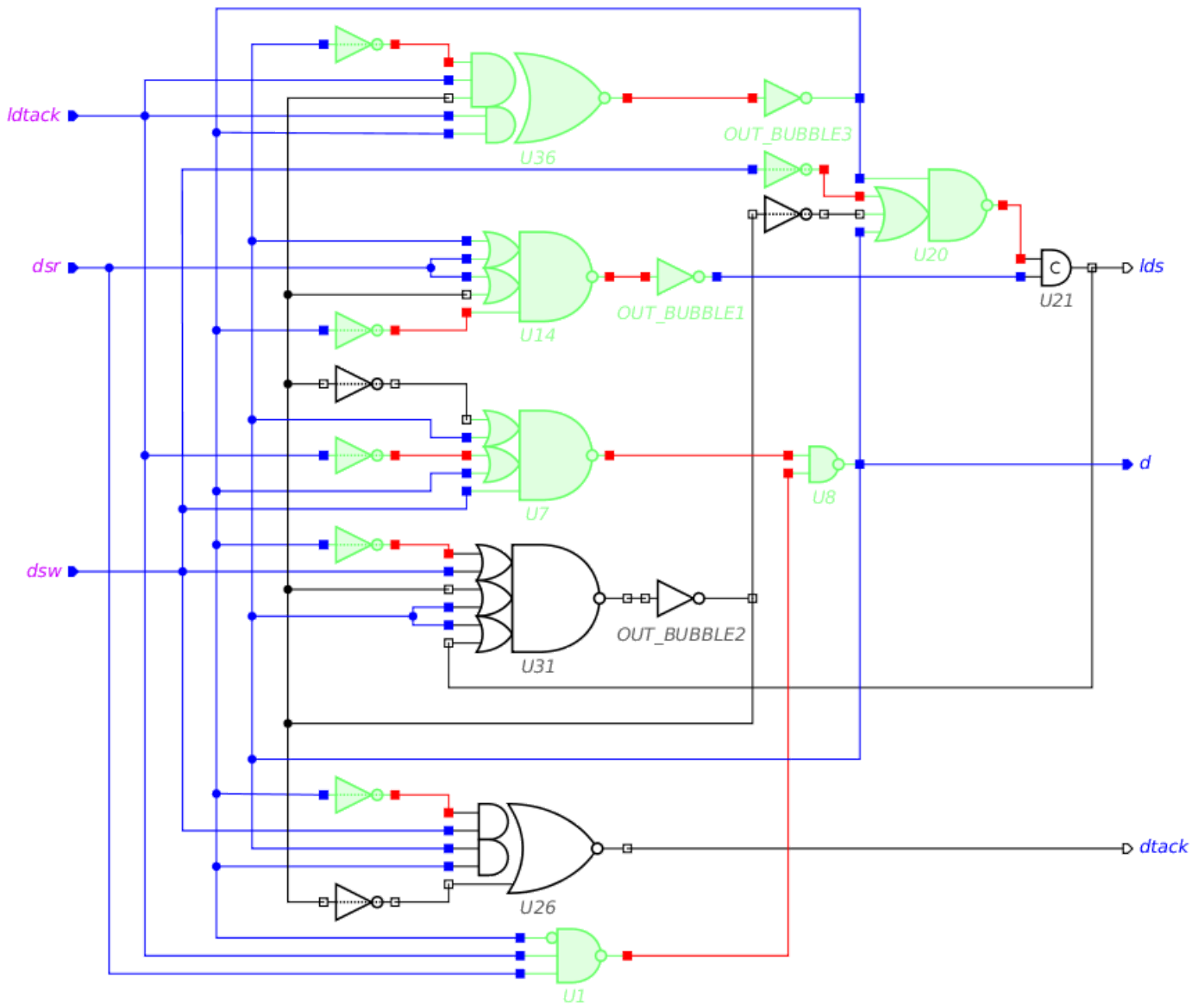Let us assume that the circuit inputs are guaranteed to be in a correct state (all zeros) by the environment – click on each input port to indicate this. Those gates that are initialised correctly through the primary inputs are highlighted **green**.



Now let us rely on C-element U21 being explicitly reset – click its output pin to indicate this. Notice that the output pin has a diamond shape now. This is to visualise the forced initialisation of the gate output (e.g. by replacing it by a C-element with explicit reset).

All the gates should be highlighted **green** now indicating that they are transitively initialised to the correct state.

If there were initialisation conflicts, the problematic gates would be highlighted in **orange**.