

# **Logic Decomposition of Asynchronous Circuits in WORKCRAFT**


**Victor Khomenko, Danil Sokolov, Alex Yakovlev**

# Motivation

- **Logic decomposition** is one of the most difficult tasks in the design flow
- Much more difficult than for synchronous circuits – no guarantee of success
- The quality of the resulting circuit (in terms of area and latency) depends to a large extent on the way logic decomposition was performed


 
# Speed-independency assumptions

- Gates are *atomic* (so no internal hazards)





- Gates' delays are positive and unbounded (and perhaps variable)
- Wire delays are negligible (SI) or, alternatively, wire forks are isochronic (QDI)

# Speed-independent decomposition

  


# VME Bus Controller

 
 




# Naïve decomposition is hazardous


 


# Decompose at the level of STG

  



# Latch utilisation

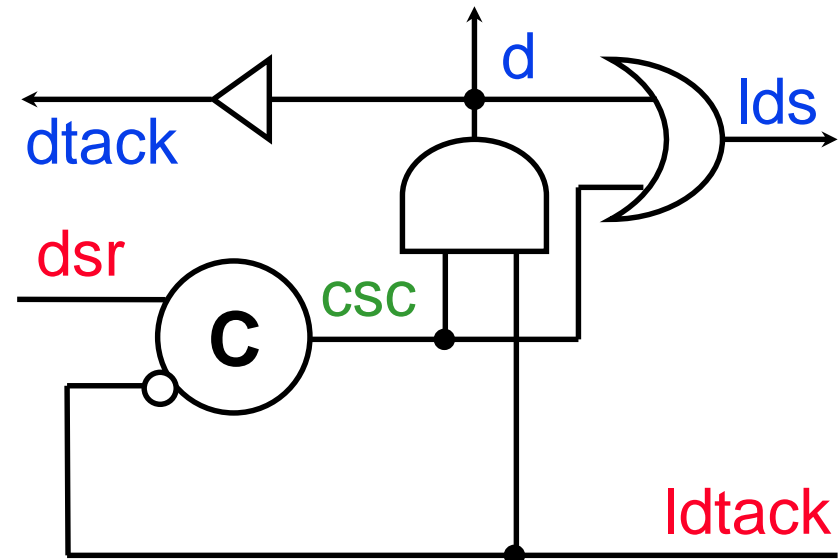 

Only possible because there is no globally reachable state at which  $dsr=ldtack=0$  and  $csc=1$


# Logic decomposition algorithm

- **Synthesise the circuit from the STG (several complex-gate and standard-C implementations are considered for each signal)**
- **Heuristically select a non-mappable gate, and a decomposition of this gate**
- **Insert a new signal into the STG for the sub-function in the selected decomposition**
- **Repeat the above steps until all gates are mappable or no further progress is possible**


# Function-guided signal insertion

**Problem:** given a Boolean function  $F$ , insert a new signal  $dec$  (i.e. a set of new transitions labelled  $dec+$  or  $dec-$ ) with the implementation  $[dec]=F$  into the STG


# Transition insertions

 

**Sequential pre-insertion**

 


**Sequential post-insertion**

 

**Concurrent insertion**



# Generalised transition insertion

 

Sources and destinations are **locked**

# Cost function

Parameterised by the user; takes into account:

- the delay introduced by the insertion
- the number of syntactic triggers of all non-input signals
- the number of inserted transitions of a signal
- the number of signals which are not **locked** with the newly inserted signal
- ...

# Overcoming mapping failure


- Logic decomposition is **not guaranteed to succeed**, so tools occasionally fail
- May need to help the tools:
  - methods & tricks
  - “think outside the box” – knowledge of the environment, capacity to redesign the system and its environment
  - “high-level understanding of the design” – knowing the causal dependencies between the signals, which environment signals are fast/slow (useful for concurrency reduction), etc.
  - relative timing assumptions



# 0 Prevention is better than cure

- **Large monolithic STGs are difficult, both for humans and for tools**
- **Hierarchical design:**
  - **architectural decomposition into modules**
  - **... until each module is small, say ~10 signals (this size is about right for humans\* and tools)**
  - **Advantages: human- and tool-friendly, more predictable, module re-use (within and between designs), easy to document and maintain, etc.**
- **Workcraft has support for hierarchical designs**

# Example: stage of multiphase buck

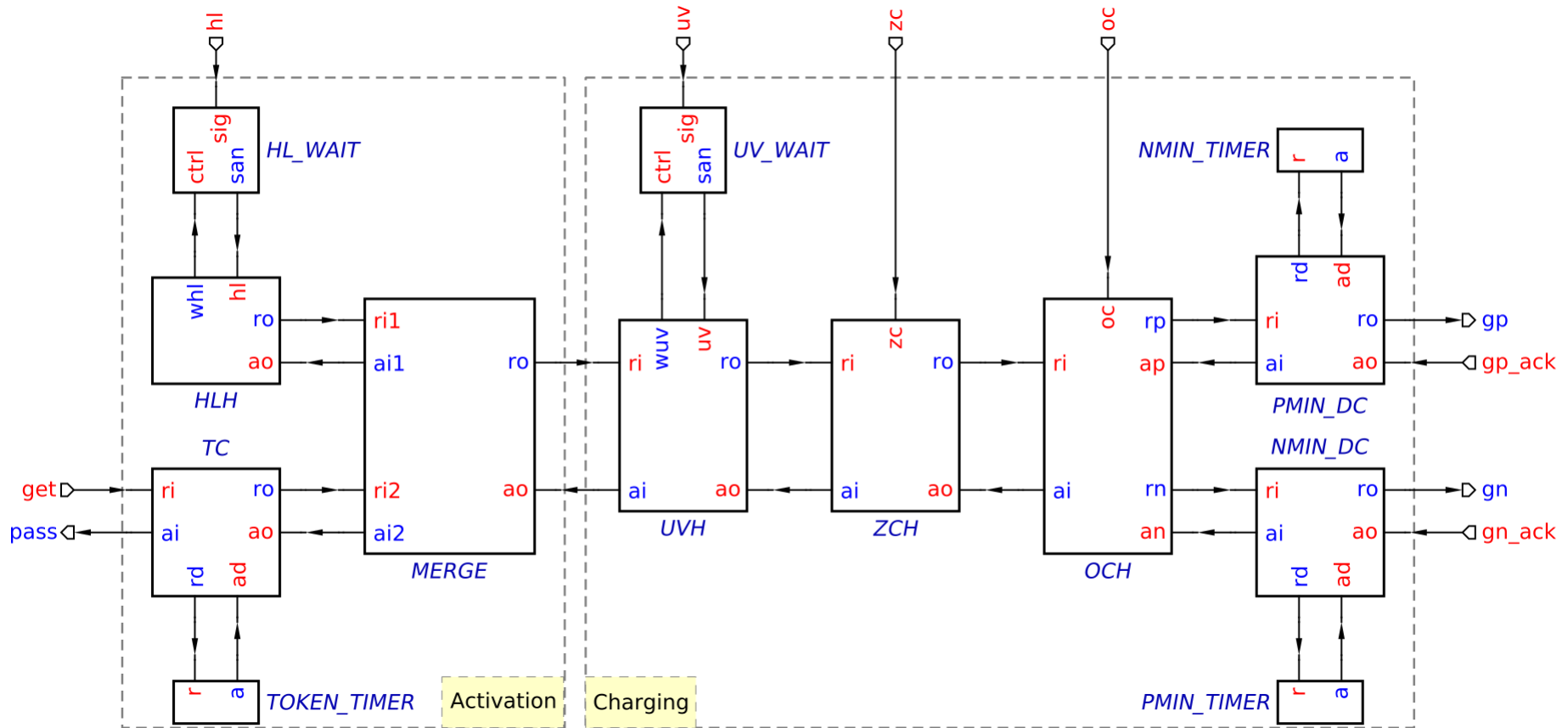



# 1 Expanding gate library

- Add a missing gate to the library
- Usually not an option 😞

# 2 Inserting a useful signal

- Tools often fail because:
  - some heuristic selects a bad sub-function
  - there is no **structural** signal insertion to implement a useful sub-function
- One can help the tool by inserting an internal signal implementing a useful sub-function



# Example: OR5

  

# 3.1 Simplifying the STG structure

- **If the STG has complicated structure, it may be impossible to insert a signal structurally (e.g. one would have to merge and then split some choice branches for that)**
- **Try to simplify the STG structure by reducing the number of choice and merge (i.e. explicit) places, in particular controlled choices can often be removed**

# Example: OR5

  

## 3.2 STG re-synthesis



- **Re-synthesis builds the state graph and then derives an equivalent STG from it, often with simpler structure**
- **Fully automatic, so easy to try if technology mapping fails**
- **Try various command-line options**





# 4 Concurrency reduction

- **CR does not necessarily decrease performance – though events are less concurrent, the gates become smaller and some internal signals may become unnecessary**
- **CR may change the contract with the environment and introduce a deadlock or global deterioration of performance that is difficult to debug**



# Example: xyz

  

# Example: xyz with CR

  


# Example: xyz with more CR

  

# 5 Relative timing assumptions

- Occasionally, the described techniques still fail to yield a solution
- Breaking up a large gate yields a non-speed-independent decomposition
- The correct operation can then be ensured by relative timing assumptions
- This has implications for place&route
- **Easy to make a mistake, need tool support**

# Example: VME read phase

 

$$\text{MaxDelay}(x-) < \text{MinDelay}(d- \rightarrow lds-)$$
$$\text{MaxDelay}(x-) < \text{MinDelay}(d- \rightarrow dtack- \rightarrow dsr+)$$

Thank you!  
Any questions?