



Asynchronous Design: Introduction to Principles and Models

Alex Yakovlev

Newcastle University

Newcastle upon Tyne, U.K.

Outline

- **Six Asynchronous Design Principles:**
 - **Asynchronous Handshaking**
 - **Delay-insensitive Encoding**
 - **Completion Detection**
 - **Causal Acknowledgement**
 - **Full Indication and Early Evaluation**
 - **Time Comparison**
- **Pros and Cons**
- **(Some of the) Models, Techniques and Tools for Asynchronous Design**
- **Asynchronous control logic synthesis from Signal Transition Graphs**
- **Why is Async good for Analog Mixed Signal?**


Asynchronous Behaviour

- **Synchronous vs Asynchronous behaviour in general terms, examples:**
 - **Orchestra playing with vs without a conductor**
 - **Party of people having a set menu vs a la carte**
- **Synchronous means all parts of the system acting globally in tact, even if some or all part ‘do nothing’**
- **Asynchronous means parts of the system act on demand rather than on global clock tick**
- **Acting in computation and communication is, generally, changing the system state**
- **Synchrony and Asynchrony can be in found in CPUs, Memory, Communications, SoCs, NoCs etc.**

Key Principles of Asynchronous Design

- **Asynchronous handshaking**
- **Delay-insensitive encoding**
- **Completion detection**
- **Causal acknowledgment (aka indication or indicatability)**
- **Strong and weak causality (full indication and early evaluation)**
- **“Time comparison” (synchronisation, arbitration)**


Why and what is handshaking?

 

Mutual Synchronisation is via Handshake


Synchronous clocking

How we think

 


(a)

What we design

 


(b)

Asynchronous handshaking

 


What we design

 

(c)

How we think

 

"Channel" or "Link"


Handshake CL

Handshake latch


(d)

Handshake Signalling Protocols


Level Signalling (RTZ or 4-phase)

 


(a)

 

Transition Signalling (NRZ or 2-phase)

 


 Why and what is delay-insensitive coding?




Data Token = (Data Value, Validity Flag)


Bundled Data

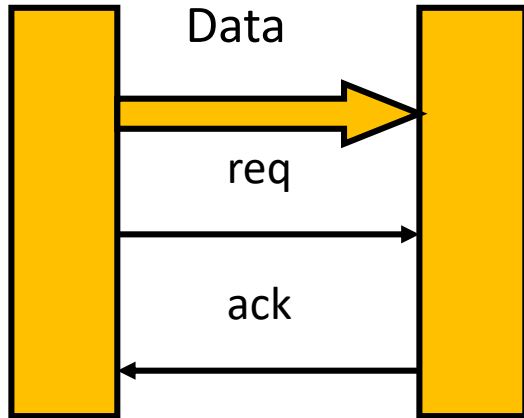


Return to Zero:

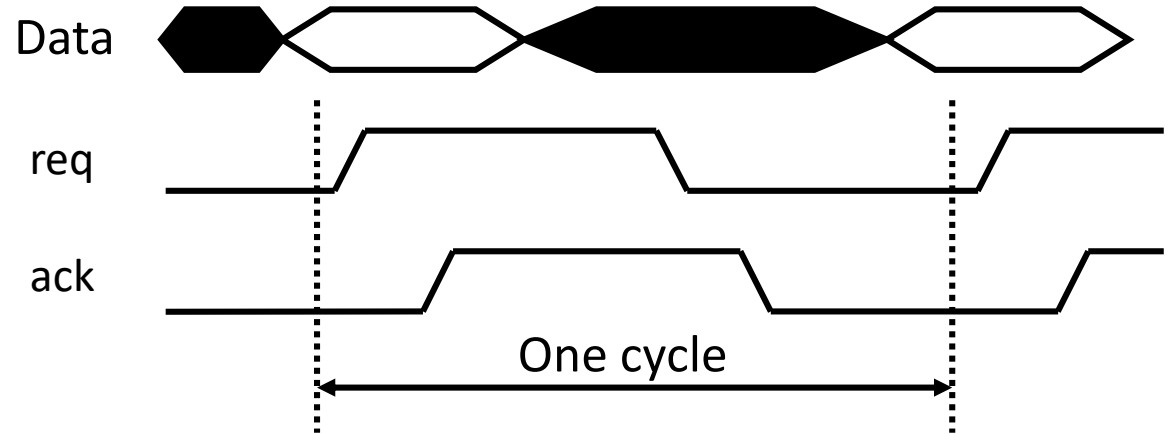


Non-Return-to-Zero

 


DI encoded data (Dual-Rail)

 

RTZ:

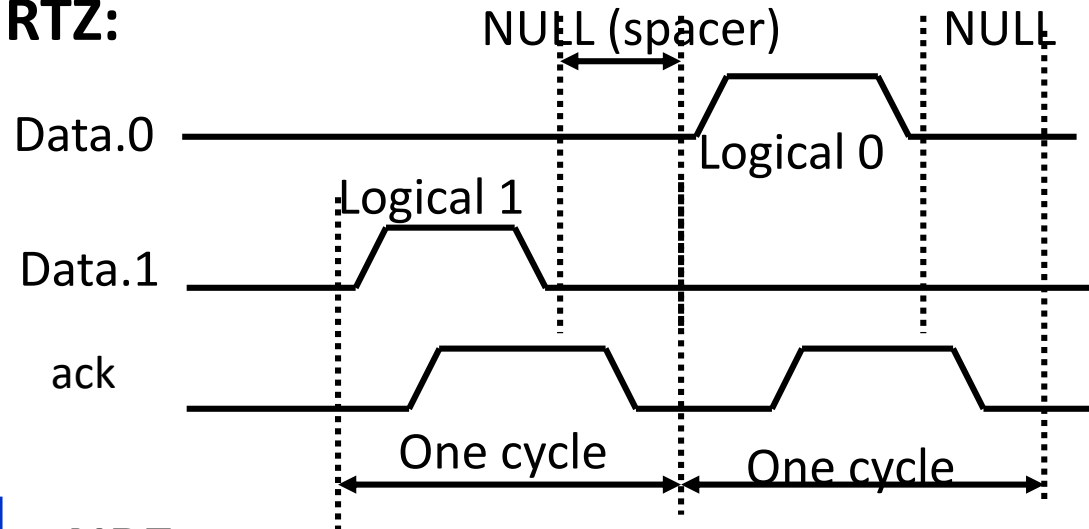

NRZ:

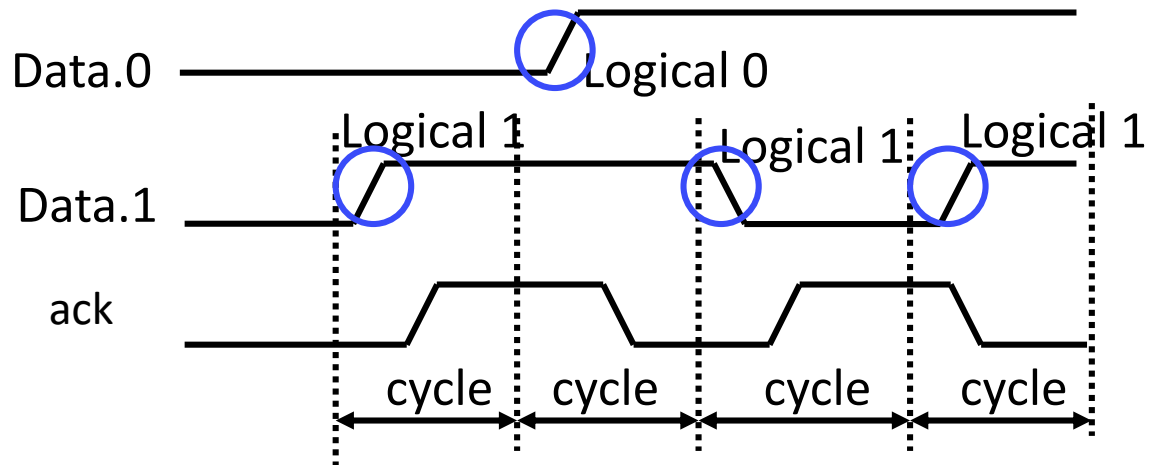


NRZ coding leads to complex logic implementation; special ways to track odd and even phases and logic values are needed, such as LEDR

DI codes (1-of-n and m-of-n)


- **1-of-4:**
 - **0001=> 00, 0010=>01, 0100=>10, 1000=>11**
- **2-of-4:**
 - **1100, 1010, 1001, 0110, 0101, 0011 – total 6 combinations (cf. 2-bit dual-rail – 4 comb.)**
- **3-of-6:**
 - **111000, 110100, ..., 000111 – total 20 combinations (can encode 4 bits + 4 control tokens)**
- **2-of-7:**
 - **1100000, 1010000, ..., 0000011 – total 21 combinations (4 bits + 5 control tokens)**

Why and what is completion detection?

 

Signalling that the Transients are over

Bundled-data logic blocks

 


Completion
is implicit:
by done
signal


The delay must
scale with the worst
case delay path,
So ... not really self-
timed

Conventional logic + matched delay


True completion detection

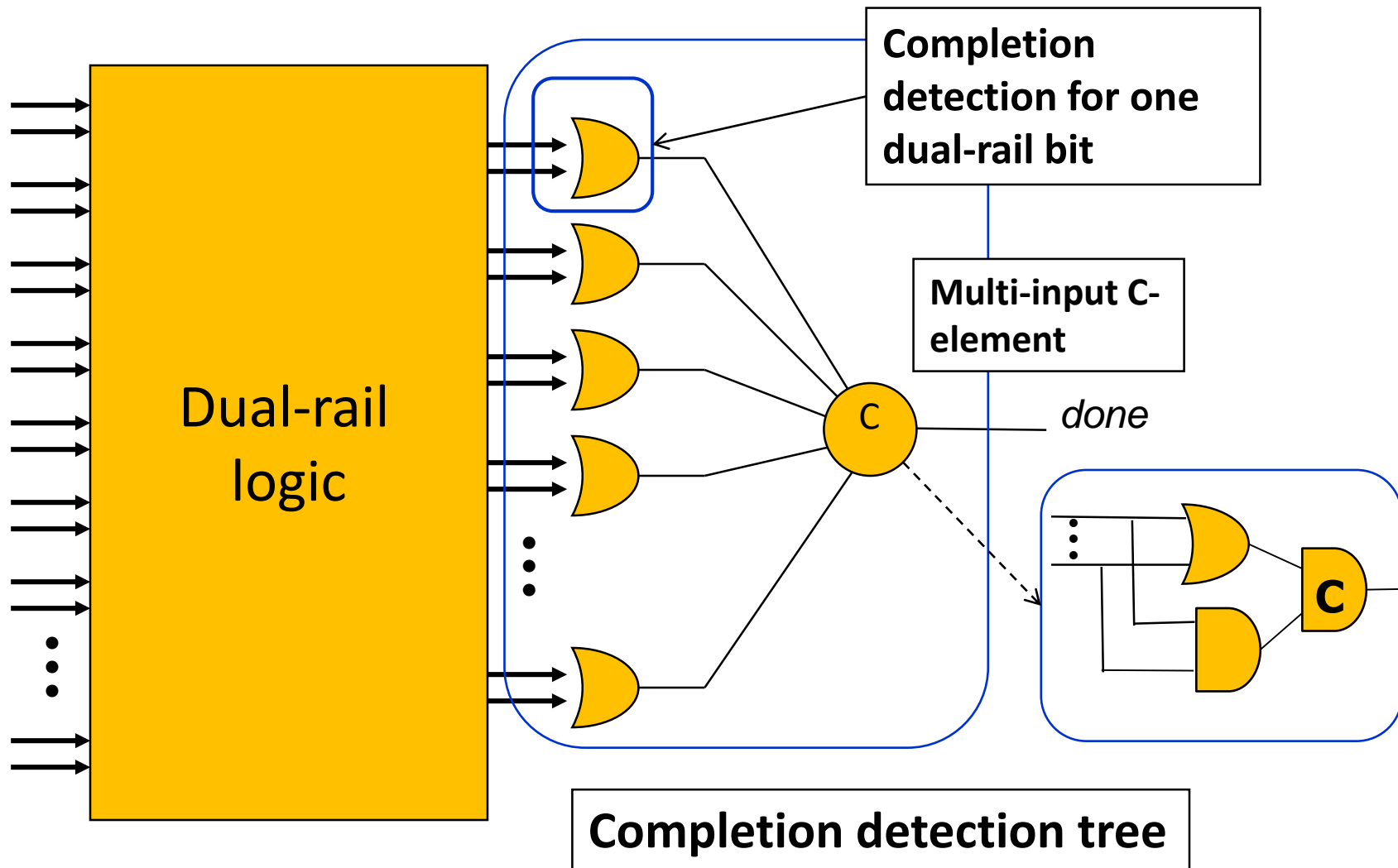



The Muller C element

 

A	B	Z ⁺
0	0	0
0	1	Z
1	0	Z
1	1	1

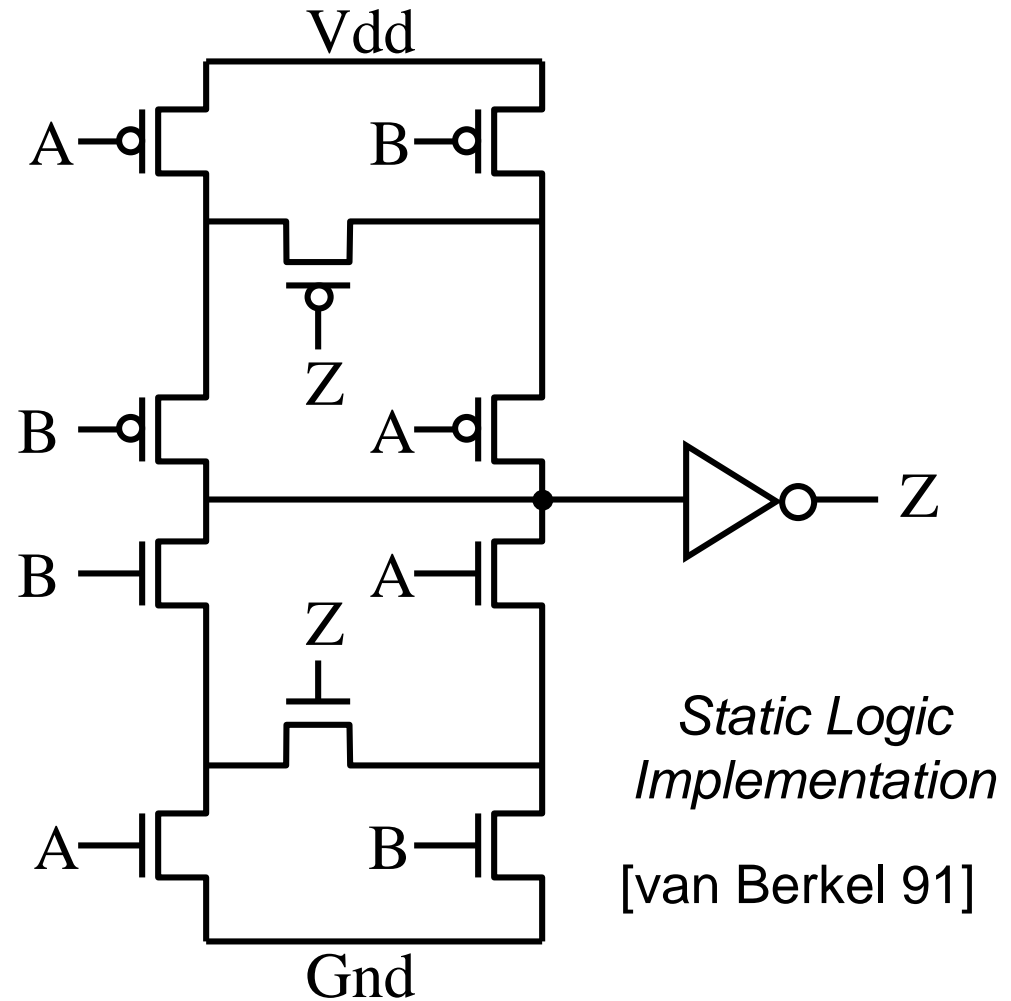

C-element: Other implementations

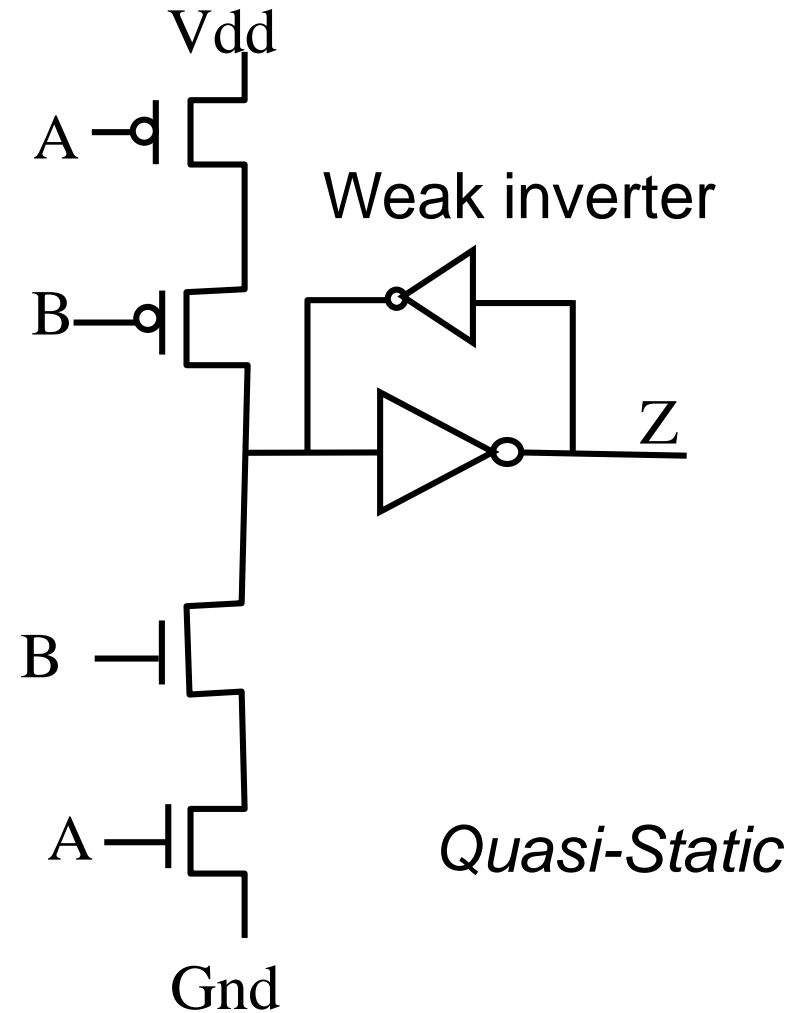
 


Why and what is causal acknowledgment?




**Every signal event must be acknowledged
by another event**

Causal acknowledgment

 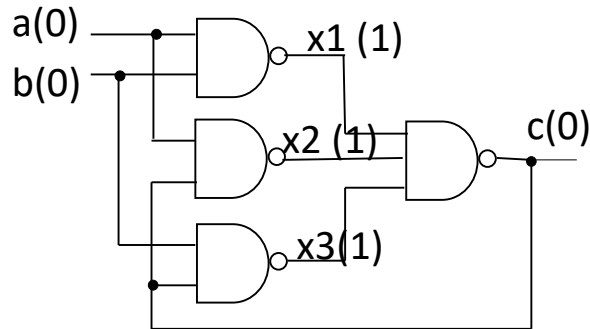


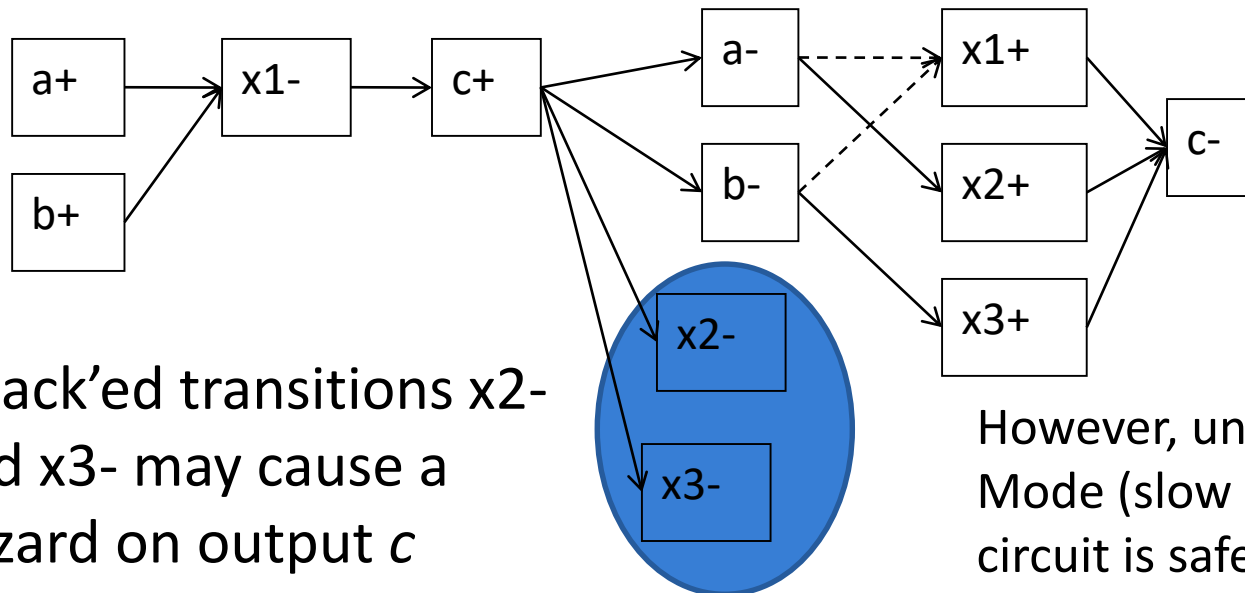
C-element implementation using simple gates





Unack'ed transitions $x2-$ and $x3-$ may cause a hazard on output c

However, under Fundamental Mode (slow environment) the circuit is safe

Principle of causal acknowledgement

  


  C-element implementation using simple gates



Each transition is causally ack'ed, hence no hazards can appear

 
Why and what are strong and weak causality ?




Degree of necessity of precedence of some events for other events

Strong Causality

 - Petri net transitions synchronising as rendez-vous



 
- Logic circuits: Muller C-element (in 0-1 and 1-0 transitions), AND gate (in 0-1 transitions), OR gate (in 1-0 transitions)




A	B	C ⁺
0	0	0
0	1	C
1	0	C
1	1	1

Weak Causality

 
- Petri net transitions communicating via places



 
- Logic circuits: AND gate (in 1-0 transitions), OR gate (in 0-1 transitions)



Full indication versus Early Evaluation

 

 Dual-rail AND gate
with full input
acknowledgement



Dual-rail AND gate
with “early propagation”

Allows outputs to be produced from NULL to Codeword only when some (required) inputs have transitioned from NULL to Codeword (similar for Codeword to NULL)

Why and what is timing comparison?




Telling if some event happened before another event

Synchronizers and arbiters


- Synchronizer

 Decides which clock cycle to use for the input data




- Asynchronous arbiter


Decides the order of inputs

 

Metastability is....

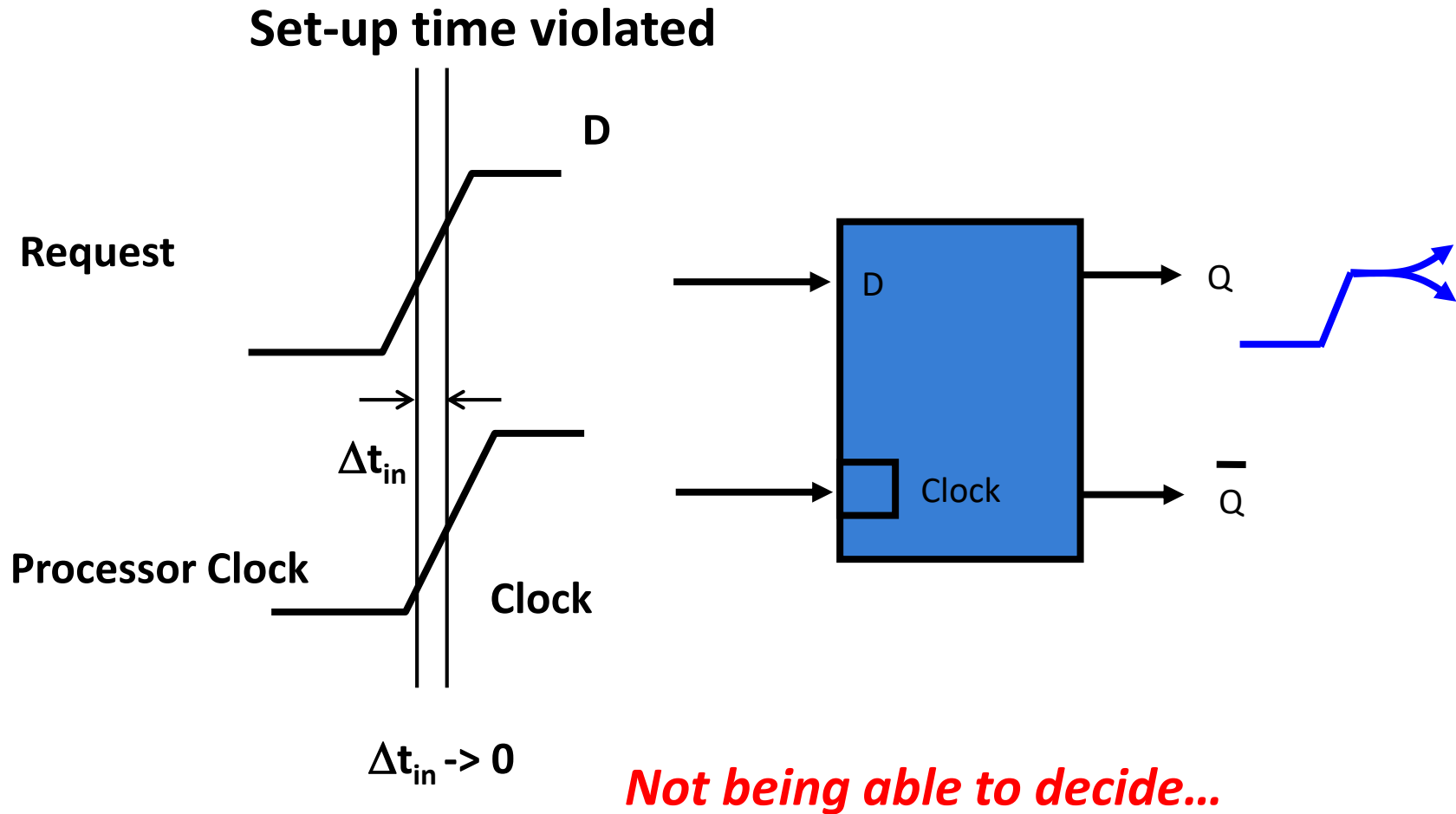


Typical responses

 

- We assume all starting points are equally probable
- Most are a long way from the “balance point”
- A few are very close and take a long time to resolve

Synchronizer


- t is time allowed for the Q to change between CLK a and CLK b
- τ is the recovery time constant, usually the gain-bandwidth of the circuit
- T_w is the “metastability window” (aperture around clock edge in which the capture of data edge causes a delay that is greater than normal propagation delay of the FF)
- τ and T_w depend on the circuit
- We assume that all values of Δt_{in} are equally probable

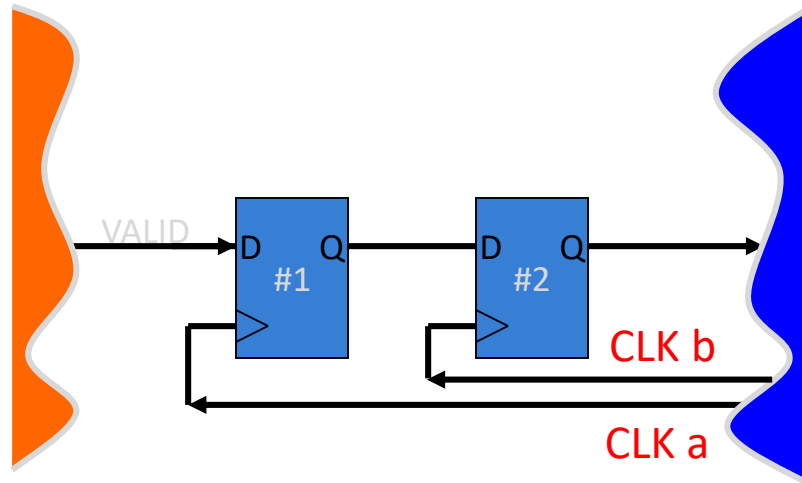

$$MTBF = \frac{e^{t/\tau}}{T_w \cdot f_c \cdot f_d}$$

Two-way arbiter (Mutual exclusion element)

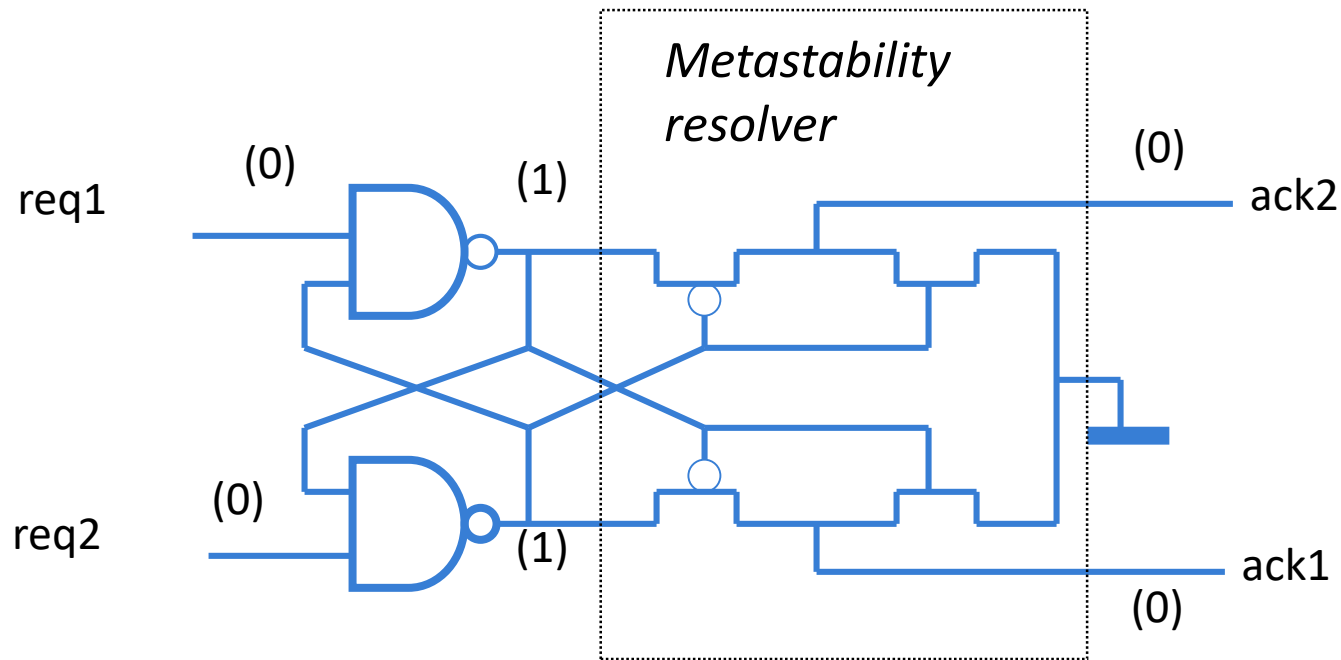Basic arbitration element: Mutex (due to Seitz, 1979)



An asynchronous data latch with metastability resolver can be built similarly

Importance of Timing Comparison

- **Understanding metastability is becoming very important as analogue and digital domains get closer, and timing uncertainty and PVT variations increase**
- **Arbitration and synchronization are increasing their importance due to many-core, timing domains, NoCs, GALS**
- **Design automation for metastability and synchronization is turning from research to practice (Blendix)**



Pros...

- People have always been excited by asynchronous design, and motivated by:
 - **Higher performance** (work on average not worst case delays)
 - **Lower power consumption** (automatic fine-grain “clock” gating; automatic instantaneous stand-by at arbitrary granularity in time and function; distributed localized control; more architectural options/freedom; more freedom to scale the supply voltage)
 - **Modularity** (Timing is at interfaces)
 - **Lower EMI and smoother I_{dd}** (the local “clocks” tend to tick at random points in time)
 - **Low sensitivity to PVT variations** (timing based on matched delays or even *delay insensitive*)
 - **Secure chips** (white noise current spectrum)
 - **Plus, ... a lot of scope and fun for research (there are many unexplored paths in this forest!)**

... Cons

- So why have async designers been often “crucified” in the past?
 - **Overhead** (area, speed, power)
 - Control and handshaking
 - Dual-rail and completion detection costs
 - **Hard to design**
 - yes and no, ... It’s different – **there are very many styles and variants to go and one can easily get confused which is better**
 - **Very few **practical** CAD tools** (but many academic tools)
 - Tools are quite specific to particular design styles and design niches; hence don’ t cover the whole spectrum
 - Complexity of timing and performance models
 - Difficulty with sign-off (for particular frequency requirements)
 - ... But the situation is improving
 - **Hard to Test**
 - Possible, but not as mature as sync

Models and techniques for design

  


Models and techniques for asynchronous design


- **Models:**
 - Delay model (inertial, pure, gate delay, wire delay, bounded and unbounded delays)
 - Models of environment (fundamental mode, input-output)
 - Models of switching behaviour (state-based, event-based, hybrid)
- **RTL level:**
 - Data and control paths separate (data flow graphs, FSMs, Signal Transition Graphs, Synchronised Transitions)
 - Pipeline based (Combinational logic plus registers and latch controllers, e.g. micropipelines, gate-level pipelining)
 - Process-based (CSP-like, Balsa, Haste, Communicating Hardware Processes)
- **High-level models**
 - Flow graphs (Marked graphs, extended MGs), Petri nets, Markov Chains
 - Behavioural HDLs (C, SystemC)

Gate vs wire delay models

 - **Gate delay model: delays in gates, no delays in wires**




 - **Wire delay model: delays in gates and wires**



Delay models for async. circuits

- **Bounded delays (BD)**: realistic for gates and wires.
 - Technology mapping is easy, verification is difficult
- **Speed independent (SI)**: Unbounded (pessimistic) delays for gates and “negligible” (optimistic) delays for wires.
 - Technology mapping is more difficult, verification is easy
- **Delay insensitive (DI)**: Unbounded (pessimistic) delays for gates and wires.
 - DI class (built out of basic gates) is almost empty
- **Quasi-delay insensitive (QDI)**: Delay insensitive except for critical wire forks (*isochronic forks*).
 - In practice it is the same as speed independent

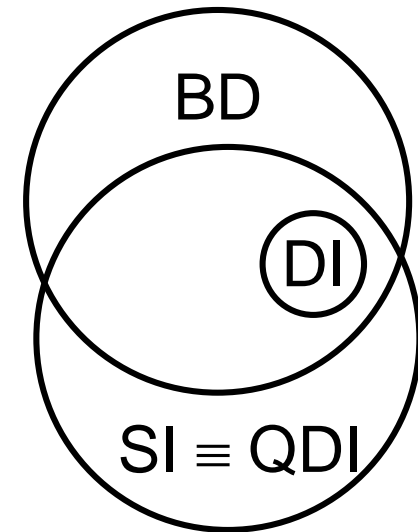


Control Logic


- **Control specification based on Petri nets (Signal Transition graphs)**

Control specification



Signal Transition Graph
(STG)

 



Timing Diagram

 



Control specification

  



Control specification

  



Control specification

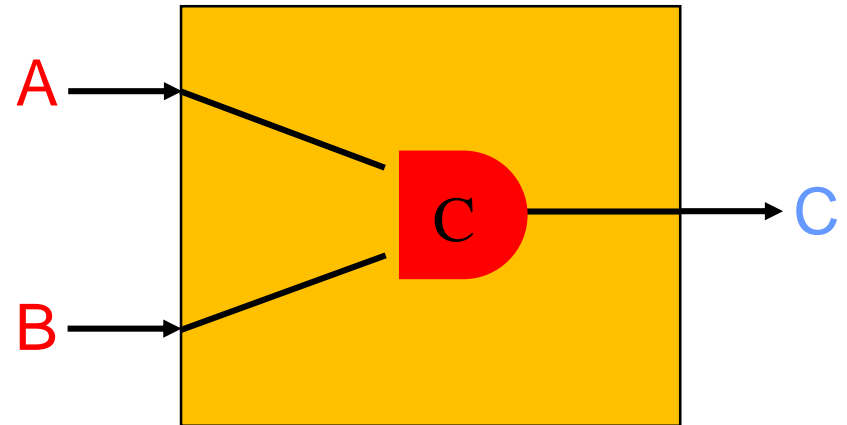 

Control specification

 
 


VME bus example using Petri nets

 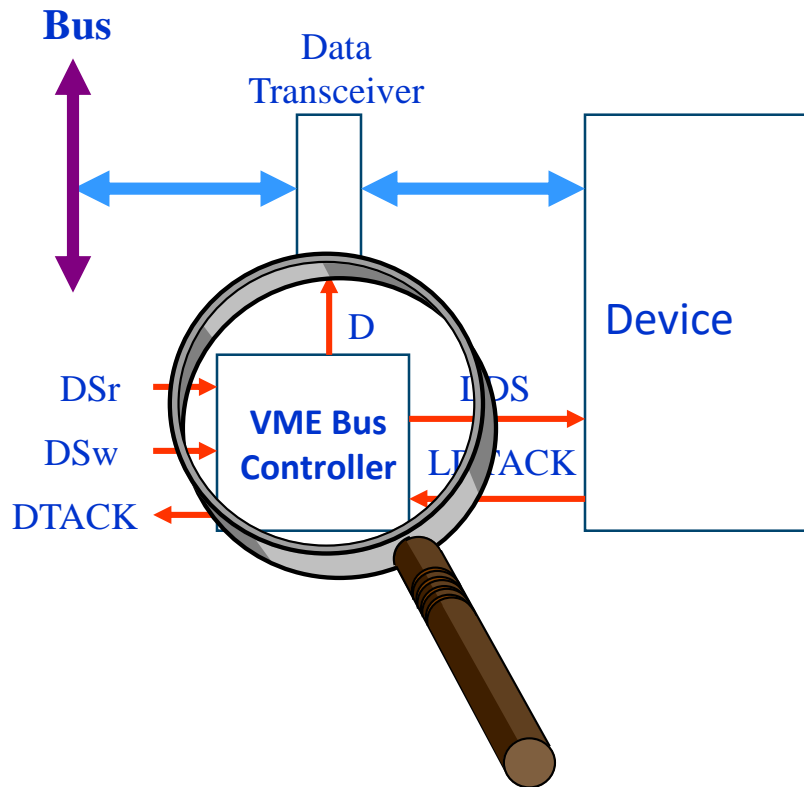


Read Cycle


STG for the READ cycle

 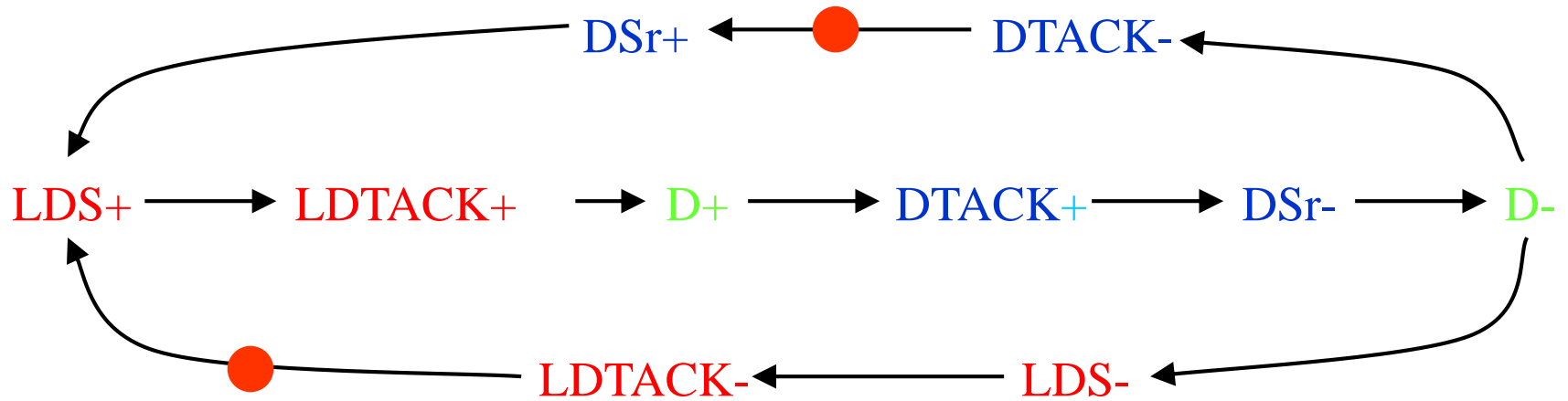

Choice: Read and Write cycles

 

Choice: Read and Write cycles

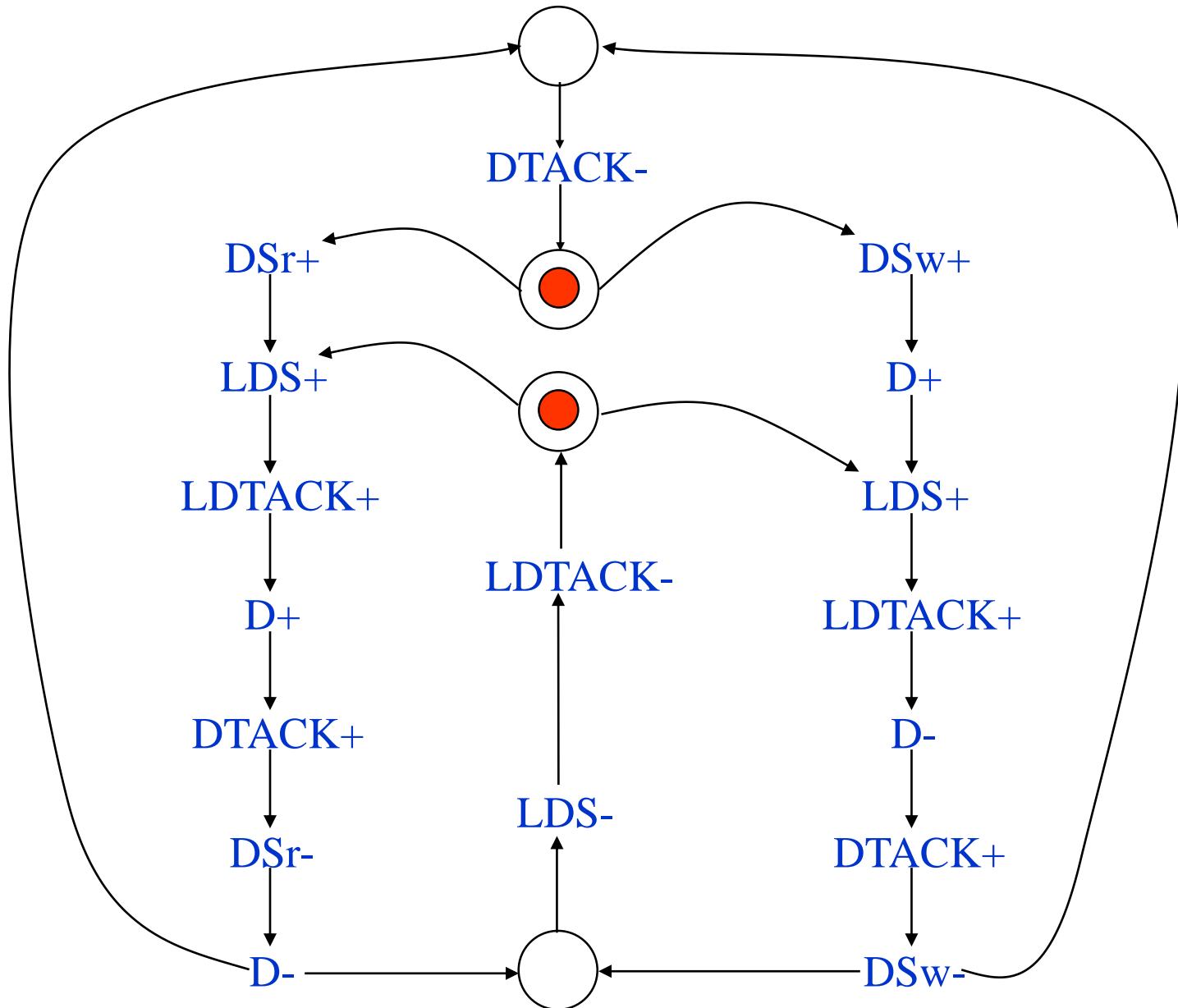

Workcraft tool: workcraft.org

- **Framework for interpreted graph models**
 - **Circuits, STGs, state graphs, dataflow structures, ...**
 - **Interoperability between different abstraction levels**
 - **Consistency for users; convenience for developers**
- **Elaborate graphical user interface**
 - **Visual editing, analysis, and simulation**
 - **Easy access to common operations**
 - **Possibility to script specialised actions**
- **Interface to back-end tools for synthesis and verification**
 - **Reuse of established theory and tools (PETRIFY , MPSAT , PUNF)**

Synthesis & verification of async circuits

The screenshot shows the Workcraft software interface. The main window displays the State Transition Graph (STG) for 'buck.stg' and the logic circuit for 'buck.circuit'. The STG shows a sequence of events: $uv+$, $gn-$, gn_ack- , $gp+$, gp_ack+ , $uv-$, $oc+$, $gp-$, gp_ack- , $gn+$, gn_ack+ , $oc-$. The circuit diagram shows the implementation of these events using logic gates and a flip-flop (C).

Verification results

Under the given environment (buck.stg.work) the circuit is:




- * conformant
- * deadlock-free
- * hazard-free

OK

Some references



- **General Async Design:** J. Sparsø and S.B. Furber, editors. *Principles of Asynchronous Circuit Design*, Kluwer Academic Publishers, 2001. (electronic version of a tutorial based on this book can be found on:
http://www2.imm.dtu.dk/pubdb/views/edoc_download.php/855/pdf/imm855.pdf)
- **Async Control Synthesis:** J. Cortadella, M. Kishinevsky, A. Kondratyev, L. Lavagno, and A. Yakovlev. *Logic Synthesis of Asynchronous Controllers and Interfaces*. Springer-Verlag, 2002. (Petrify software can be downloaded from: <http://www.lsi.upc.edu/~jordicf/petrify/>)
- **Arbiters and Synchronizers:** D.J. Kinniment, *Synchronization and Arbitration in Digital Systems*, Wiley and Sons, 2007 (a tutorial on arbitration and synchronization from ASYNC/NOCS 2008 can be found: <http://async.org.uk/async2008/async-nocs-slides/Tutorial-Monday/Kinniment-ASYNC-2008-Tutorial.pdf>)
- **Asynchronous on-chip interconnect:** John Bainbridge, *Asynchronous System-on-Chip Interconnect*, BCS Distinguished Dissertations, Springer-Verlag, 2002 (electronic version of the PhD thesis can be found on: http://intranet.cs.man.ac.uk/apt/publications/thesis/bainbridge00_phd.php)

Logic synthesis: xyz-example

  
 


Signal Transition Graph (STG)

Token flow

  

State graph

  


Next-state functions

$$x = \bar{z} \cdot (x + \bar{y})$$

$$y = z + x$$

$$z = x + \bar{y} \cdot z$$

 

Deriving next state functions

1) Truth Table

Previous state	Next State
0*0 0	1 0 0
1 0*0*	1 1 1
0 1*0	0 0 0
1 1 0*	1 1 1
0 0*1	0 1 1
1*0*1	0 1 1
0 1 1*	0 1 0
1*1 1	0 1 1

2) Boolean Minimization

xy	00	10	11	01
z				
0	1	1	1	0
1	0	0	0	0

$$x = \bar{z} \cdot (x + \bar{y})$$

Observations in this example:

- 1) All combinations are used as states
- 2) All states appear uniquely


Generally, this is not always the case!

Complex Gate netlist

$$x = \bar{z} \cdot (x + \bar{y})$$

$$y = z + x$$

$$z = x + \bar{y} \cdot z$$

 

Circuit synthesis

- **Goal:**
 - **Derive a hazard-free circuit under a given delay model and mode of operation**

Speed independence

- **Delay model**
 - Unbounded gate / environment delays
 - Certain wire delays shorter than certain paths in the circuit
- **Conditions for implementability:**
 - Consistency
 - Complete State Coding
 - Persistency

Implementability conditions

- **Consistency**
 - Rising and falling transitions of each signal alternate in any trace
- **Complete state coding (CSC)**
 - Next-state functions correctly defined
- **Persistency**
 - No event can be disabled by another event (unless they are both inputs)

Implementability conditions




- **Consistency + CSC + persistency**



- **There exists a speed-independent circuit that implements the behavior of the STG**

(under the assumption that any Boolean function can be implemented with one complex gate)

Persistency

   


60

Speed independence \Rightarrow glitch-free output behavior under any delay

Why Async for Analog



Emergence of little digital electronics

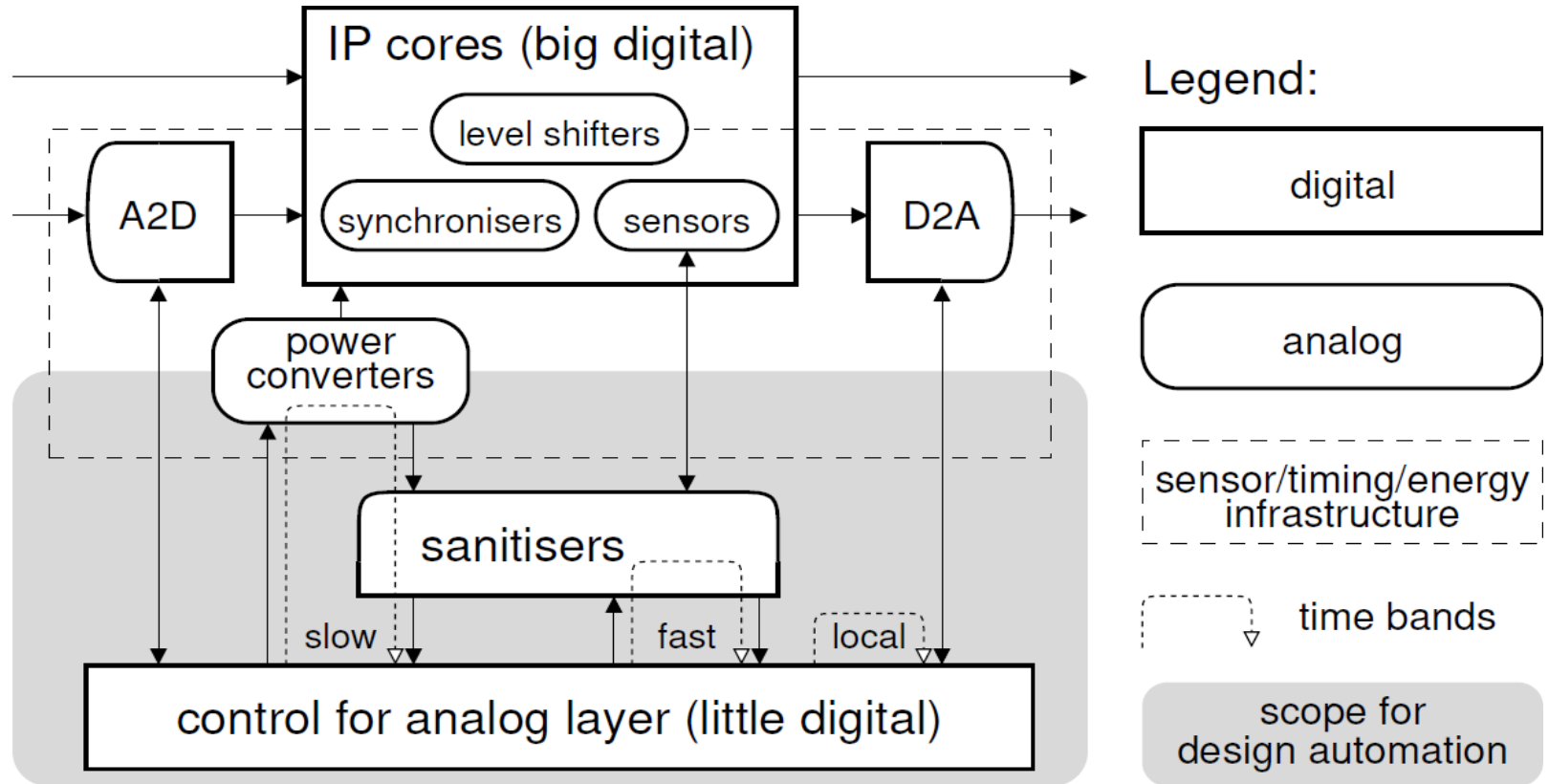


- Analog and digital electronics are becoming more intertwined
- Analog domain becomes complex and needs digital control


Motivation: power electronics context

- **Efficient implementation of power converters is paramount**
 - Extending battery life for mobile gadgets
 - Reducing energy bill for PCs and data centres (5% and 3% of global electricity production, respectively)
- **Need for responsive and reliable control circuits**
 - Millions of control decisions per second for years
 - A wrong decision may permanently damage the circuit
- **Need for EDA (*little digital vs big digital* design flow)**
 - RTL flow is optimised for sync data processing
 - *Ad hoc* async solutions are prone to errors and hard to verify


A4A design flow (supported by Workcraft)

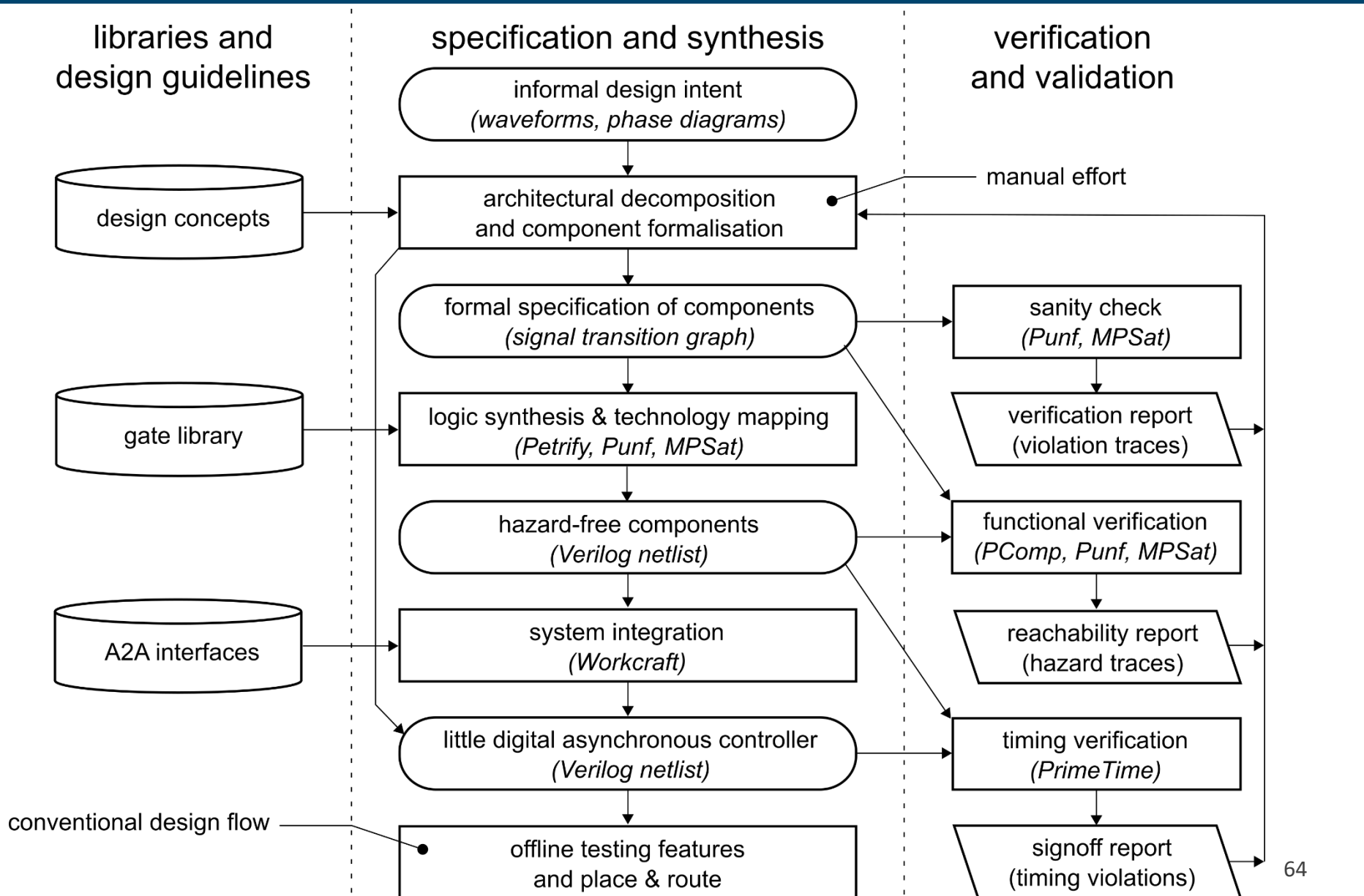

Case study: Multiphase buck

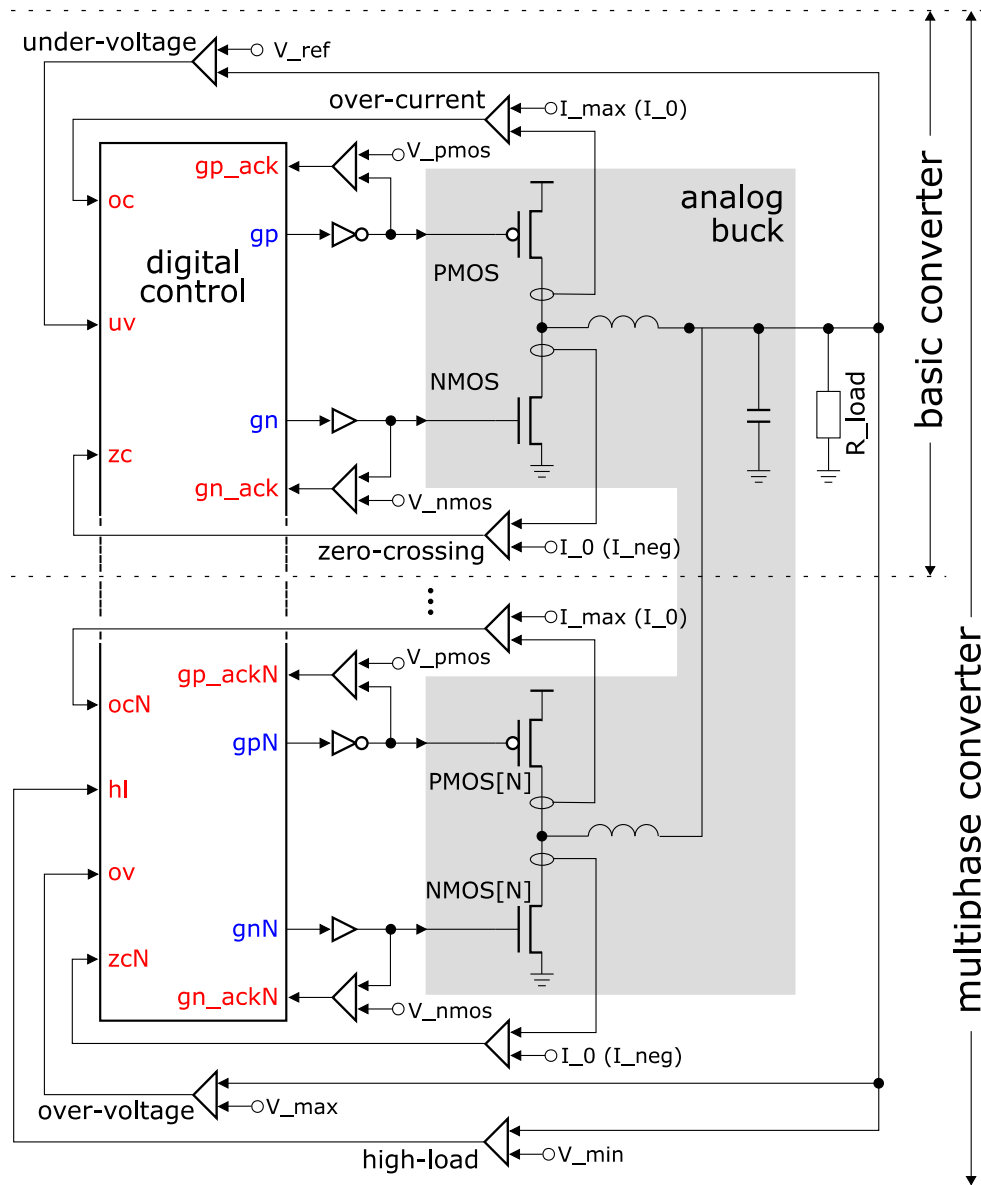


Multiphase Buck: Sync Control

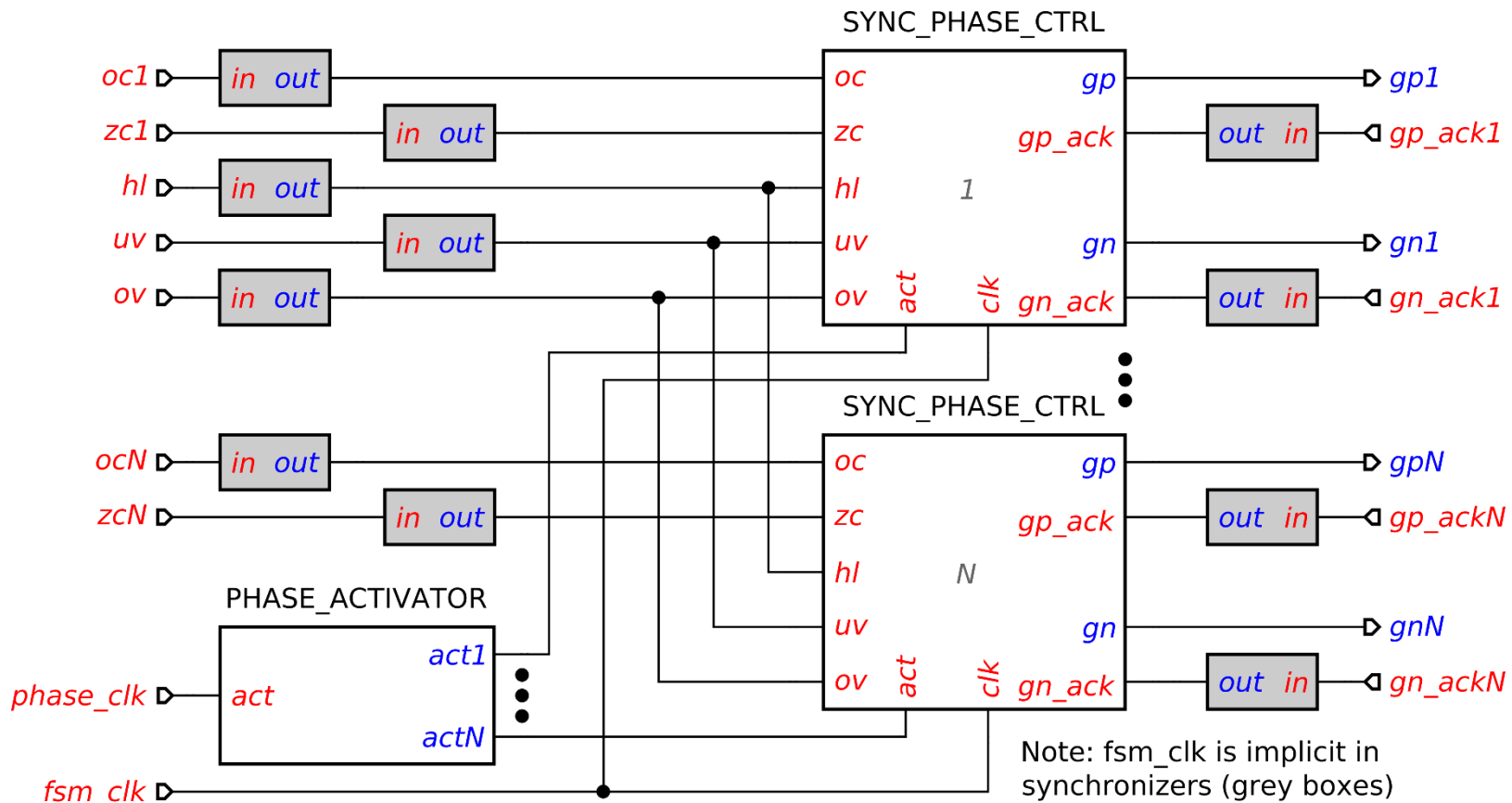

- Two clocks: phase activation (slow) and sampling (fast)
- Conventional RTL design flow
- Response time is of order of clock periods
- Need for multiple synchronizers (grey boxes) – latency, metastability
- Power consumed even when idle


Multiphase Buck: Async Control

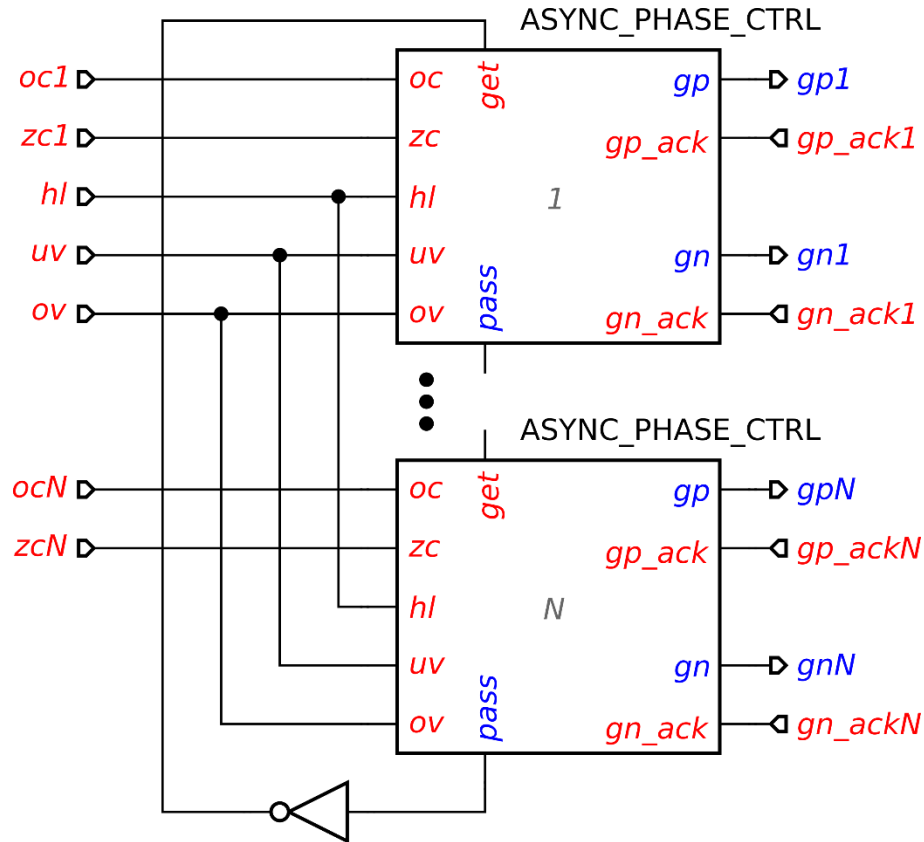


- Token ring instead of phase activation clock
- Response time of order of gate delays
- No dynamic power consumption when idle
- No need for synchronisers – all signals are asynchronous
- A4A design flow

Simulation results

synchronous @ 333MHz

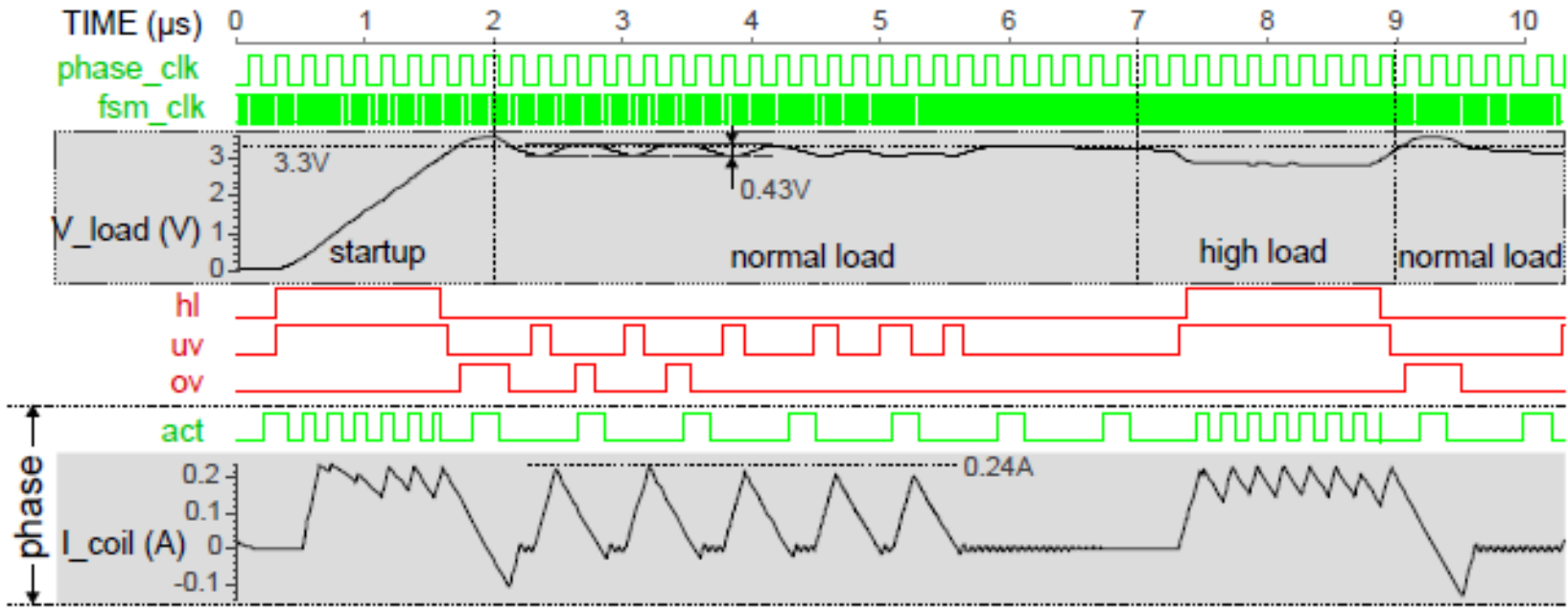

asynchronous

 


Reaction time


Buck controller	HL (ns)	UV (ns)	OV (ns)	OC (ns)	ZC (ns)
SYNC @ 100MHz	25.00	25.00	25.00	25.00	25.00
SYNC @ 333MHz	7.50	7.50	7.50	7.50	7.50
SYNC @ 666MHz	3.75	3.75	3.75	3.75	3.75
SYNC @ 1GHz	2.50	2.50	2.50	2.50	2.50
ASYNC	1.87	1.02	1.18	0.75	0.31
Improvement over 333MHz	4x	7x	6x	10x	24x

Synchronous buck controllers exhibit latency of 2.5 clock cycles.

Peak current

 

Inductor losses

 

Design Results

Design flow is automated to large extent

- Library of A2A components
- Automatic logic synthesis
- Formal verification at the STG and circuit levels

Analog-2-Async (A2A):
Wait, WaitX, Sample...

Benefits of asynchronous multiphase buck controller

- Reliable, no synchronization failures
- Quick response time (few gate delays)
- Reaction time can be traded off for smaller coils
- Lower voltage ripple and peak current