



# **Logic Synthesis and Implementation Styles in Asynchronous Circuits Design**


**[Victor.Khomenko@ncl.ac.uk](mailto:Victor.Khomenko@ncl.ac.uk)**

**School of Computing Science,**

**Newcastle University, UK**

 
# Speed-independence assumptions

- Gates/latches are **atomic** (so no internal hazards)




- Gate delays are positive and finite, but variable and unbounded
- Wire delays are negligible (SI)
- Alternatively, [some] wire forks are isochronic (QDI), i.e. wire delays can be added to gate delays

# SI decomposition

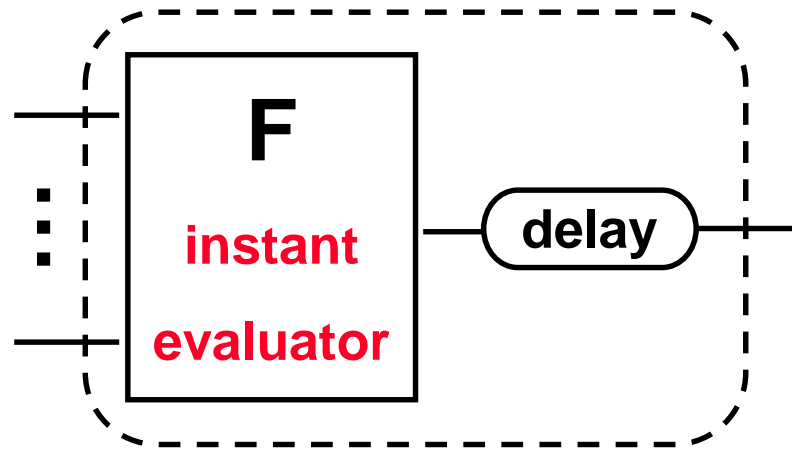

 Hazards can be introduced due to these delays!




# Gates & latches

- Good citizens: **unate** gates/latches, e.g. BUFFER, AND, OR, NAND, NOR, AND-OR, OR-AND, C-element, SR-latch, RS-latch
  - Output inverters ('bubbles') can be used liberally, e.g. NAND, NOR, as the inverter's delay can be added to the gate's delay
  - Input inverters are suspect as they introduce delays, but in practice are ok if the wire between the inverter and the gate is short
- Suspects: **binate** gates, e.g. XOR, NXOR, MUX, D-latch – may have internal hazards, but may still be useful

# Logic synthesis

- **Encoding (CSC) conflicts must be resolved first**
- **Several kinds of implementation can then be derived automatically:**
  - **complex-gate (CG)**
  - **generalised C-element (gC)**
  - **standard-C implementation (stdC)**
- **Can mix implementation styles on per-signal basis**
- **Logic decomposition may still be required if the gates are too complex**


# Example: complex-gate synthesis

 


Code	Nxt <sub>c</sub>
0100	1
0000	0
1000	0
0110	1
0010	0
1100	0
1110	1
1111	1
1101	1
else	-
Eqn	$(\bar{a}+c)b+d$

$$Nxt_z(s) = Code_z(s) \oplus Out_z(s)$$

 
**The size of this Boolean expression is not limited!**



# Support, triggers and context

 

 Signals whose occurrence can immediately enable a signal are called its **triggers**, e.g. the triggers of  $c$  are  $\{b, d\}$ . Triggers are unique, and are always in the support.




Signals that are the inputs of the gate producing a signal form its **support**, e.g. the support of  $c$  is  $\{a, b, c, d\}$ . Supports are not unique in general.

Signals in the support which are not triggers are called the **context**, e.g. the context of  $c$  is  $\{a, c\}$ . Context is not unique in general.

**support = triggers + context**


# Example: gC implementation

 

Code	Set <sub>c</sub>	Reset <sub>c</sub>
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-
Eqn	$\bar{a}b+d$	$\bar{b}$


$$Set_z(s) = \begin{cases} 1 & \text{if } Out_{z+}(s) = 1 \\ 0 & \text{if } Next_z(s) = 0 \\ - & \text{otherwise} \end{cases} \quad Reset_z(s) = \begin{cases} 1 & \text{if } Out_{z-}(s) = 1 \\ 0 & \text{if } Next_z(s) = 1 \\ - & \text{otherwise} \end{cases}$$

 Implemented as pull-up and pull-down networks of transistors + 'keeper'; assumed to be **atomic**; risk of transient short-circuit during initialisation







# Example: stdC implementation

 

Code	Set <sub>c</sub>	Reset <sub>c</sub>
0100	1	0
0000	0	-
1000	0	-
0110	-	0
0010	0	1
1100	0	-
1110	-	0
1111	-	0
1101	1	0
else	-	-

'Monotonic cover' constraints

Eqn	$\bar{a}b\bar{c}+d$	$\bar{b}$
-----	---------------------	-----------

  

# Logic Decomposition

- Often complex-gates are too complex to be mapped to a gate library, and so logic decomposition is required
- Cannot naïvely break up complex-gates – this is likely to introduce hazards (at least, timing assumptions are required)
- Decomposition is one of the most difficult tasks – no guarantee that automatic decomposition will succeed
- Online tutorial on logic decomposition and technology mapping:

[https://workcraft.org/tutorial/synthesis/technology\\_mapping/start](https://workcraft.org/tutorial/synthesis/technology_mapping/start)