


# Designing asynchronous circuits with timing conditions

Vision statement for possible CAD development under Workcraft


Original document:

A. Yakovlev, Synthesis from timing diagrams: rough notes and examples, Tech Memo, March 7, 1998; written on the basis of discussions with Ed Cerny and Luciano Lavagno
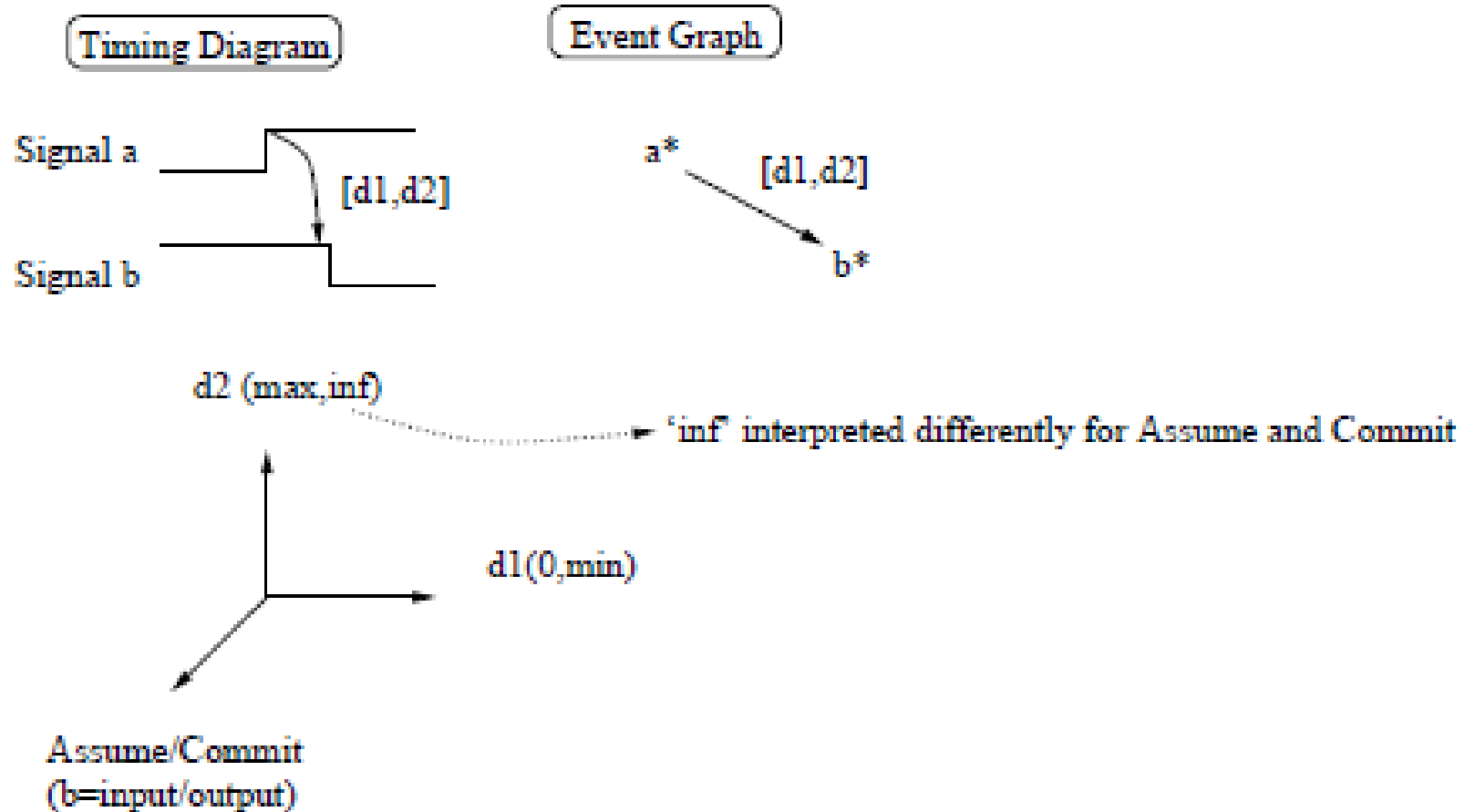
# Basic classification of timing conditions


 
# STG interpretation of Assume conditions



(1) Case  $d1 = 0, d2 = \infty$   
Corresponds to delay-independent handshake

(2) Case  $d1 = min > 0, d2 = \infty$   
Corresponds to delayed (by min value) response from the environment

(3) Case  $d1 = 0, d2 = max < \infty$   
Corresponds to bounded response, e.g. from clock signal

(4) Case  $d1 = min > 0, d2 = max < \infty$   
Combination of (2) and (3), i.e. imaginary handshake with input clock

STG

$d1=0 \quad d2=\text{inf}$

$b+ \dots \rightarrow a-$   
delay-independent handshake

$d1=\text{min} \quad d2=\text{inf}$

$b+ \xrightarrow{> d1} a-$   
"delayed" response


$d1=0 \quad d2=\text{max}$

$b+ \xrightarrow{< d2} a-$   
"fast" handshake

$d1=\text{min} \quad d2=\text{max}$

{can be used as one of the above}

# STG interpretation of commits

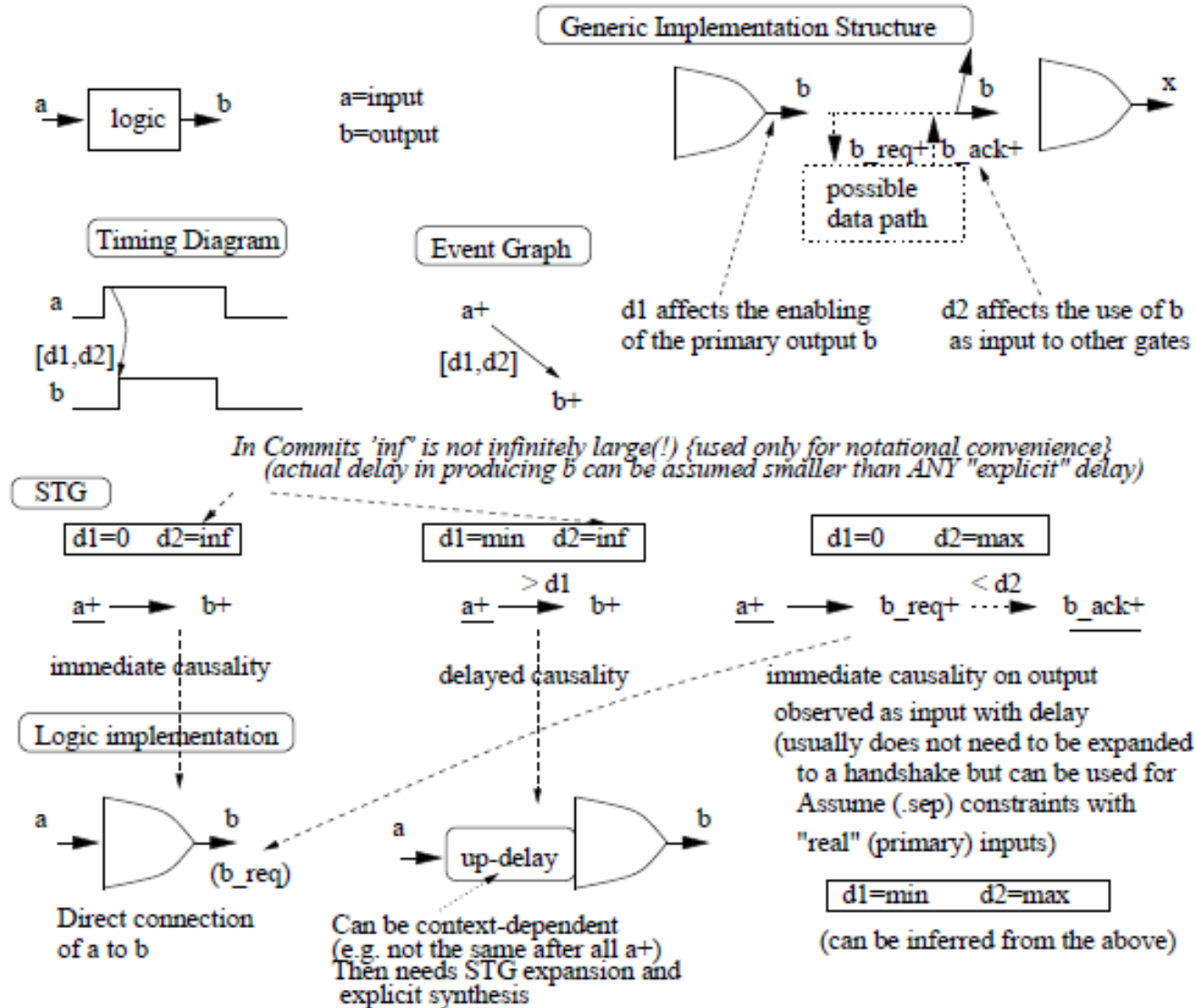

(1) Case  $d1 = 0, d2 = \infty$

Corresponds to immediate causality between input a and the logic producing output b

(2) Case  $d1 = min > 0, d2 = \infty$

Corresponds to delayed causality, e.g. for producing skew compensation (bundled data strobe or setup)



(3) Case  $d1 = 0, d2 = max < \infty$

Corresponds to immediate causality but observing of the output b may be after some (up to max) delay

(4) Case  $d1 = min > 0, d2 = max < \infty$

Combination of (2) and (3)

# Simple buffer example

  

Initial Constraints:


Commit:  
 $a+ \xrightarrow{[d1, d2]} b+$

Assume:  
 $a+ \xrightarrow{[d3, d4]} a-$

Let  $d2 < d3$ :


Hence (via Timing Analysis) we have a new Assume .sep  $b+ < a-$  ( $b+$  before  $a-$ )  
 Since this .sep affects input ( $a-$ ) we introduce an explicit arc

Modelling style 1:  
 (event-driven)

 


STG output-persistent by construction  
 but inbounded without "Assume"


Modelling style 2:  
 (level-driven)

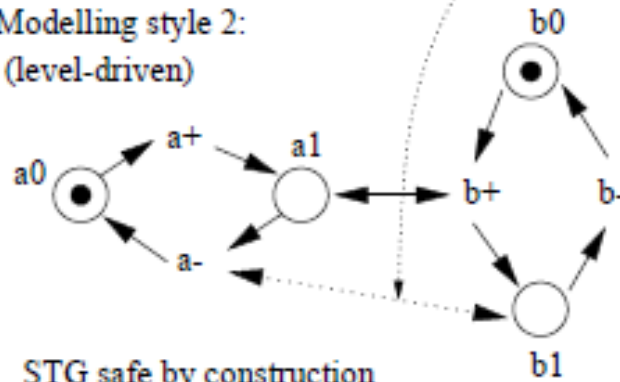

 
STG safe by construction  
 but not out-persistent without "Assume"



 This transition is impossible due to "Assume"





# Clocked write controller

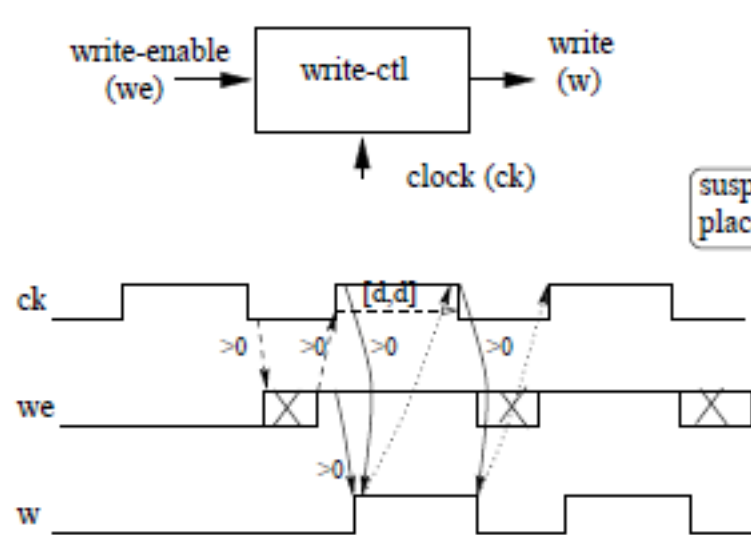

Constraints:

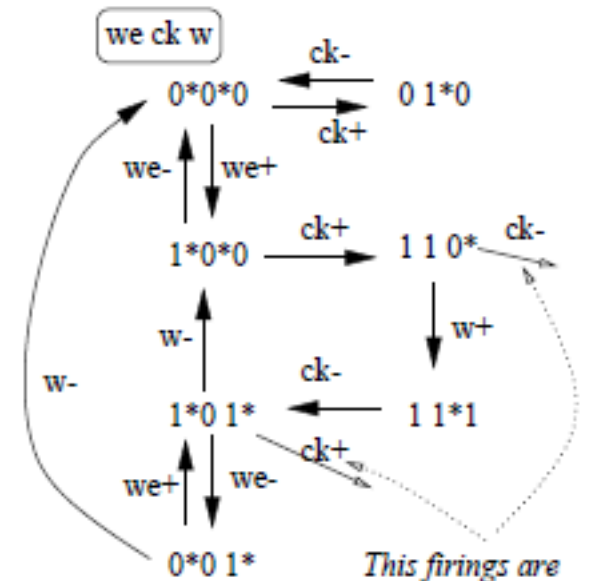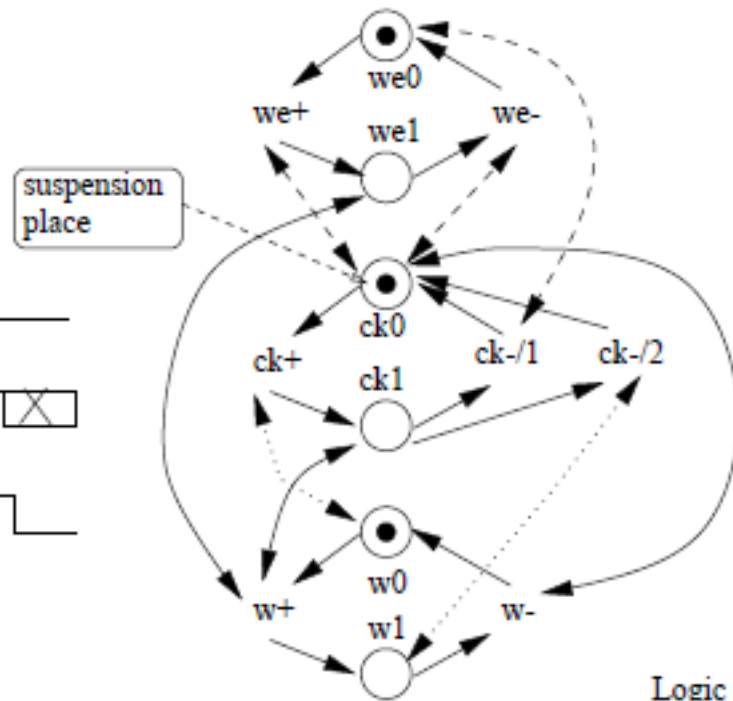- causal commit
- order assume input-input
- ..... order assume output-input




Logic implementation:

$$w = ck\ we$$

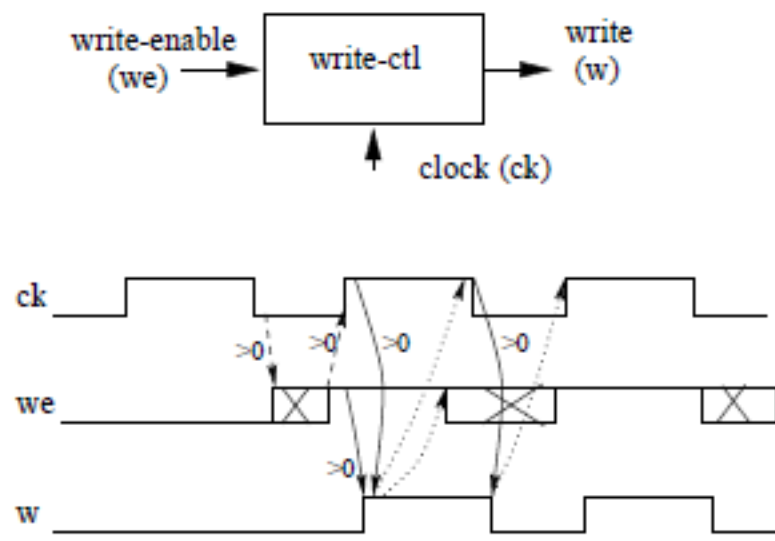
# Very simple clocked write controller

Here we allow 'we' to resume its change after 'w' goes high



Constraints:

 
- causal commit
- order assume input-input
- ..... order assume output-input




Logic implementation:

$$w = ck\ we + ck\ w$$

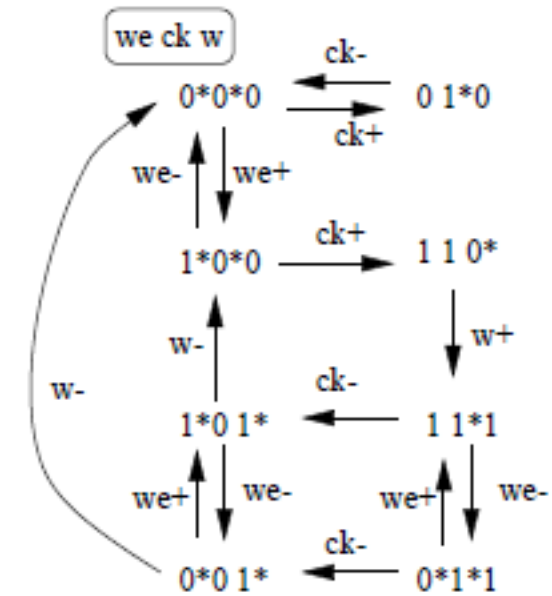$w = ck\ we$  if, additionally, `.sep ck-/1 < we-` is applied





# Clocked D-latch

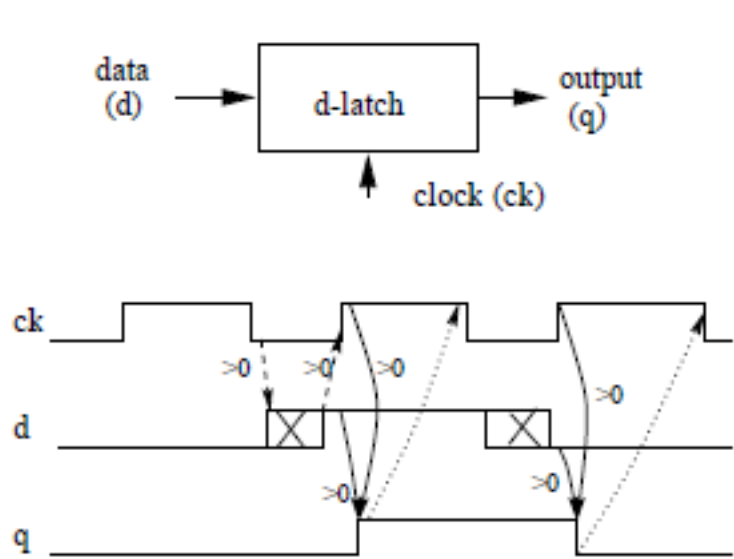

Constraints:

 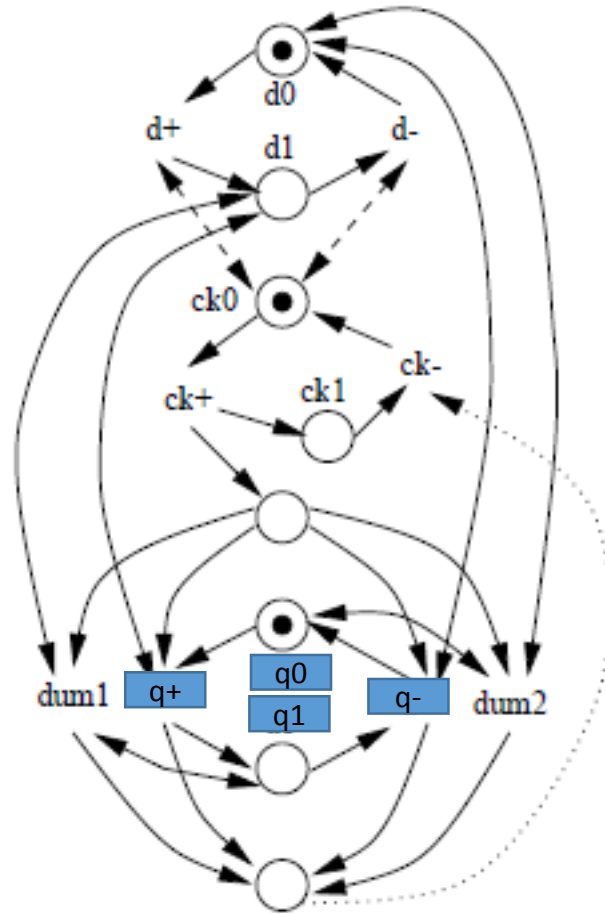- causal commit
- order assume input-input
- ..... order assume output-input




Logic implementation:

$$q = ck d + ck' q$$


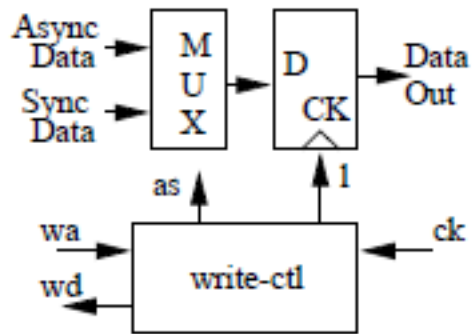
# Dual (Sync/Async) mode write ctl with external choice



Mode (as):  
 $async=1$   
 $sync=0$

Possible constraints in async part:  
 commit:

C1:  $l+1 \rightarrow l-1$  ( $\geq \min$ )

C2:  $wa- \rightarrow l-1$

C3:  $l-1 \rightarrow wd-$


assume:

to help csc or logic

A1:  $l-1 \rightarrow wa+$   
 (a bit milder than C3)

also: commit on set-up delay

C4: before  $l+1$  and  $l+2$  (???)

 

Logic implementations:

(1) no constraints in async part:

$$wd = csc0 (wa \ l + wd)$$

$$as = as \ ck' + wa$$

$$l = csc0 (wd' (as + 1) + ck)$$

$$csc0 = l' (as' + wa) + csc0 (ck + wa)$$

(2) with C2

$$wd = csc0 \ as \ (1 + wa')$$

$$as = as \ ck' + wa$$

$$l = csc0 (wa \ as + as' \ 1 + ck)$$

$$csc0 = l' (as' + wa) + csc0 (ck + wa)$$


(3) with C3 or with A1:

$$wd = as \ l$$

$$as = wa + as \ ck'$$

$$l = wa \ as + ck \ as'$$
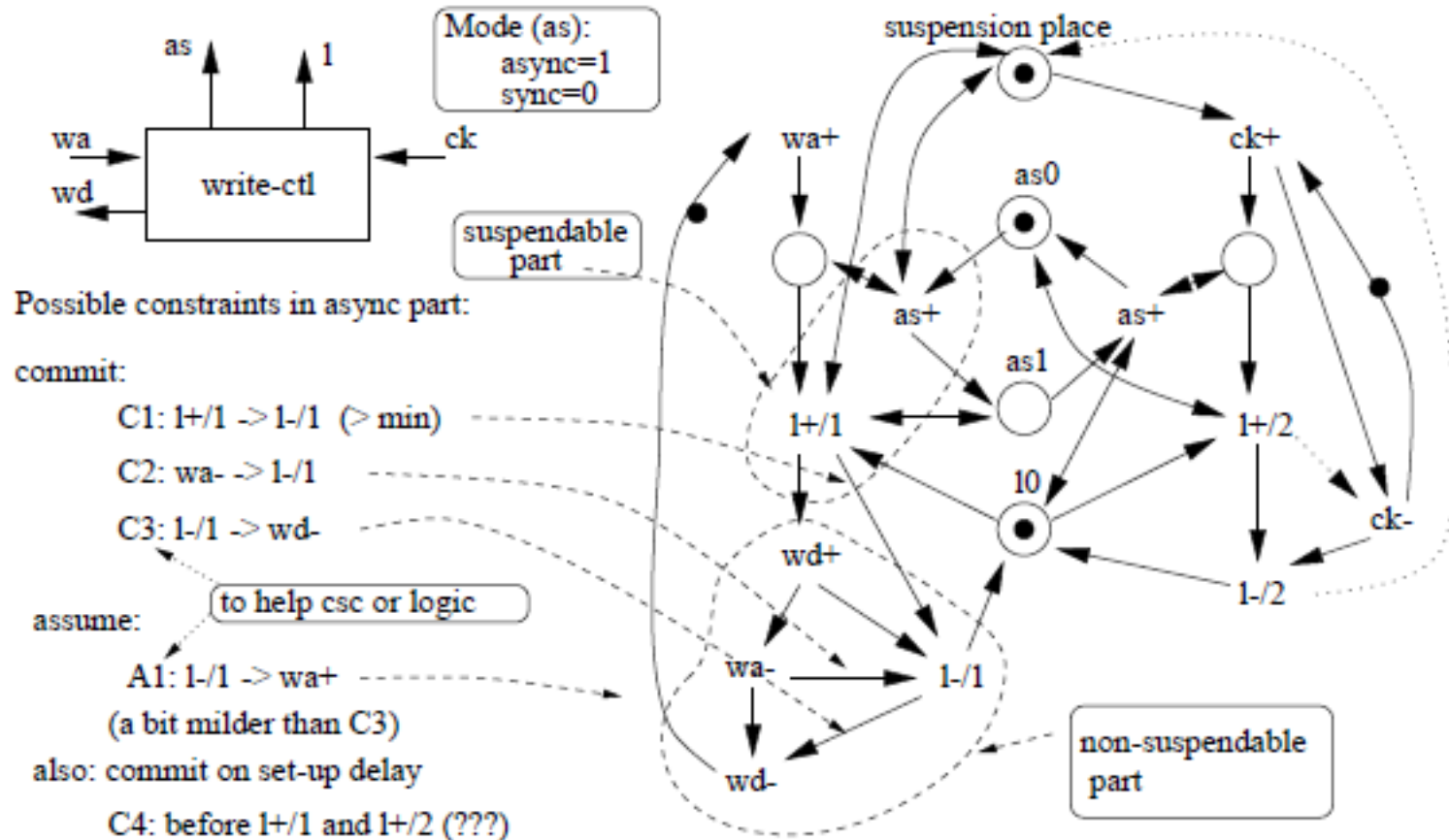
# Dual (Sync/Async) mode write ctl with pre-emption by Sync



Logic implementations:


(1) no constraints in async part:

$$\begin{aligned}
 wd &= csc0 (as \ 1 + wd) \\
 as &= wa \ ck' \ wd' \ 1' + as (ck' + 1) \\
 1 &= csc0 \ wd' \ as (ck' + 1) + ck \ as' \\
 csc0 &= wa (1 + csc0 + as')
 \end{aligned}$$

(3) with C3:


$$\begin{aligned}
 wd &= as \ 1 \\
 as &= wa \ ck' \ 1' + as (1 + ck') \\
 1 &= wa \ ck' \ as + ck (wa \ 1 + as')
 \end{aligned}$$
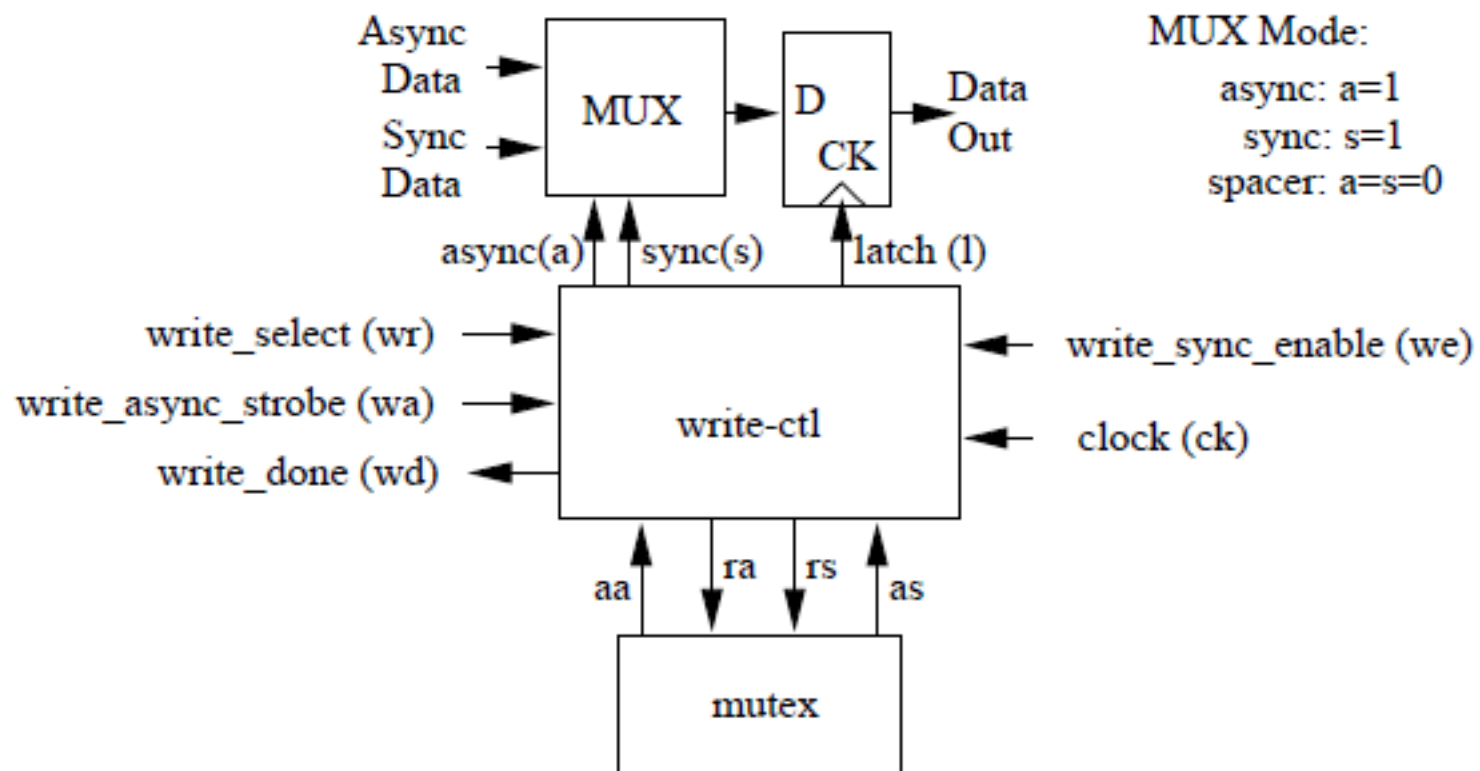
# Dual (Sync/Async) mode write ctl with Mutex



# Dual mode write ctl: timing diagrams

Async1

 

special commit constraints:


\* maybe min set-up time

\*\* maybe min hold time

special assume constraint:


\*\*\* length of clock pulse must allow for at least one mutex tenure on async (to avoid missing sync cycles)

Async 2

 


max mutex tenure

Sync

 
 
# Dual mode write ctl with Mutex: STG and logic




Logic implementation:

$$\begin{aligned}
 wd &= aa \cdot l + wd \cdot (aa + wa) \\
 a &= wd' \cdot aa \\
 s &= ck \cdot as \\
 l &= wd' \cdot a + ck \cdot s \\
 ra &= wa \cdot wr \cdot wd' + l \cdot aa + a \\
 rs &= l \cdot as + we \cdot ck + s
 \end{aligned}$$

With extra commits ( $wa-/1 \rightarrow \{a-, l-/1\}$ ):

$$\begin{aligned}
 wd &= l \cdot a + wd \cdot aa \\
 a &= wa \cdot aa \\
 s &= as \cdot ck \\
 l &= wa \cdot a + ck \cdot s \\
 ra &= l \cdot aa + wr \cdot wa + a \\
 rs &= l \cdot as + we \cdot ck + s
 \end{aligned}$$
 
# Example of Z84 write i/f: Initial Event Graph




Constraint types:  $\text{commit} (\{I, O\} \rightarrow O)$  and  $\text{assume} (\{I, O\} \rightarrow I)$

commit 1 (C1):  $[0, \text{max}]$  or  $[0, \text{inf}] \Rightarrow$  'immediate causal' ASAP (for enabling); but maybe as long as max if with max, this can be used as assume (?)

commit 2 (C2):  $[\text{min}, \text{inf}] \Rightarrow$  'delayed causal' ASAP (via min delay); must not be less than min

assume (A):  $[\text{min}, \text{max}] \Rightarrow$  'timing assumptions' to avoid inconsistency, nonpersistence, state coding conflicts and to optimize logic (wrt area and/or speed)

 Example with Z84  
write i/f: deriving  
STG from initial  
constraints



Constraint types:  $\text{commit} (\{I,O\} \rightarrow O)$  and  $\text{assume} (\{I,O\} \rightarrow I)$


$\text{commit 1 (C1)}$ :  $[0, \max]$  or  $[0, \text{inf}] \Rightarrow$  'immediate causal' ASAP (for enabling); but maybe as long as max  
 if with max, this can be used as assume (?)

$\text{commit 2 (C2)}$ :  $[\min, \text{inf}] \Rightarrow$  'delayed causal' ASAP (via min delay); must not be less than min

$\text{assume (A)}$ :  $[\min, \max] \Rightarrow$  'timing assumptions' to avoid inconsistency, nonpersistence, state coding conflicts  
 and to optimize logic (wrt area and/or speed)

*Additional assume constraints inferred from C1 (with max) and A to help state coding and logic*
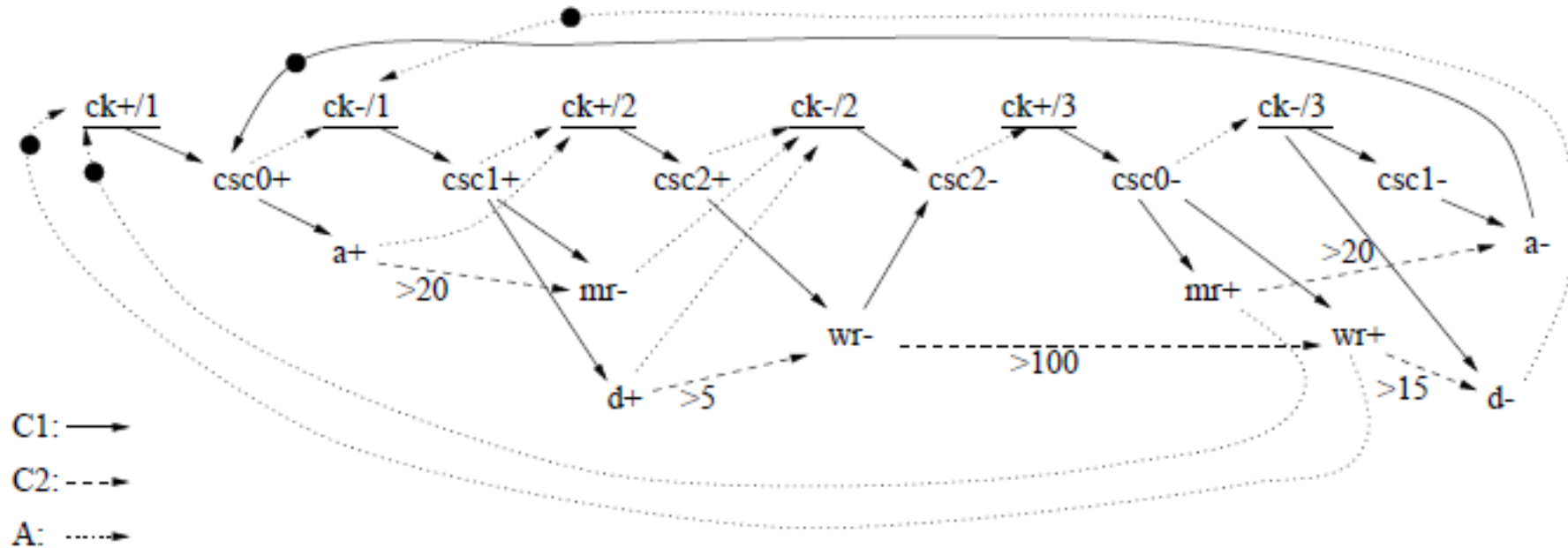
# Example with Z84 write i/f: STG-based synthesis



Logic implementation:

$$a = csc0 + csc1 + \overline{mr}$$

$$\overline{mr} = (csc0 \overline{csc1} a)$$

$$\overline{wr} = csc0 \overline{d} + csc2 \overline{wr}$$

$$d = csc1(csc0 + ck) \overline{wr}$$

$$csc0 = csc2 + ck a' + csc0 (ck' + wr)$$


$$csc1 = csc0 ck' + csc1 ck$$

$$csc2 = ck wr csc0 csc1 + csc2 (ck + wr)$$

commit C2 constraints have to be satisfied by inserting delays into trigger inputs


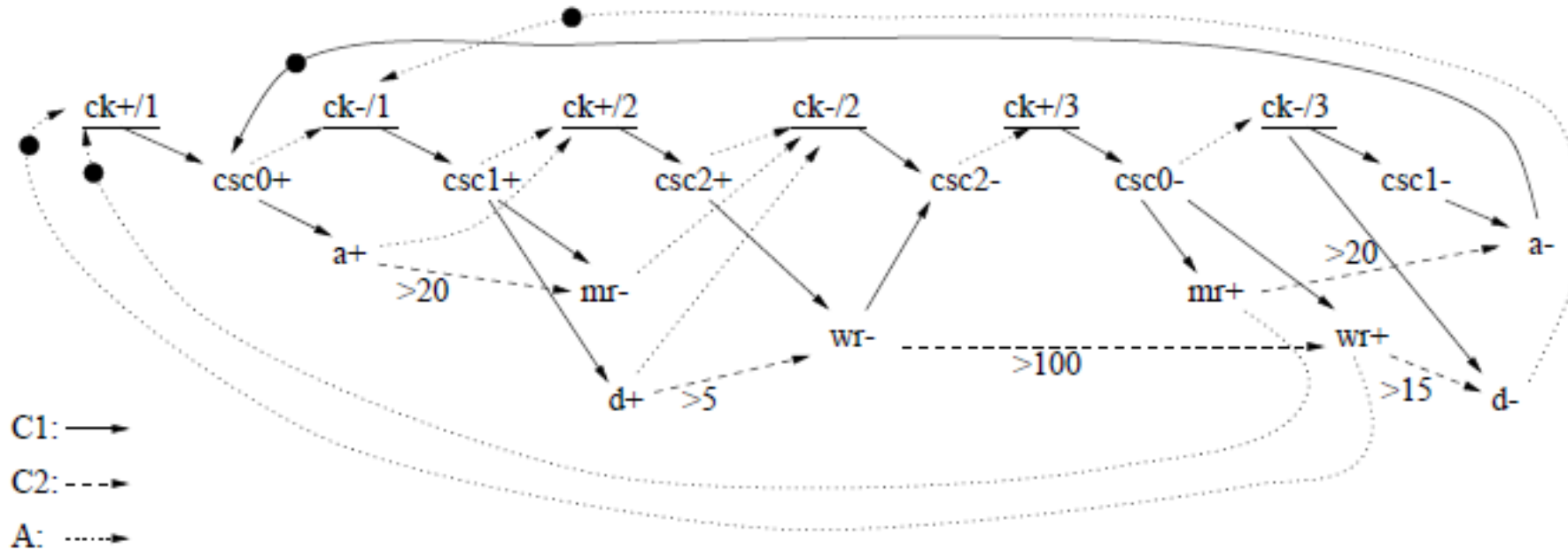
# Example with Z84 write i/f: using stricter (burst) constraints



Logic implementation:

$$a = csc0 + csc1 + \underline{mr}$$

$$\underline{mr} = (csc0 \ csc1 \ a)$$

$$\underline{wr} = csc0' + \underline{d}' + csc2' \ \underline{wr}$$

$$\underline{d} = csc1(csc0 + ck) \ \underline{wr}$$

$$csc0 = csc2 + ck \ a' + csc0 (ck' + \underline{wr})$$

$$csc1 = csc0 \ ck' + csc1 \ ck$$

$$csc2 = ck \ \underline{wr} \ csc0 \ csc1 + csc2 (ck + \underline{wr})$$

commit C2 constraints have to be satisfied by inserting delays into trigger inputs

# STG synthesis problems

**Problem 5.1** *Given a Timing Diagram specification (or better say, an Event Graph, whose arcs are annotated with timing constraints), synthesize an ‘equivalent’ STG with three types of arcs (or places and arcs if choice is involved): “immediate causality” arcs, “delayed causality” arcs and “input order” arcs.*

**Problem 5.2** *Find an optimal (speed/area of future logic) asynchronous schedule in terms of “precedence” (b always occurs after a) and “delayed precedence” (b always occurs after a with a delay of  $\delta$  units <sup>4</sup>) arcs that satisfies the original Timing Diagram (Event Graph).*

# Related work

A. El-Aboudi, E. -. Aboulhamid and E. Cerny, "Synthesis of interface controllers from timing diagram specifications," *Proceedings of the IEEE 1998 Custom Integrated Circuits Conference (Cat. No.98CH36143)*, Santa Clara, CA, USA, 1998, pp. 89-92.

doi: 10.1109/CICC.1998.694913

P. Vanbekbergen, G. Goossens and H. De Man, "Specification and analysis of timing constraints in signal transition graphs," [1992] *Proceedings The European Conference on Design Automation*, Brussels, Belgium, 1992, pp. 302-306.

doi: 10.1109/EDAC.1992.205943

K. -. Chung, R. K. Gupta and C. L. Liu, "An algorithm for synthesis of system-level interface circuits," *Proceedings of International Conference on Computer Aided Design*, San Jose, CA, USA, 1996, pp. 442-447.

doi: 10.1109/ICCAD.1996.569835